


Chapter 4

**DC-DC Converters
(DC Choppers)**



DC choppers = DC-to-DC converters

A chopper can be considered as a DC equivalent to an AC transformer with a continuously variable turns ratio. Like a transformer, it can be used to step-down or step-up a DC voltage source.

A DC-DC Converter System

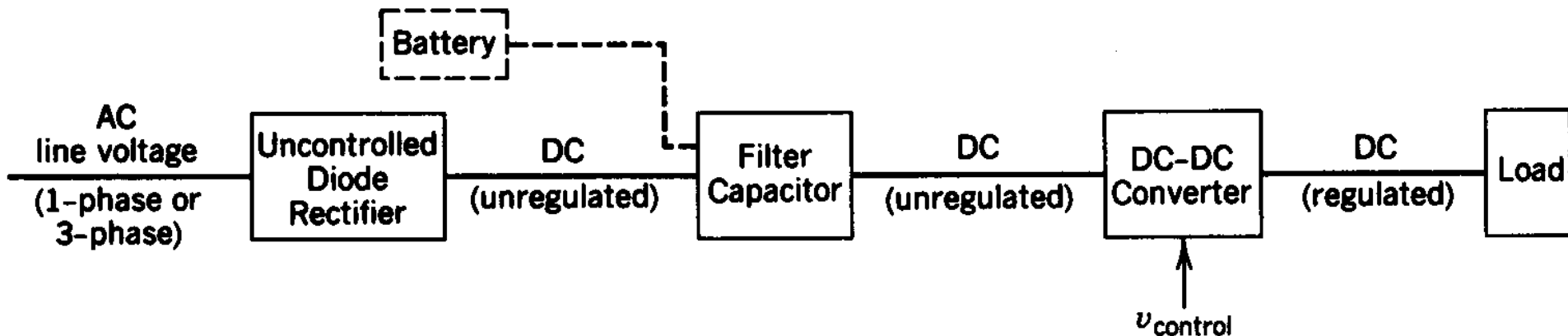

Basic Principle

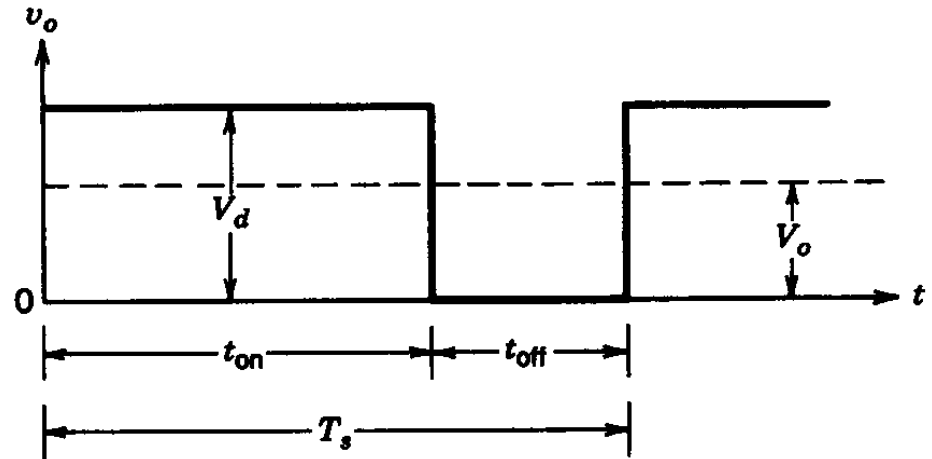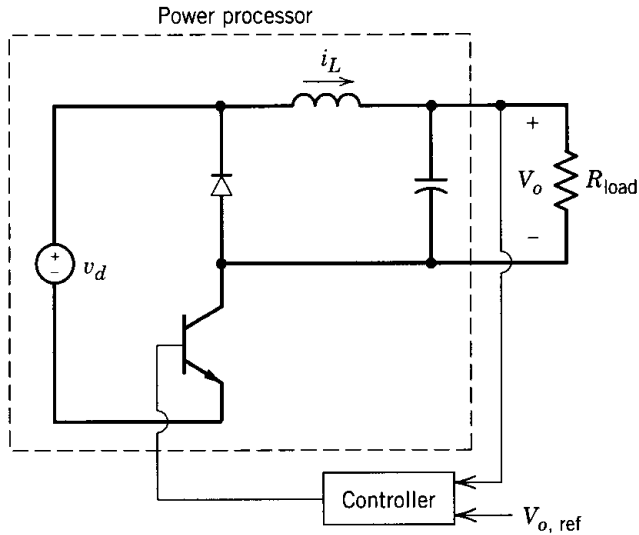


$$V_o = \frac{1}{T_s} \int_0^{t_{on}} v_o dt = \frac{t_{on}}{T_s} V_d = f_s t_{on} V_d = D V_d$$

D – duty ratio


2 methods to control the output voltage:

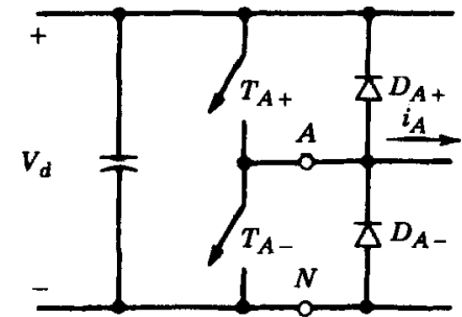- 1) frequency fixed, on-duration adjusted -- PWM
- 2) Both frequency and on-duration adjusted.




Basic Unit of PWM circuit

Modulation of DC-DC converters by PWM

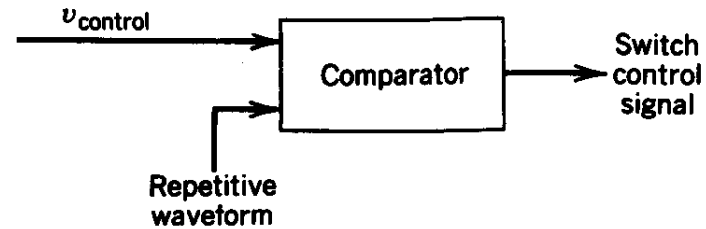

(a)

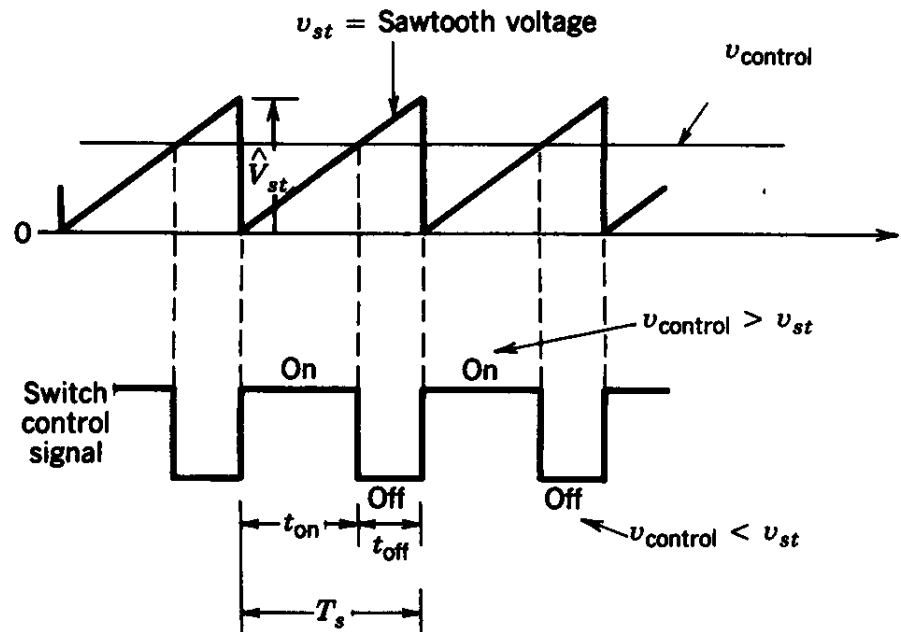

(switching frequency $f_s = \frac{1}{T_s}$)



(b)

Basic topologies of DC-DC Converters:


- 1 Buck regulators (step-down)**
- 2 Boost regulators (step-up)**
- 3 Buck-Boost regulators**
- 4 Cuk regulators**
- 5 Full-bridge regulators**

a key term: PWM (pulse-width modulation)



DC-DC Choppers

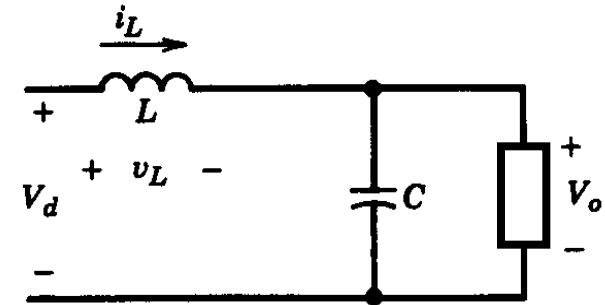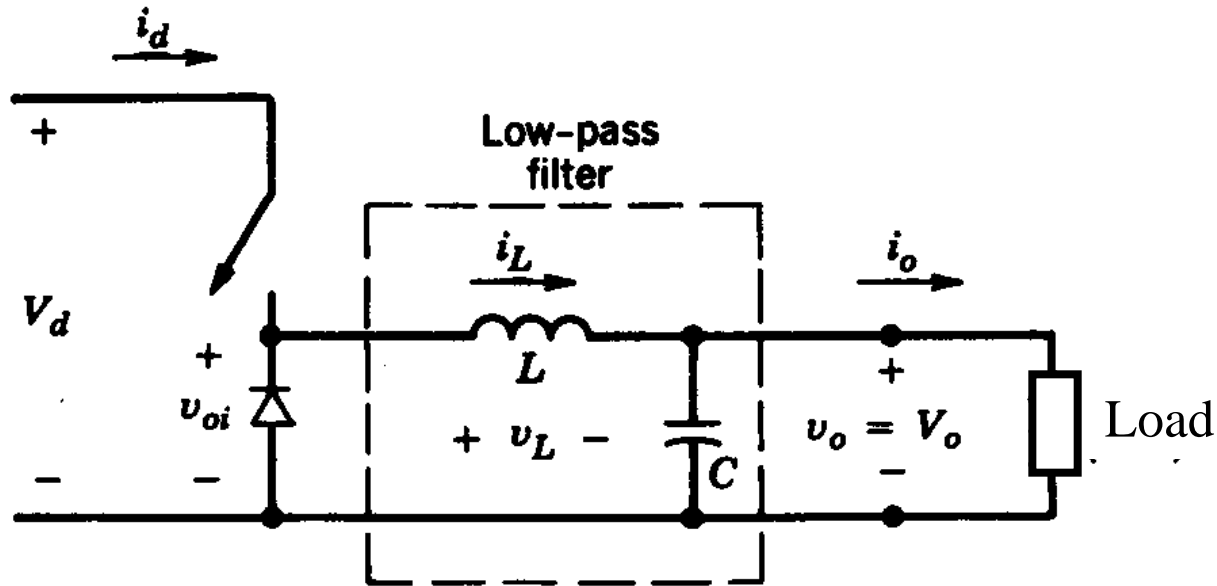

Mode 1 — on

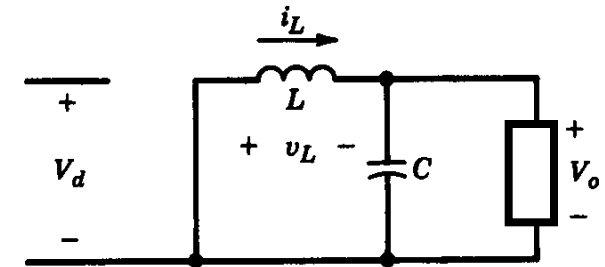

Mode 2 — off

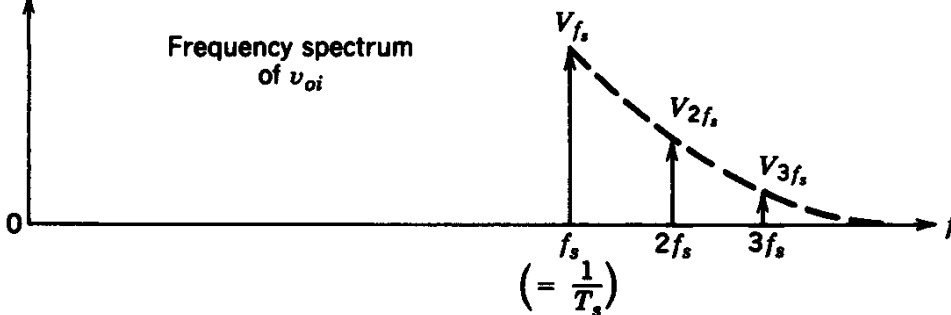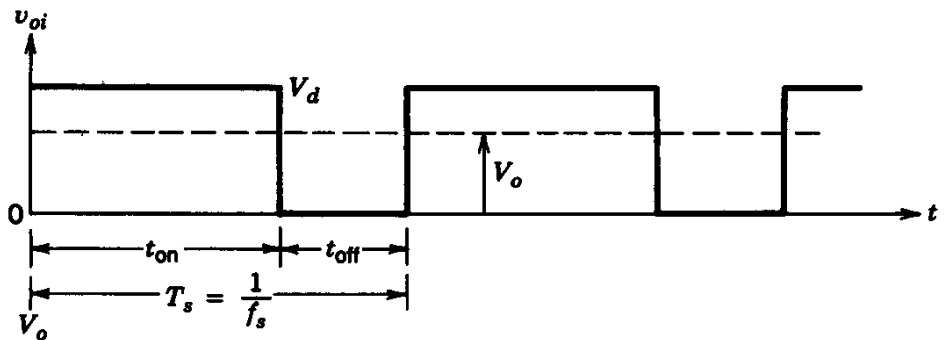

5-1. Buck Regulators

Focus on steady state

Continuous-conduction



inductor current positively continuous

C1: Capacitor voltage can be seen as constant unless the purpose is for voltage ripple calculation (capacitor large enough)


C2: $I_C = 0$ ($I_L = I_o$), $V_L = 0$ in a cycle

Assuming i_L rises linearly by ΔI_L in time t_{on}

Assuming i_L drops linearly by ΔI_L in time t_{off}

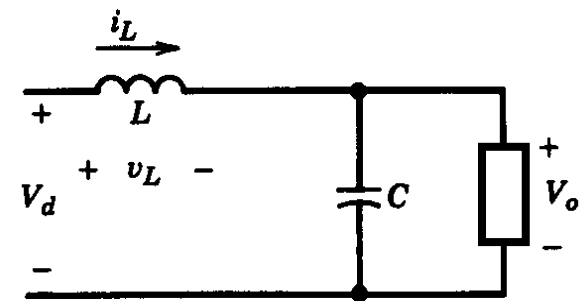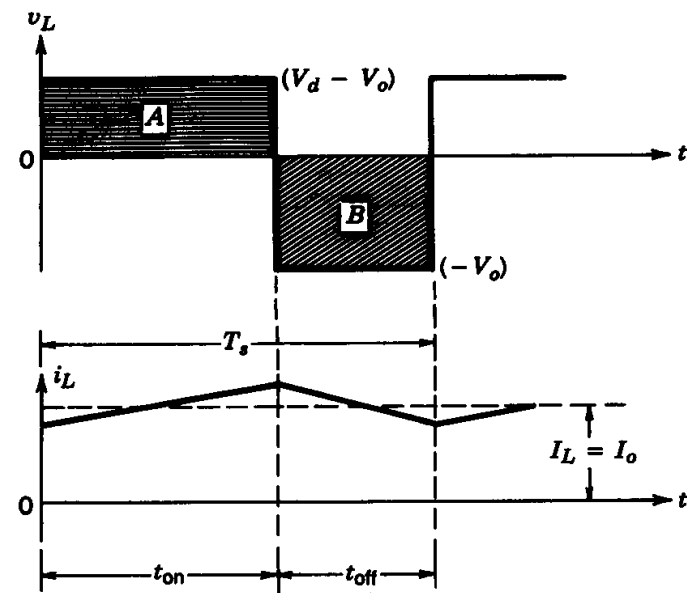

Mode 1 — on

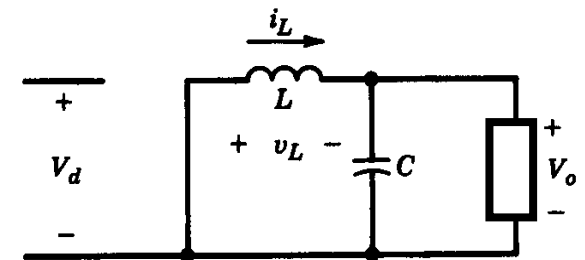

Mode 2 — off

$$V_d - V_o = L \frac{\Delta I_L}{t_{on}}$$

$$-V_o = -L \frac{\Delta I_L}{t_{off}}$$

$$V_o = DV_d$$


equal to that before LC

$$V_d * I_d = V_o * I_o$$


$$I_d = DI_o$$

$$\Delta I_L = \frac{V_d D(1-D)}{f_s L}$$


Output Voltage Ripple

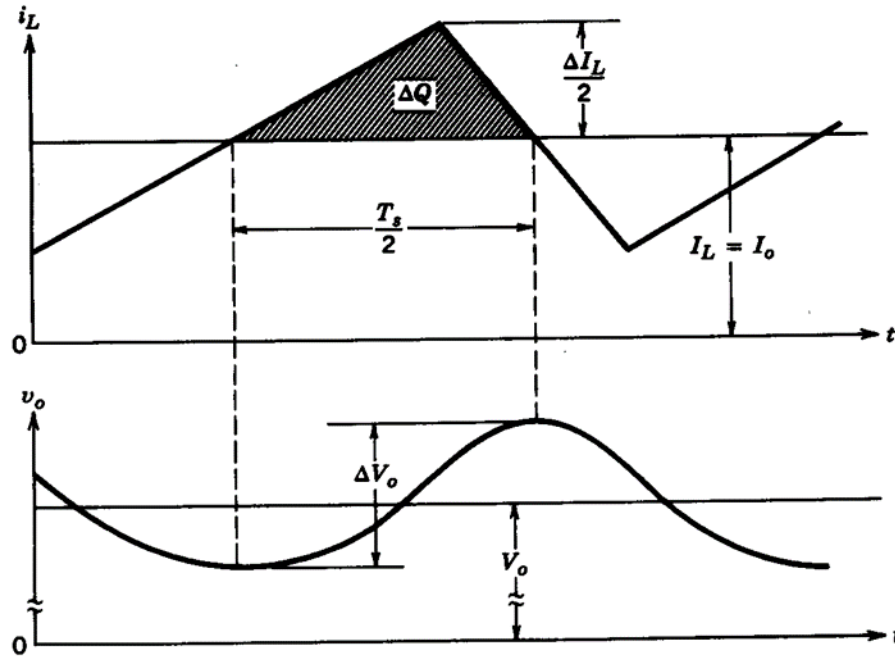

$$\Delta V_o = \frac{V_d D(1-D)}{8LCf_s^2}$$

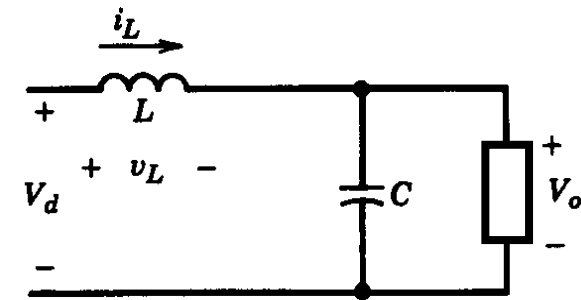

Mode 1 — on

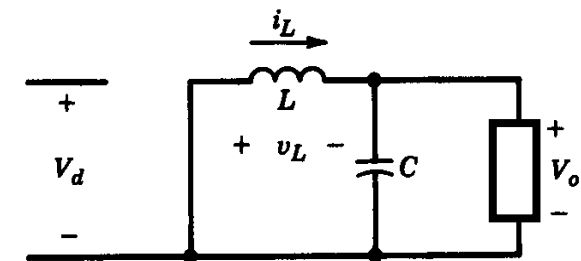


Mode 2 — off

Discontinuous-conduction



inductor current is discontinuous

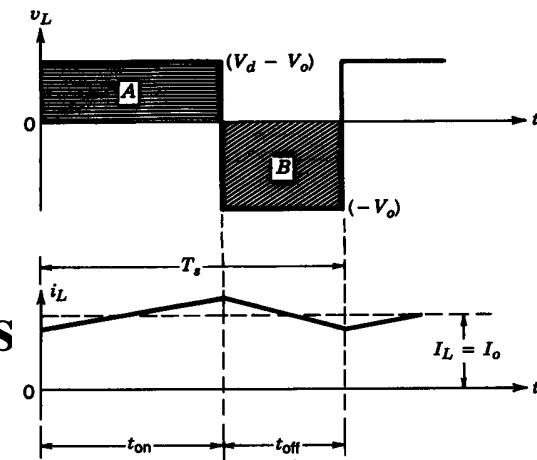Boundary between continuous and discontinuous



$$I_{LB} = I_{oB} = 0.5\Delta I_L$$

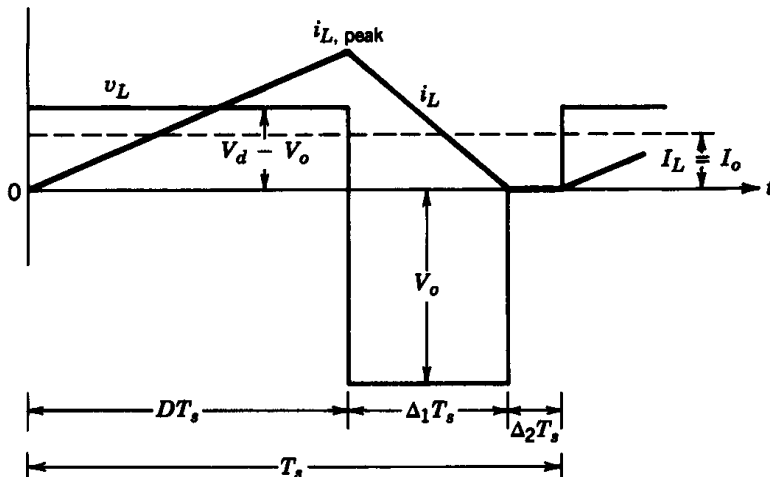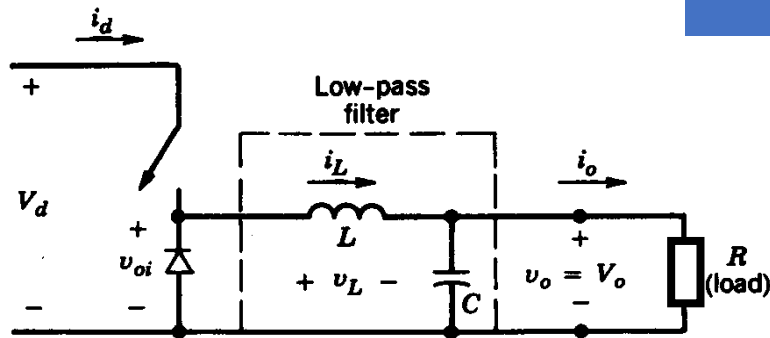
$$\Delta I_L = \frac{V_d D(1-D)}{f_s L}$$



In steady state, the average inductor voltage must be zero.



$$\frac{V_o}{V_d} = \frac{D}{D + \Delta_1}$$

$$\Delta_1 = \frac{2f_s L}{V_d D} I_o$$

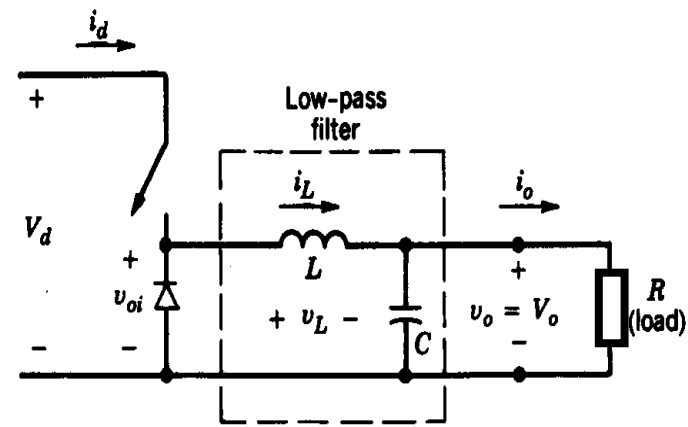


Characteristics of Buck circuits:

1. step-down ;
2. simple, requiring only one *device*;
3. high efficient (>90%);
4. the input current discontinuous and a smoothing input filter normally required;
5. providing only positive output voltage and unidirectional output current.

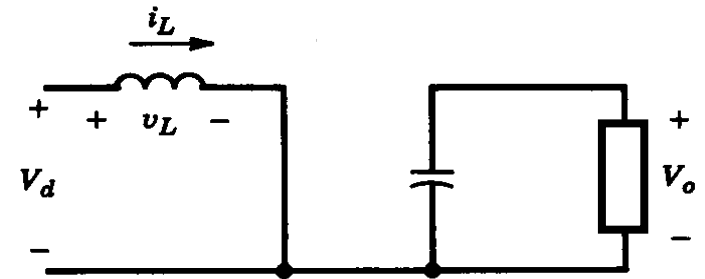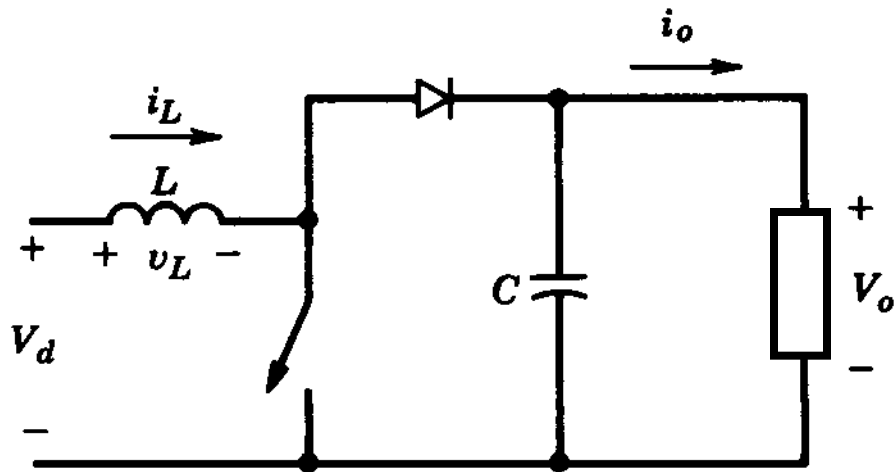

Mode 1 — on

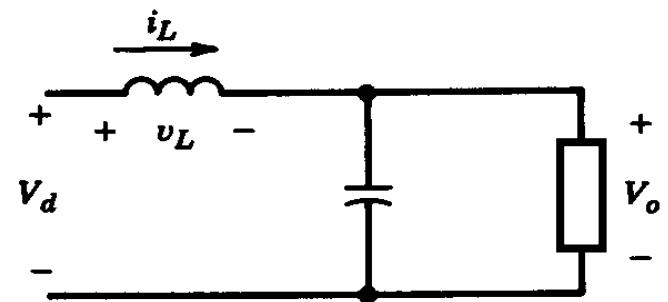

Mode 2 — off

5-2. Boost Regulators

Continuous-conduction

C1 and C2 are still feasible

Assuming i_L rises linearly by ΔI_L in time t_{on}

Assuming i_L drops linearly by ΔI_L in time t_{off}

$$V_d = L \frac{\Delta I_L}{t_{on}}$$



$$V_d - V_o = -L \frac{\Delta I_L}{t_{off}}$$

$$V_o = \frac{V_d}{1-D}$$


$$V_d * I_d = V_o * I_o$$

$$I_d = \frac{I_o}{1-D}$$

$$\Delta I_L = \frac{V_d D}{f_s L}$$

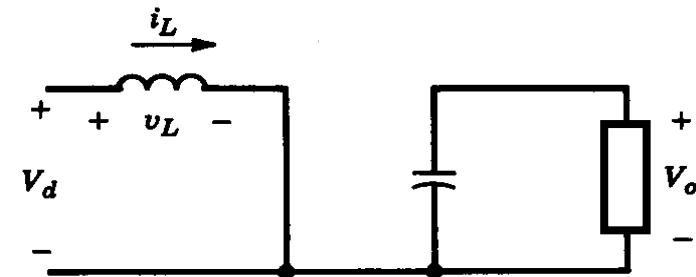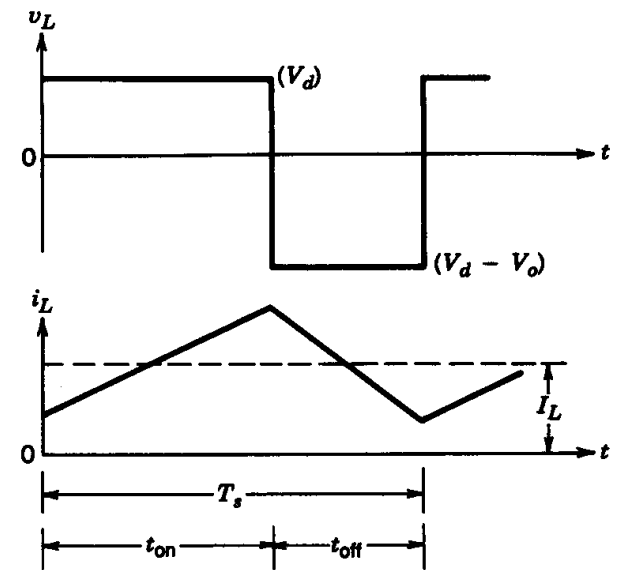


Mode 1 — on

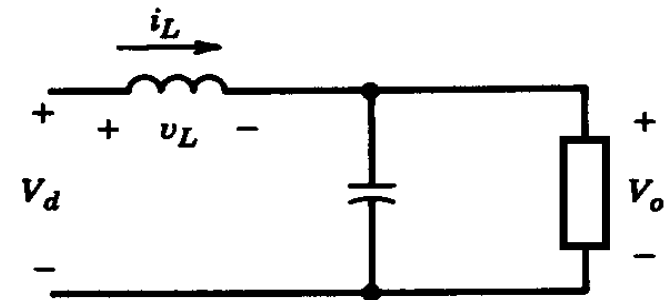


Mode 2 — off


Output Voltage Ripple

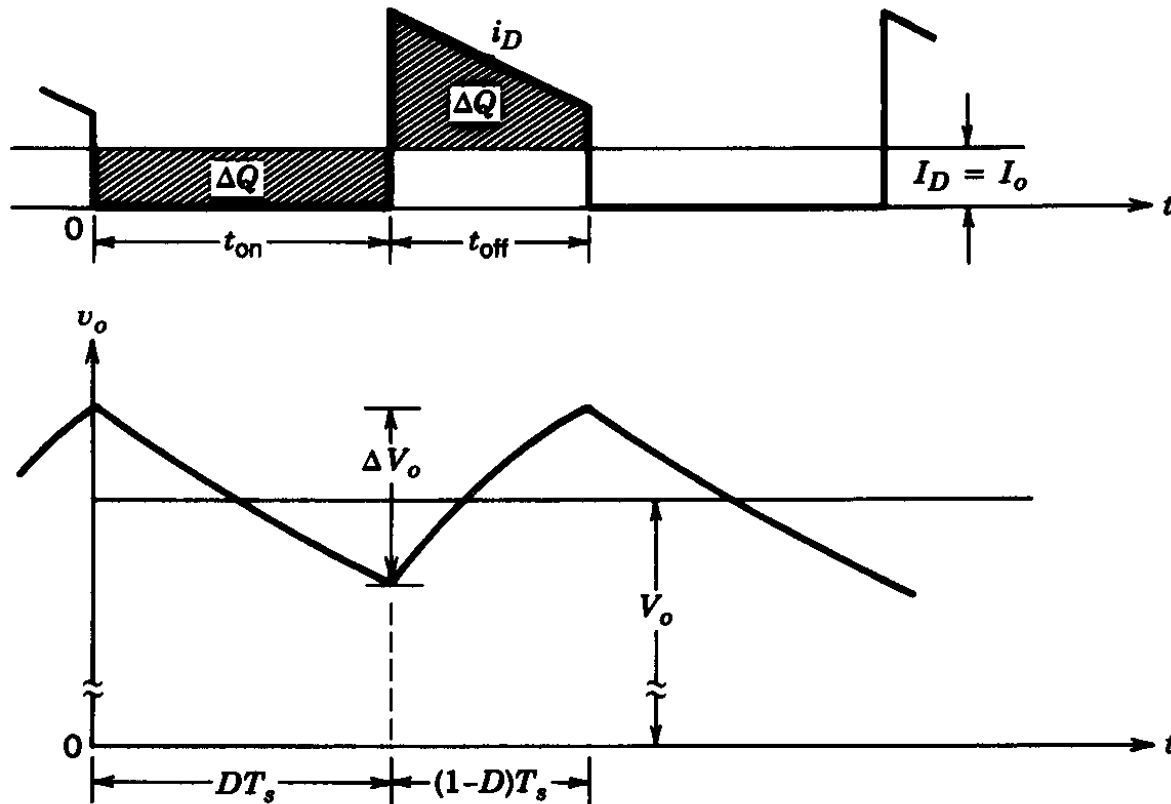

$$\Delta V_o = \frac{I_o D}{f_s C}$$

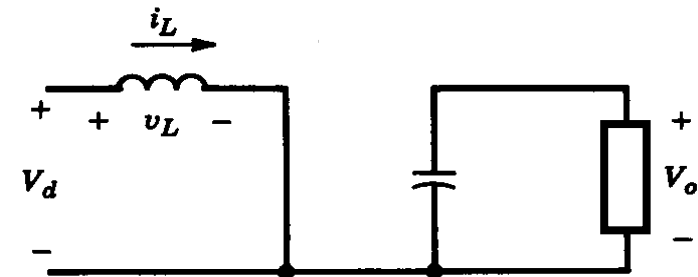



Mode 1 — on

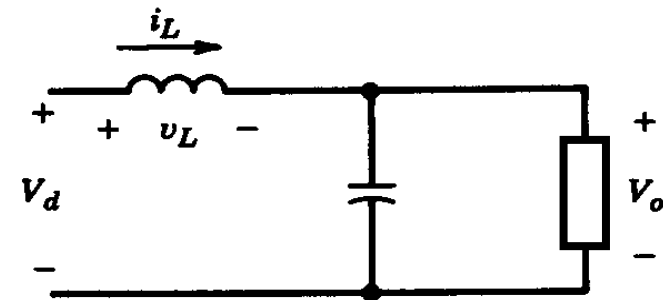

Mode 2 — off

Discontinuous-conduction

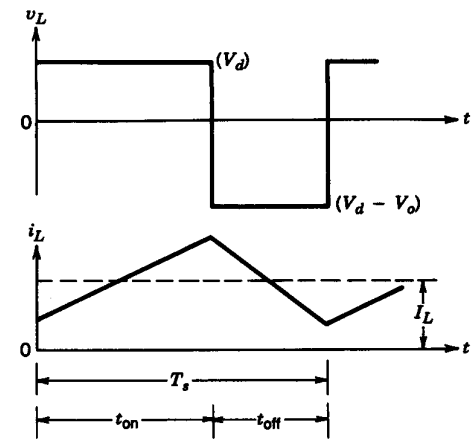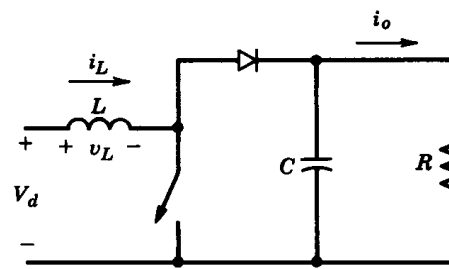
Boundary between continuous and discontinuous



$$I_{LB} = 0.5 \Delta I_L$$

$$I_{oB} = I_{LB}(1-D)$$

$$\Delta I_L = \frac{V_d D}{f_s L}$$

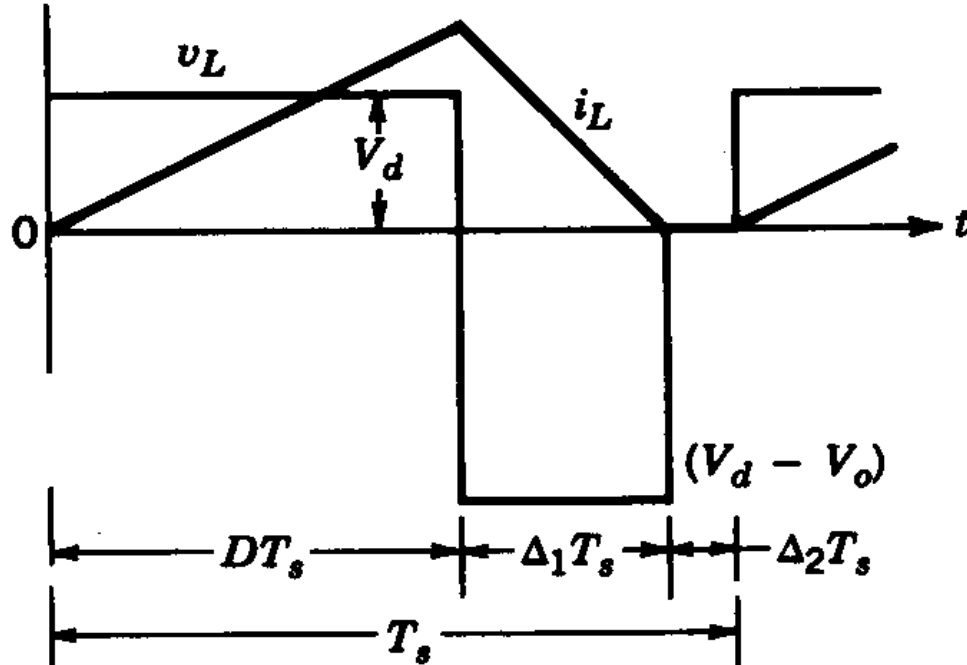


In steady state, the average inductor voltage must be zero.

$$\frac{V_o}{V_d} = \frac{\Delta_1 + D}{\Delta_1}$$


$$\Delta_1 = \frac{2 f_s L}{V_d D} I_o$$

Characteristics of Boost circuits:

1. step-up;
2. simple, requiring only one device;
3. high efficient;
4. input current continuous;
5. output voltage very sensitive to changes in duty cycle k , making it difficult to stabilize the regulator;
6. average output current less than the average inductor current by a factor of $(1-D)$ and a much higher rms current flowing through the filter capacitor, resulting in the use of a larger filter capacitor than those of a Buck regulator.




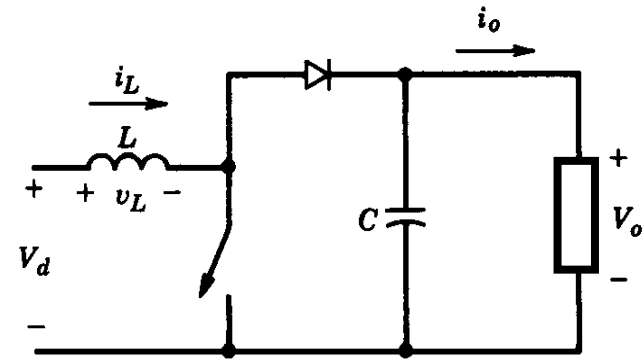




Supplement 4-1 Buck-Boost: Cascade of Buck and Boost

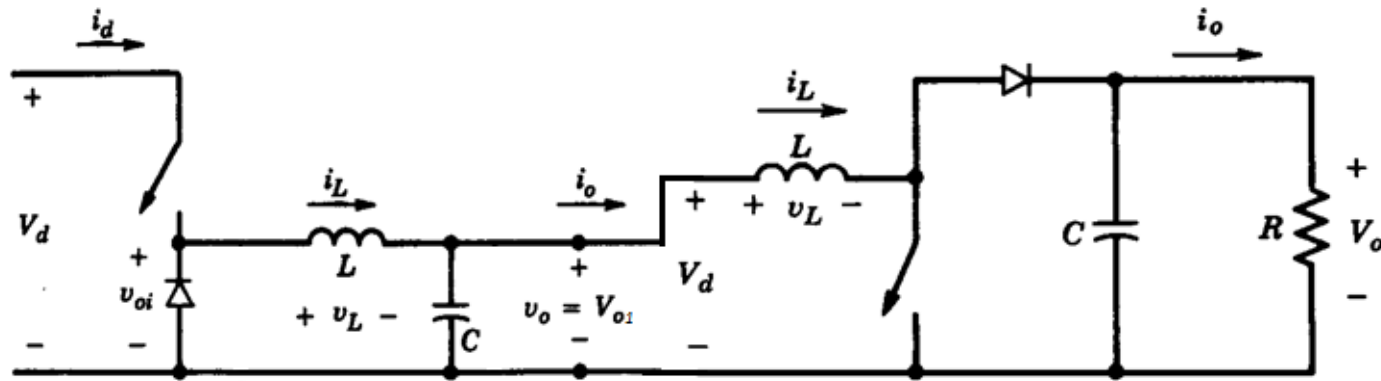


Mode 1 — on

Mode 2 — off

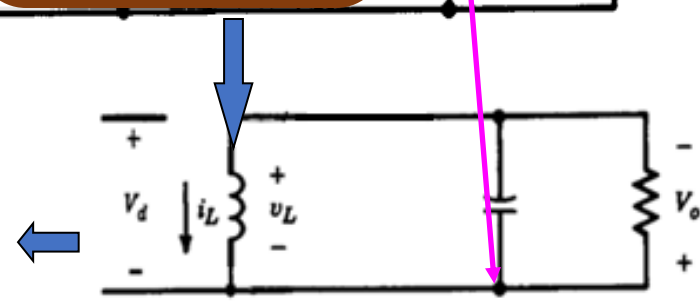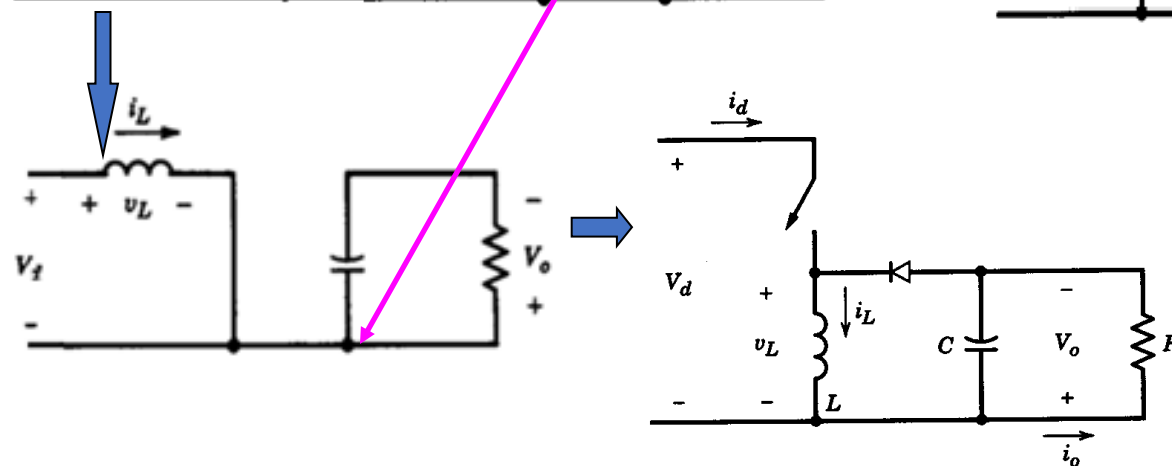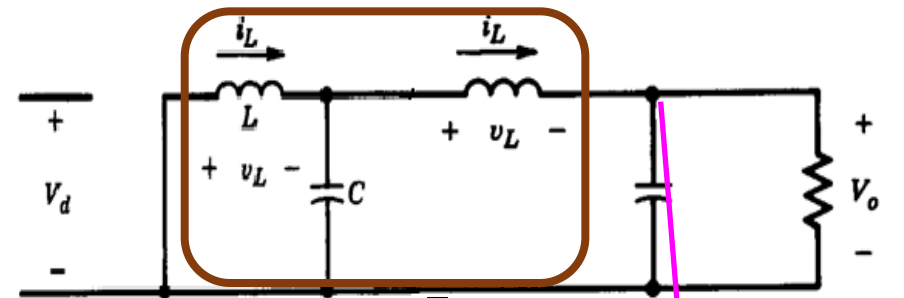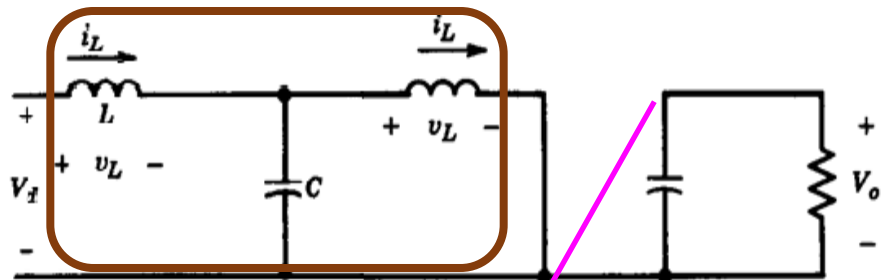

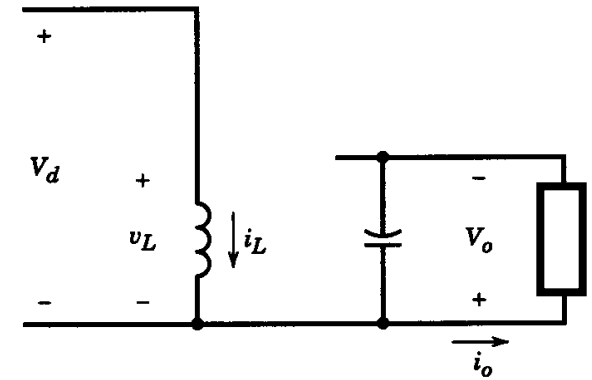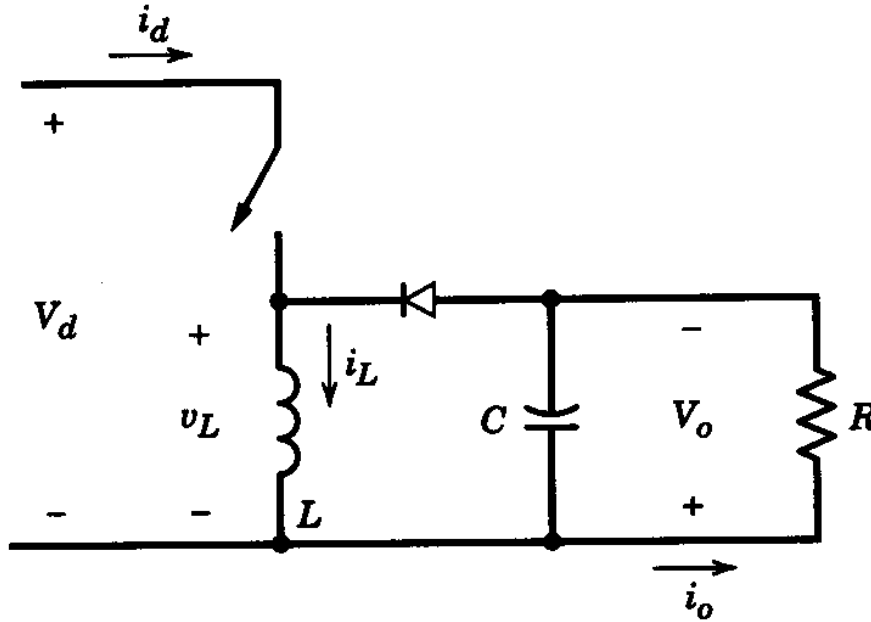

Mode 1 — on

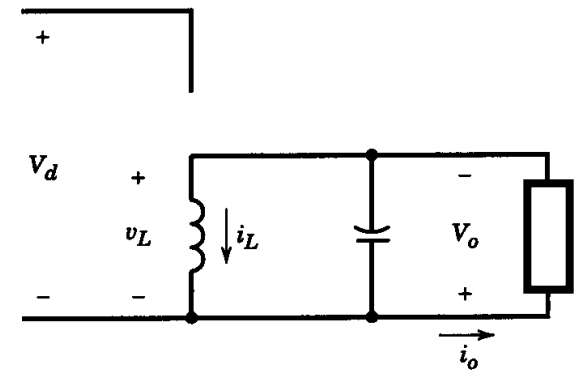

Mode 2 — off

5-3. Buck-Boost Regulators

Continuous-conduction

Assuming i_L rises linearly by ΔI_L in time t_{on}

Assuming i_L drops linearly by ΔI_L in time t_{off}

$$V_d = L \frac{\Delta I_L}{t_{on}}$$



$$V_o = L \frac{\Delta I_L}{t_{off}}$$

$$V_o = \frac{V_d D}{1-D}$$


$$V_d * I_d = V_o * I_o$$

$$I_d = \frac{I_o D}{1-D}$$

$$\Delta I_L = \frac{V_d D}{f_s L}$$

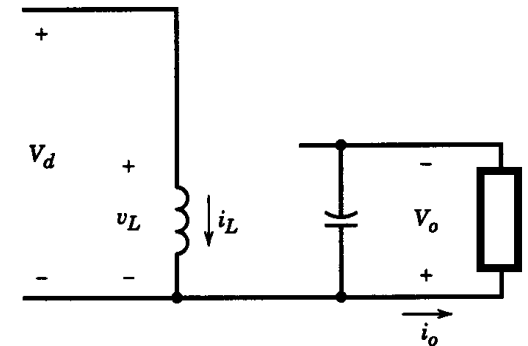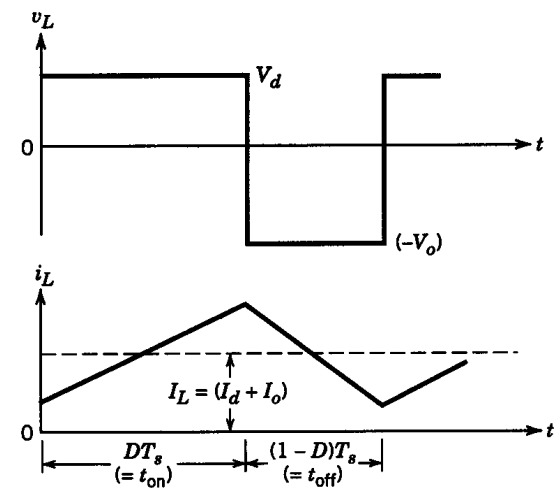


Mode 1 — on

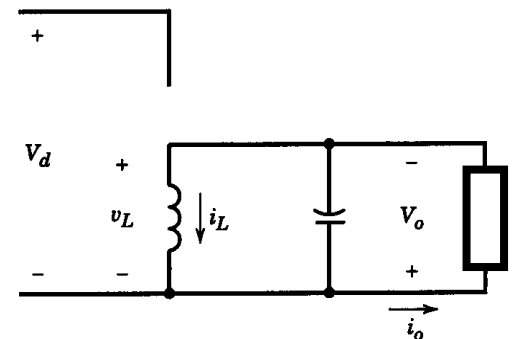


Mode 2 — off


Output Voltage Ripple

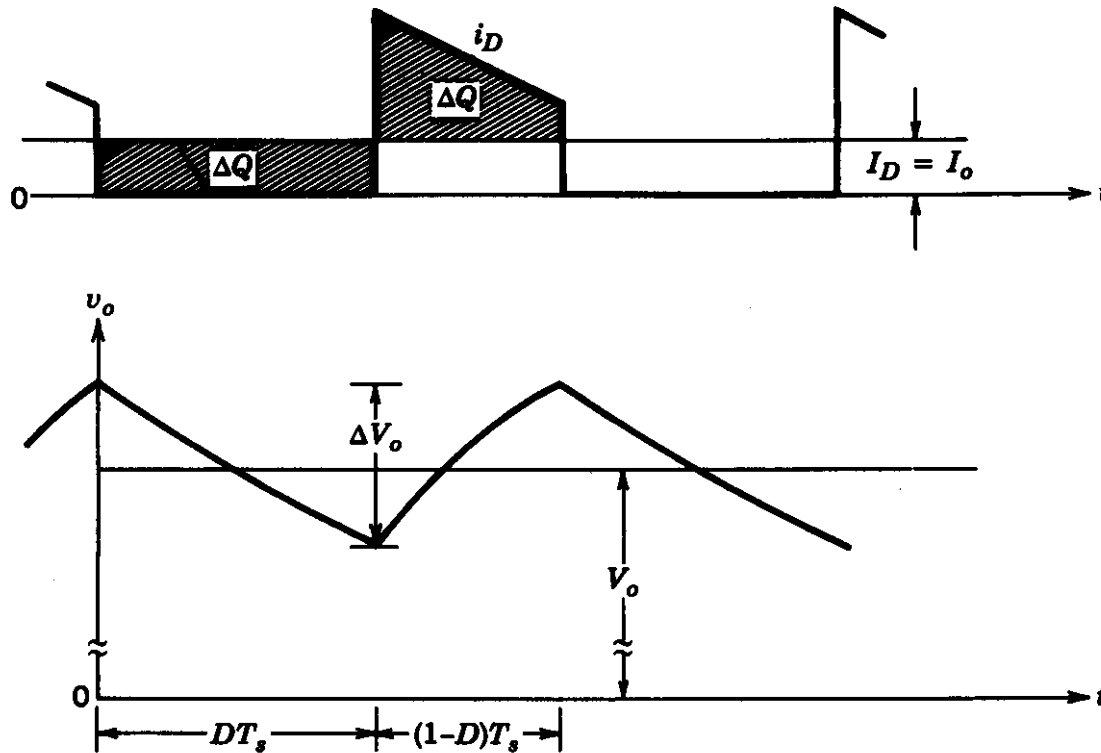

$$\Delta V_o = \frac{I_o D}{f_s C}$$

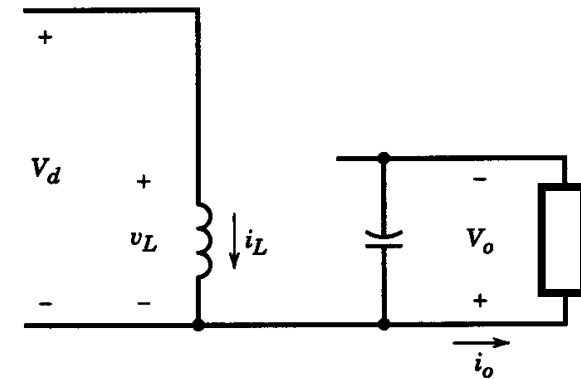


Mode 1 — on

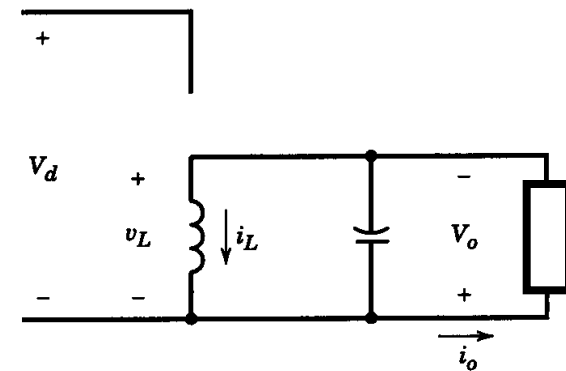

Mode 2 — off

Discontinuous-conduction

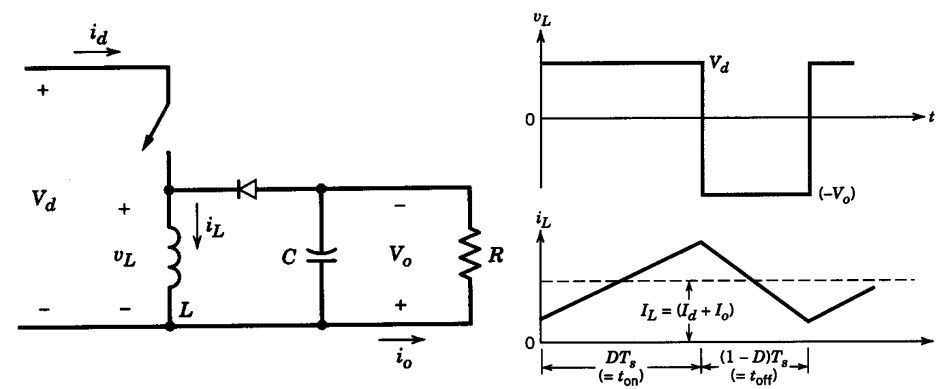
Boundary between continuous and discontinuous



$$I_{LB} = 0.5\Delta I_L$$

$$I_{oB} = I_{LB}(1-D)$$


$$\Delta I_L = \frac{V_d D}{f_s L}$$

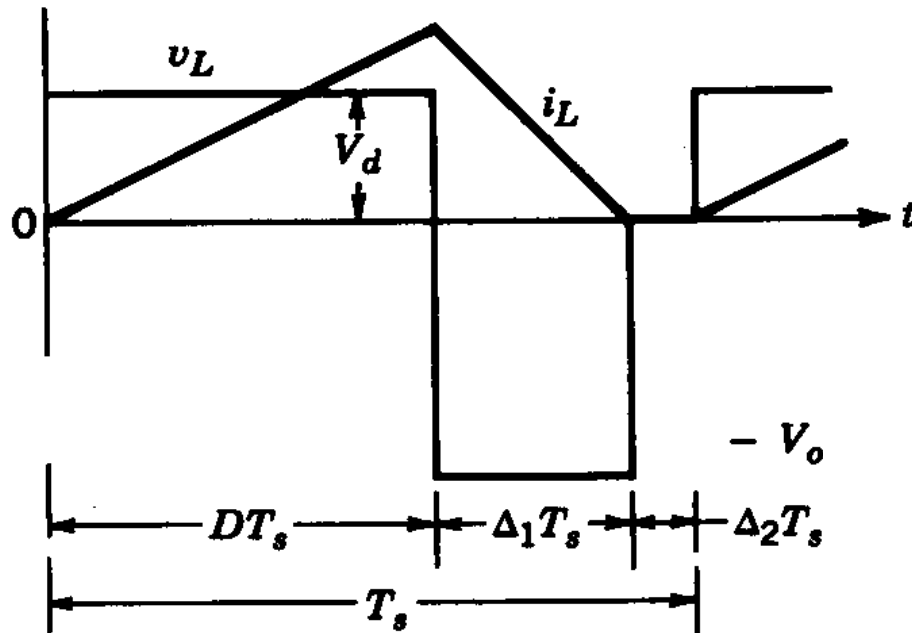

In steady state, the average inductor voltage must be zero.

$$\frac{V_o}{V_d} = \frac{D}{\Delta_1}$$


$$\Delta_1 = \frac{2f_s L}{V_d D} I_o$$

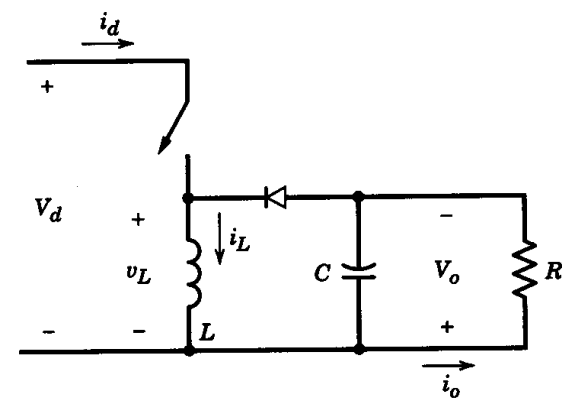

Characteristics of Buck-Boost circuits:





1. step-down or –up;
2. simple, requiring only one device;
3. high efficient;
4. polarity of output voltage reversed;
5. the input current discontinuous and a high peak current flowing through the device.

Supplement 4-2 Cuk: Cascade of Boost and Buck


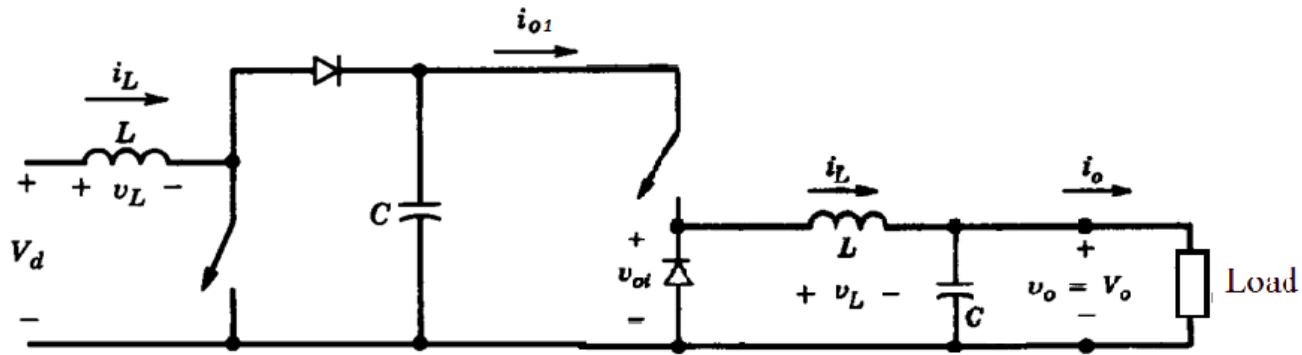


Mode 1 — on

Mode 2 — off

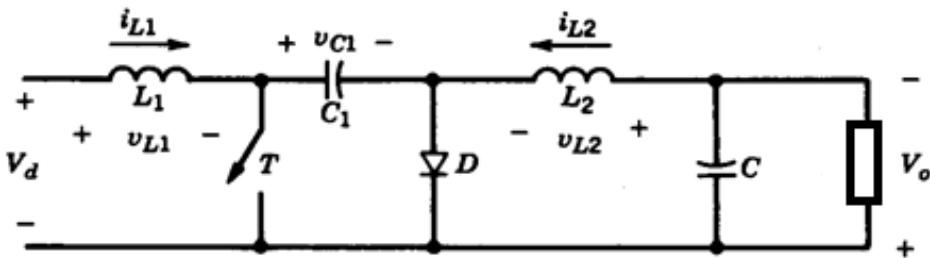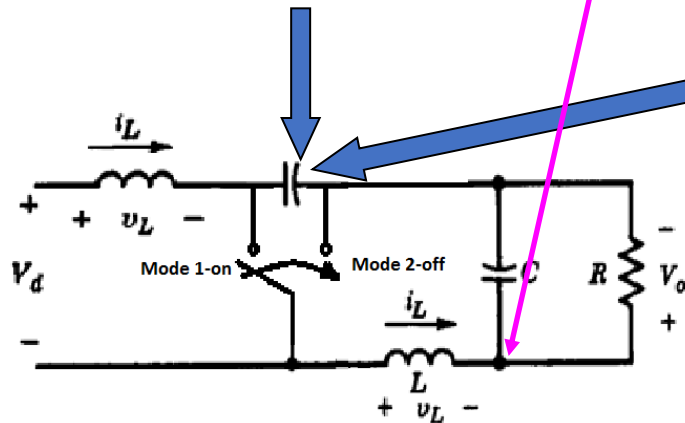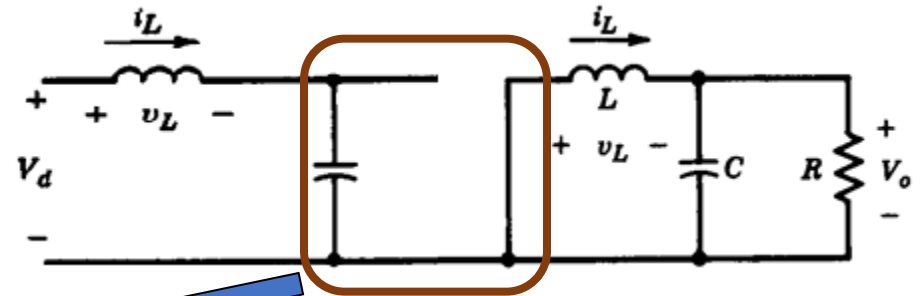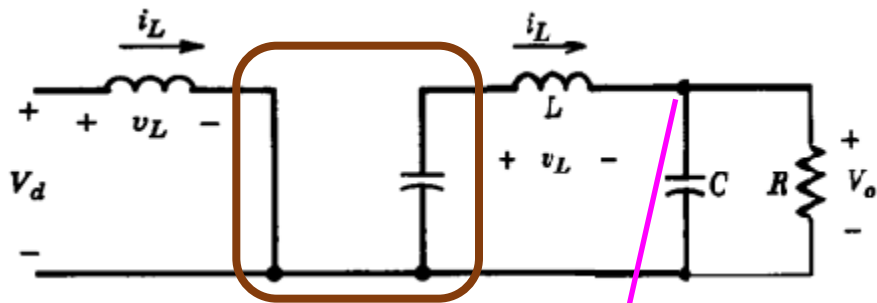

5-4. Cuk Regulators

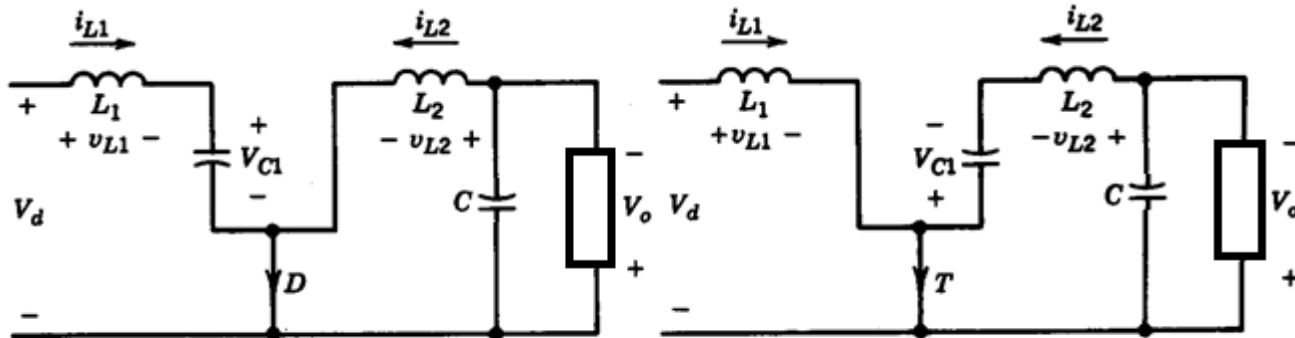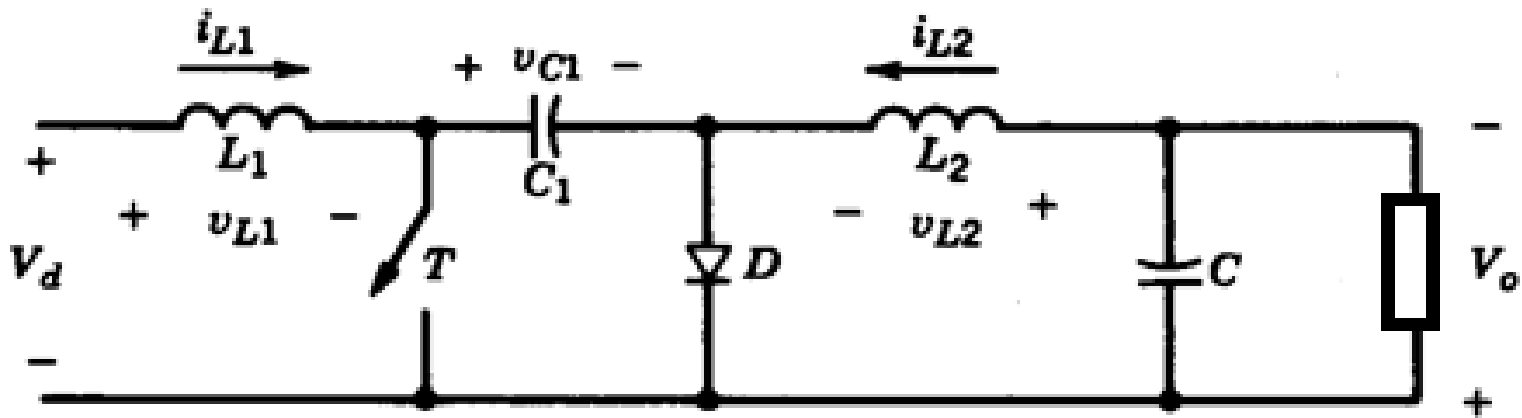

Mode 1 — off

Mode 2 — on

Continuous-conduction

$$V_d - V_{c1} = -L_1 \frac{\Delta I_{L1}}{t_{off}}$$

$$V_d = L_1 \frac{\Delta I_{L1}}{t_{on}}$$

$$V_o = L_2 \frac{\Delta I_{L2}}{t_{off}}$$

$$V_{c1} - V_o = L_2 \frac{\Delta I_{L2}}{t_{on}}$$

$$V_{c1} = \frac{V_d}{1-D}$$

$$V_{c1} = \frac{V_o}{D}$$

$$V_o = \frac{DV_d}{1-D}$$






$$I_d = \frac{DI_o}{1-D}$$

$$\Delta I_{L1} = \frac{DV_d}{f_s L_1}$$

$$\Delta I_{L2} = \frac{DV_d}{f_s L_2}$$


$$\Delta V_{c1} = \frac{I_d(1-D)}{f_s C_1}$$
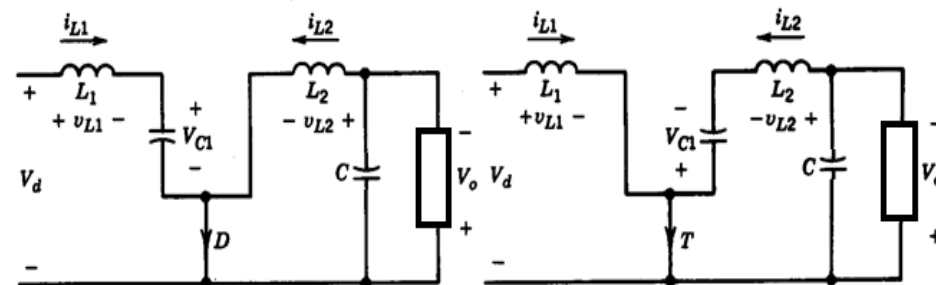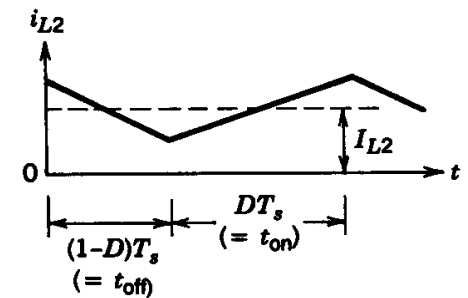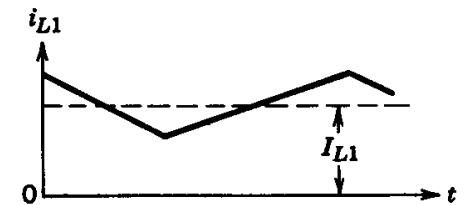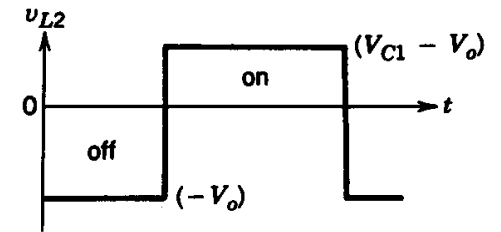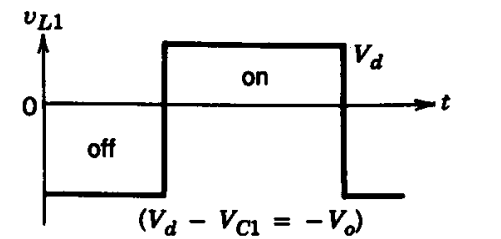
$$\Delta V_{c2} = \frac{DV_d}{8C_2 L_2 f_s^2}$$



Model 1 off

Model 2 on

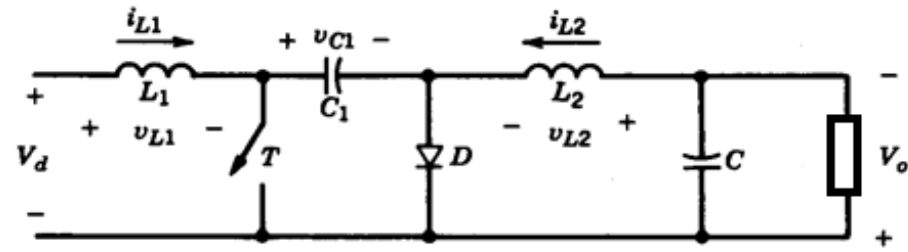

Characteristics of Cuk circuits:

1. step-down or –up;
2. requiring only one device;
3. high efficient;
4. input current continuous;
5. ripple current of C_1 high;
6. additional capacitor and inductor.

Summary:

- Buck (step-down), Boost (step-up), Buck-Boost (step-up & -down), Cuk (Boost-Buck, step-up & -down)
- Topologies of these DC choppers and circuits in different modes
- Key waveforms and calculations based on two rules


DC components of input/output voltage/current

DC components of capacitor voltage and inductor current

Ripples of capacitor voltage and inductor current



- Design of DC choppers
- Difference between continuous- and discontinuous-conduction

5-5. Full-bridge Regulators

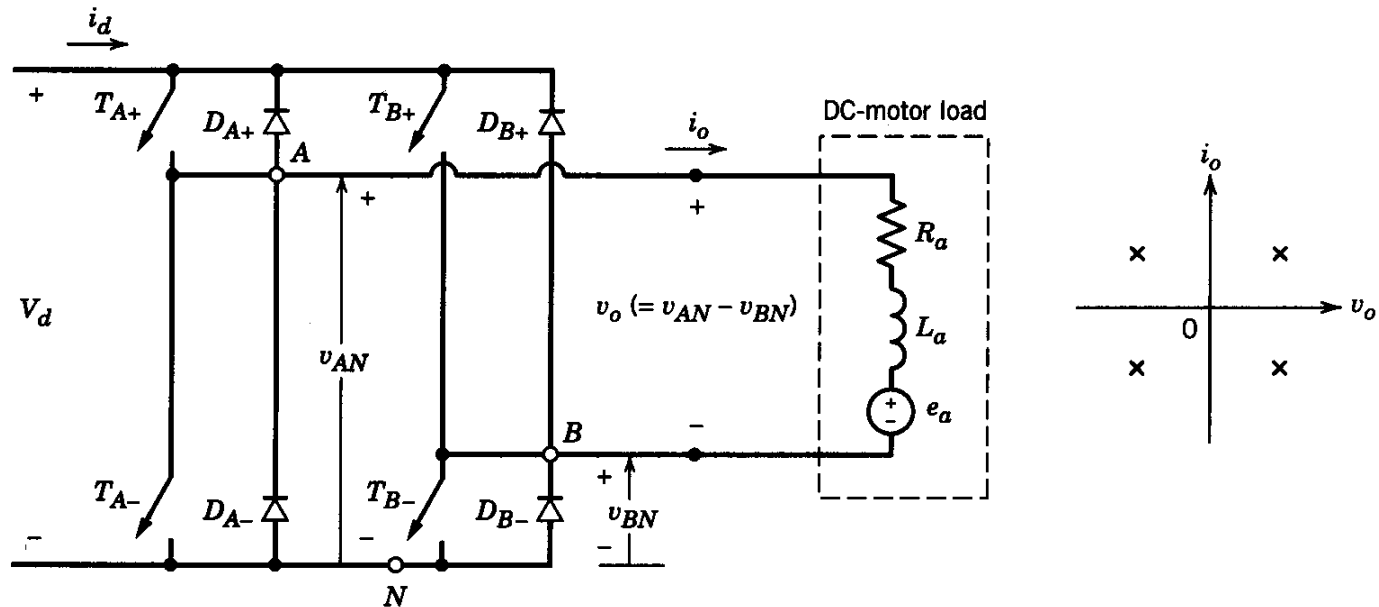

Four quadrant operation is possible.

PWM with Bipolar Voltage Switching

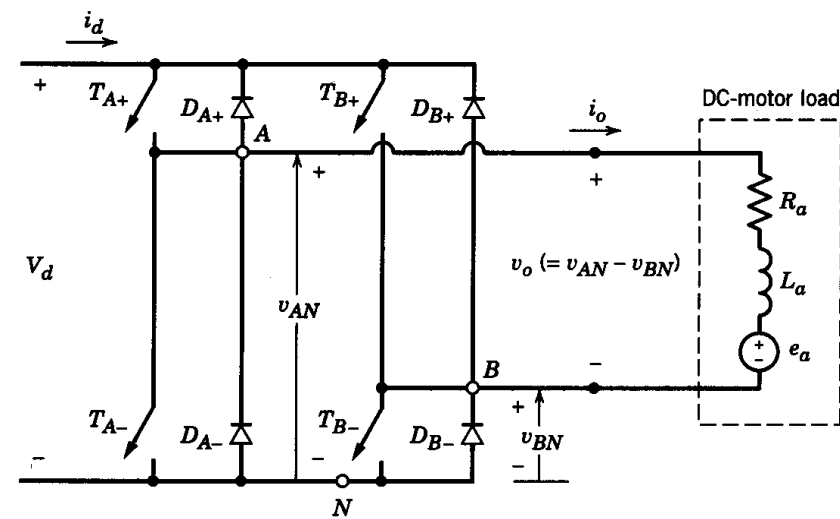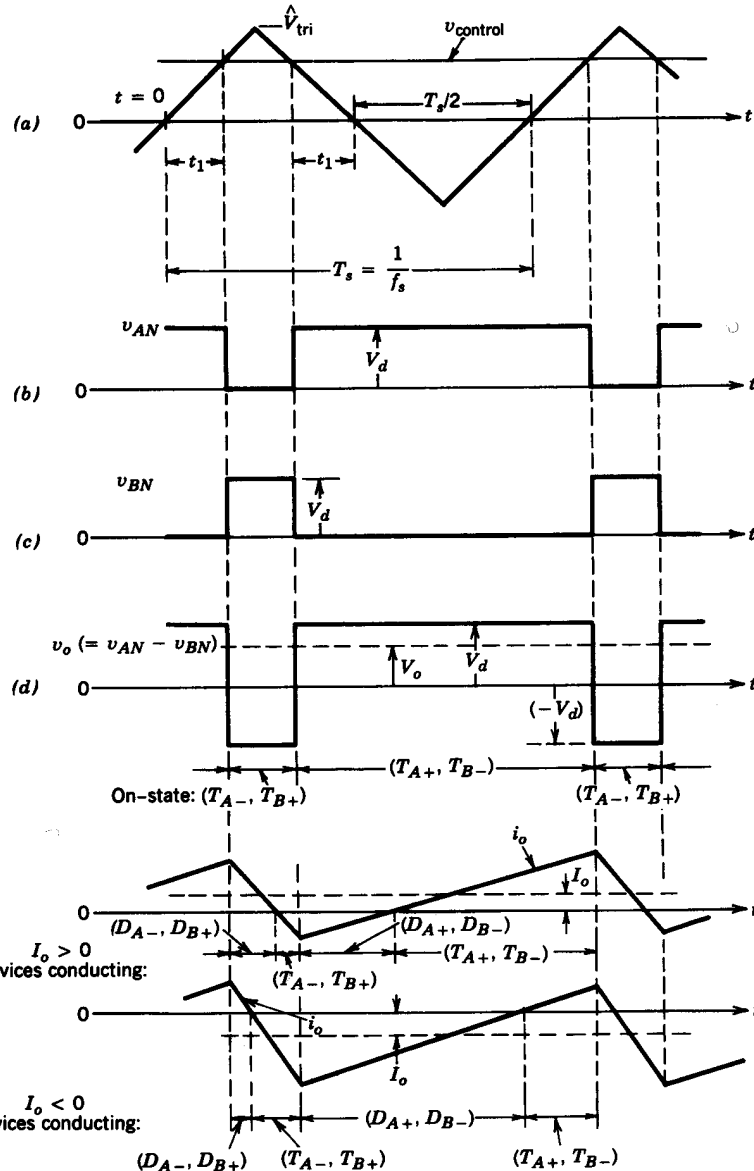

$$v_{control} > v_{tri}$$

$$T_{A+}, T_{B-} \text{ on: } v_{AN} = V_d, v_{BN} = 0;$$

$$(T_{A-}, T_{B+} \text{ off})$$

$$v_o = V_d$$

$$i_o > 0 \quad T_{A+}, T_{B-} \text{ conduct; } i_d = i_o$$

$$i_o < 0 \quad D_{A+}, D_{B-} \text{ conduct; } i_d = i_o$$

$$v_{control} < v_{tri}$$

$$T_{A-}, T_{B+} \text{ on: } v_{AN} = 0, v_{BN} = V_d;$$



$$(T_{A+}, T_{B-} \text{ off})$$

$$v_o = -V_d$$

$$i_o < 0 \quad T_{A-}, T_{B+} \text{ conduct; } i_d = -i_o$$

$$i_o > 0 \quad D_{A-}, D_{B+} \text{ conduct; } i_d = -i_o$$

PWM with Unipolar Voltage Switching

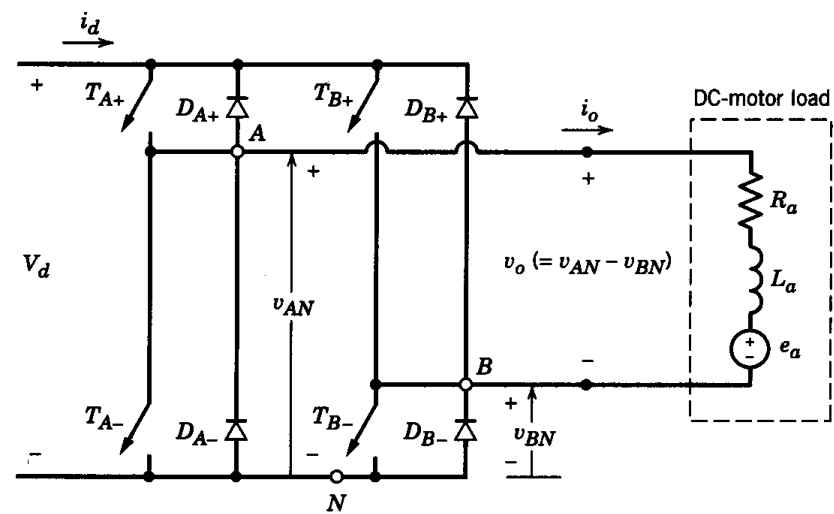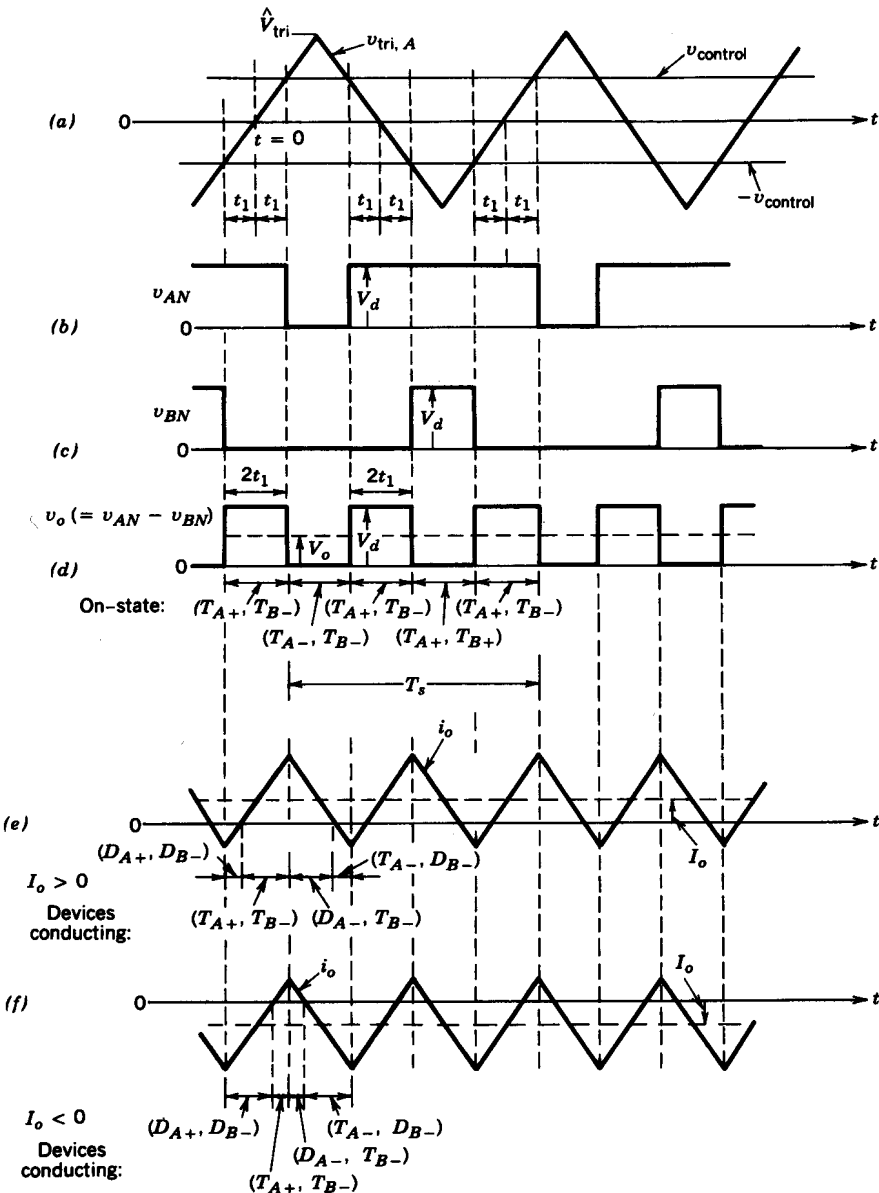

Leg A:

$v_{control} > v_{tri}$ T_{A+} on (T_{A-} off) $v_{AN} = V_d$;

$v_{control} < v_{tri}$ T_{A-} on (T_{A+} off) $v_{AN} = 0$;

Leg B:



$-v_{control} > v_{tri}$ T_{B+} on (T_{B-} off) $v_{BN} = V_d$;

$-v_{control} < v_{tri}$ T_{B-} on (T_{B+} off) $v_{BN} = 0$;

$$v_o = v_{AN} - v_{BN}$$

“effectively” doubling f_s

PWM with Unipolar Voltage Switching

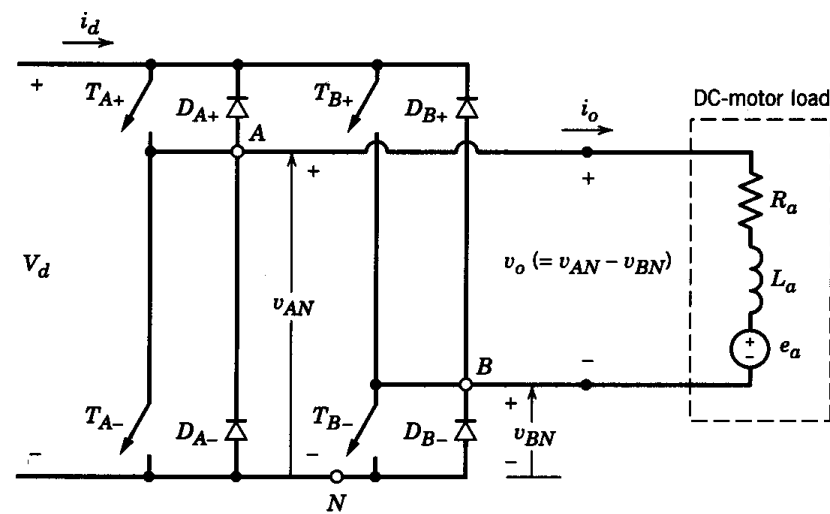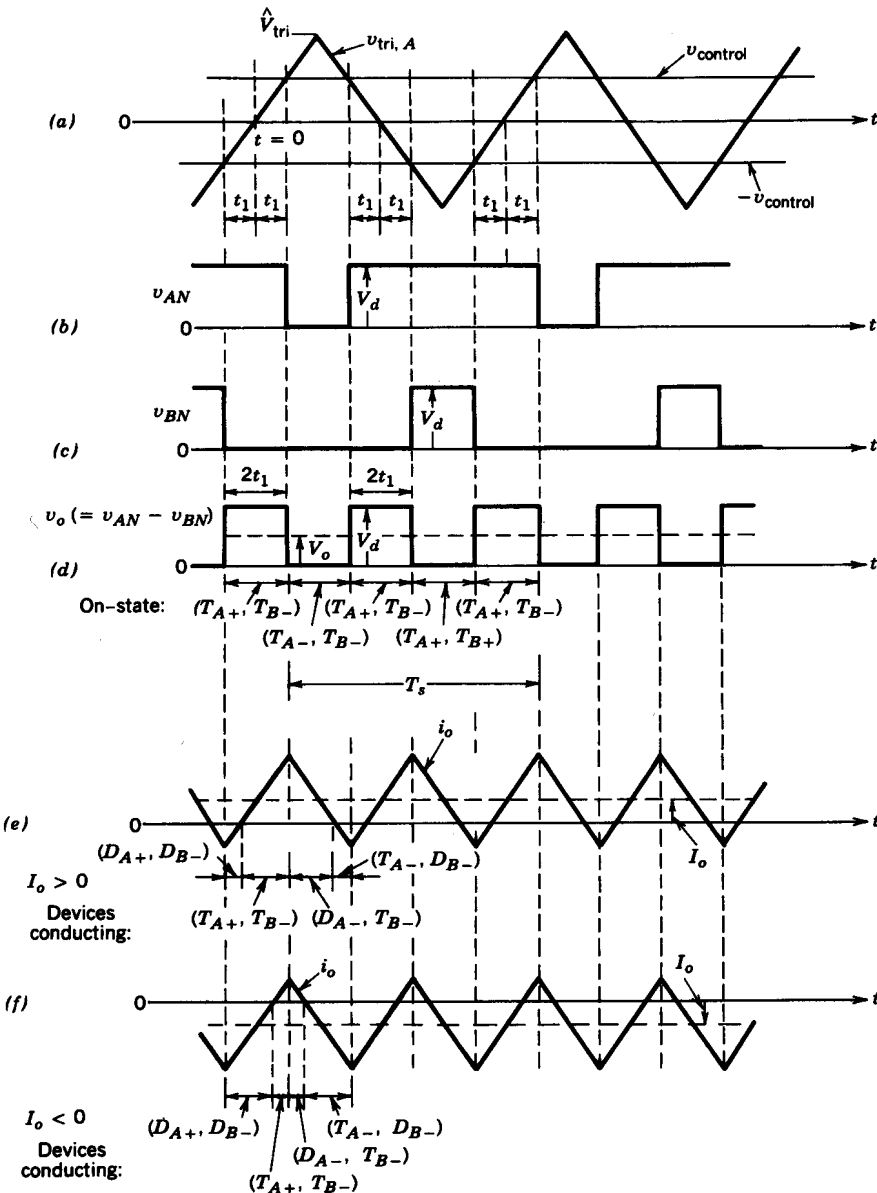

Leg A:

T_{A+} on $i_o > 0$ T_{A+} conducts; $i_{d1} = i_o$
 $i_o < 0$ D_{A+} conducts; $i_{d1} = i_o$
 T_{A-} on $i_o < 0$ T_{A-} conducts; $i_{d1} = -i_o$
 $i_o > 0$ D_{A-} conducts; $i_{d1} = -i_o$


Leg B:

T_{B+} on $i_o < 0$ T_{B+} conducts; $i_{d2} = -i_o$
 $i_o > 0$ D_{B+} conducts; $i_{d2} = -i_o$
 T_{B-} on $i_o > 0$ T_{B-} conducts; $i_{d2} = i_o$
 $i_o < 0$ D_{B-} conducts; $i_{d2} = i_o$

$$i_d = i_{d1} + i_{d2}$$

Output Ripple of Full-bridge Regulators

using PWM with (a) bipolar and (b) unipolar voltage switching

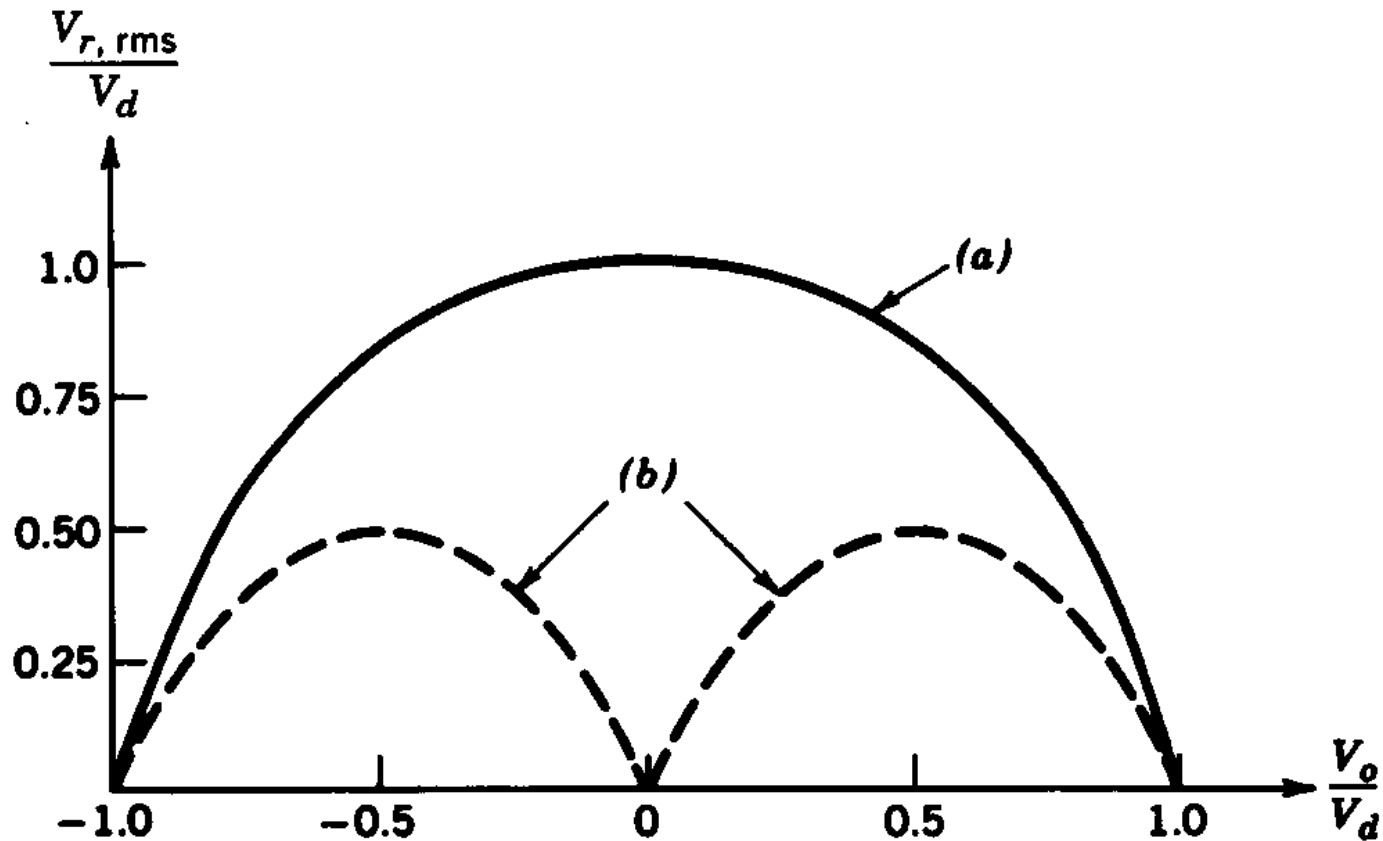

Supplement 4-3 Simulation of the Cuk by Matlab




The working procedure of the Cuk regulators can be represented by two modes:

• Mode 1

$$\begin{cases} \frac{di_{L_1}}{dt} = \frac{V_s}{L_1} \\ \frac{di_{L_2}}{dt} = \frac{1}{L_2}(v_{c1} - v_{c2}) \\ \frac{dv_{c1}}{dt} = -\frac{i_{L_2}}{C_1} \\ \frac{dv_{c2}}{dt} = \frac{1}{C_2}\left(\frac{v_{c2}}{R} - i_{L_2}\right) \end{cases}$$

• Mode 2
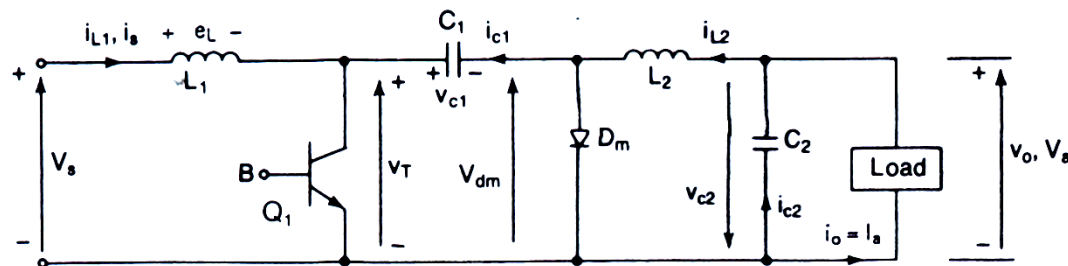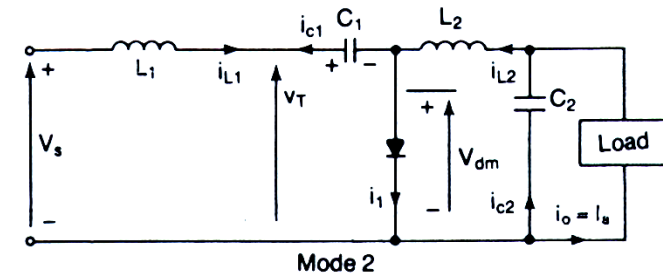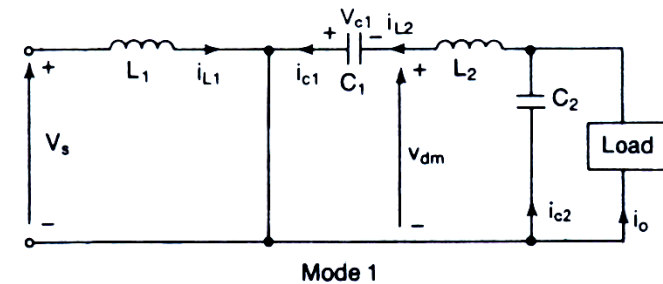
$$\begin{cases} \frac{di_{L_1}}{dt} = \frac{1}{L_1}(V_s - v_{c1}) \\ \frac{di_{L_2}}{dt} = \frac{v_{c2}}{L_2} \\ \frac{dv_{c1}}{dt} = \frac{i_{L_1}}{C_1} \\ \frac{dv_{c2}}{dt} = \frac{1}{C_2}\left(\frac{v_{c2}}{R} - i_{L_2}\right) \end{cases}$$



The load is assumed as a pure resistor R .

Simulation Parameters:





$V_s=5\text{V}$, $C_1=C_2=100\mu\text{F}$, $L_1=L_2=0.5\text{mH}$;

$R_{\text{load}}=5\Omega$;





$f_s=10\text{kHz}$, $D=0.8$.

*The functions used to solve the
state equations in Matlab:*





ode23, ode45

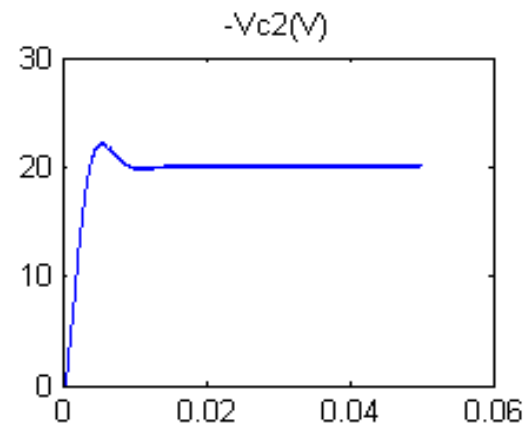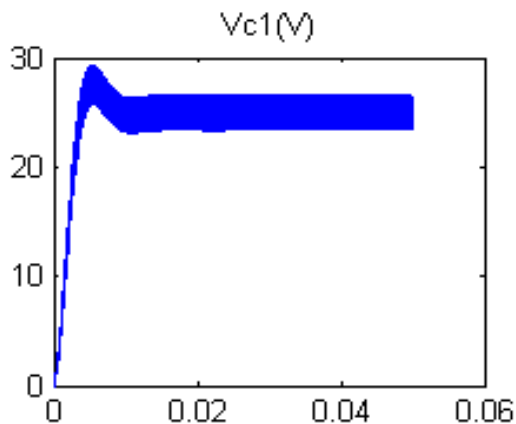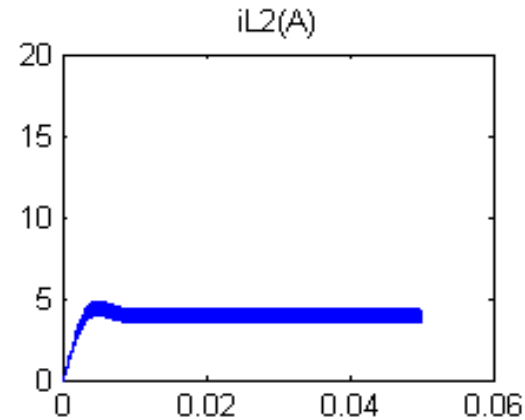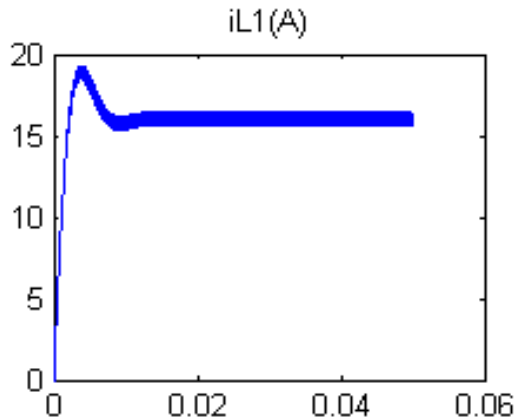

The first five cycles

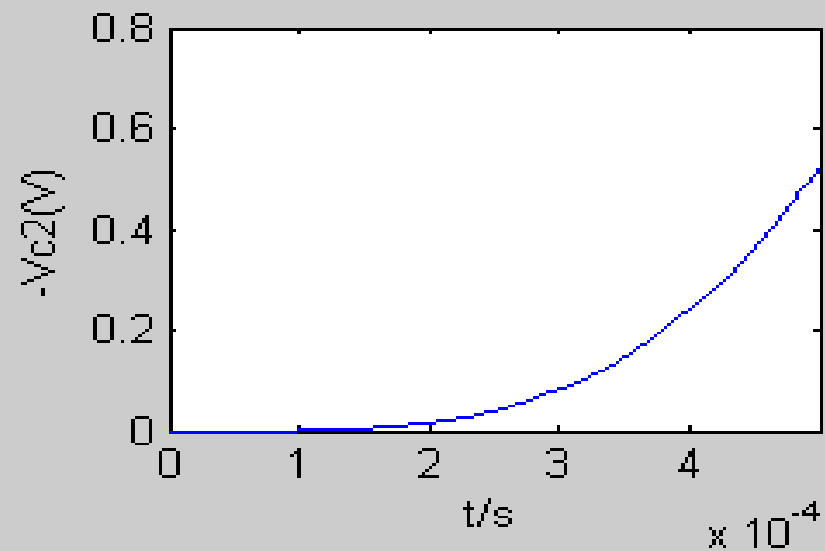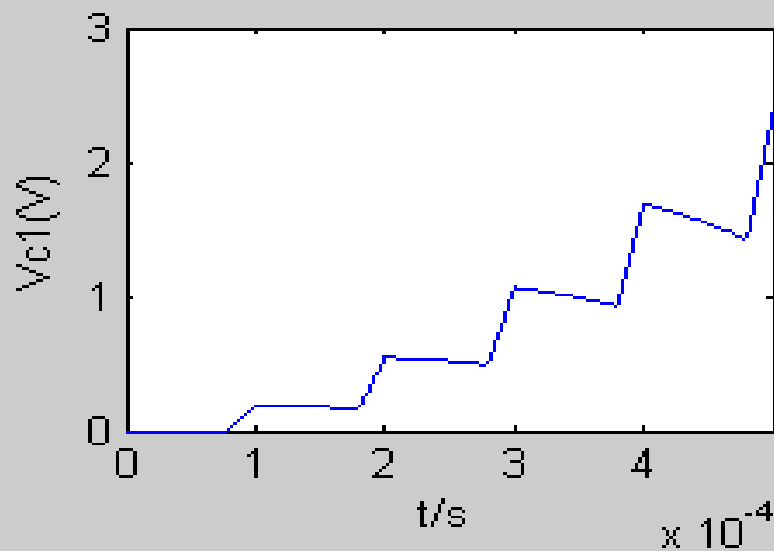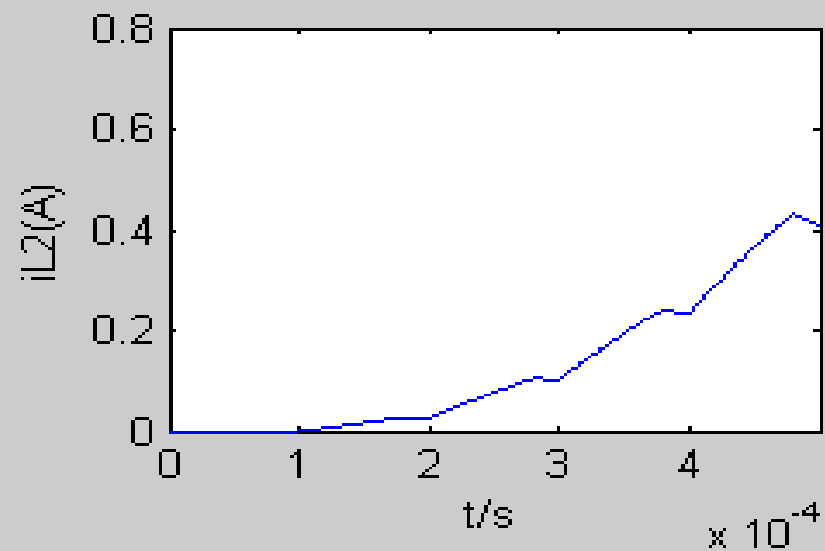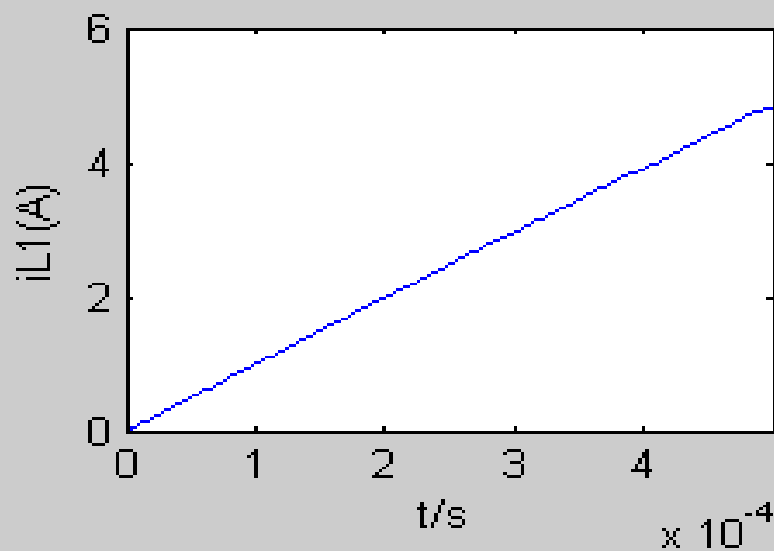

Five cycles in steady state

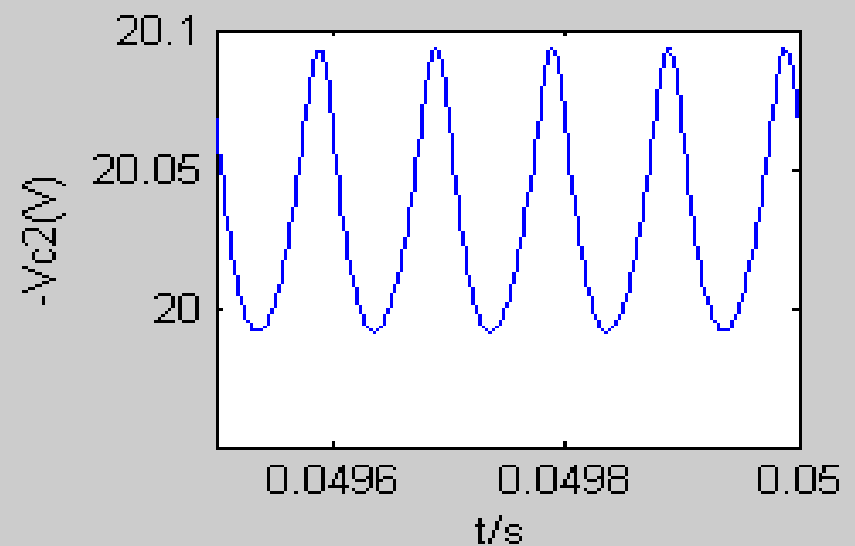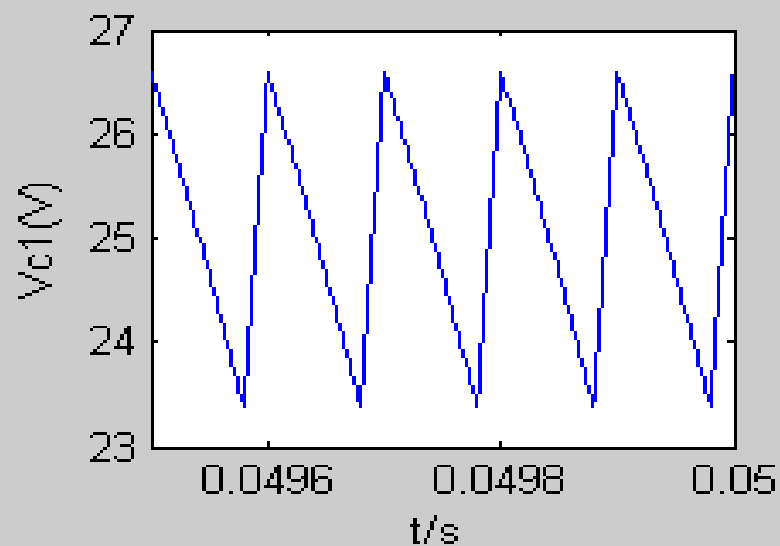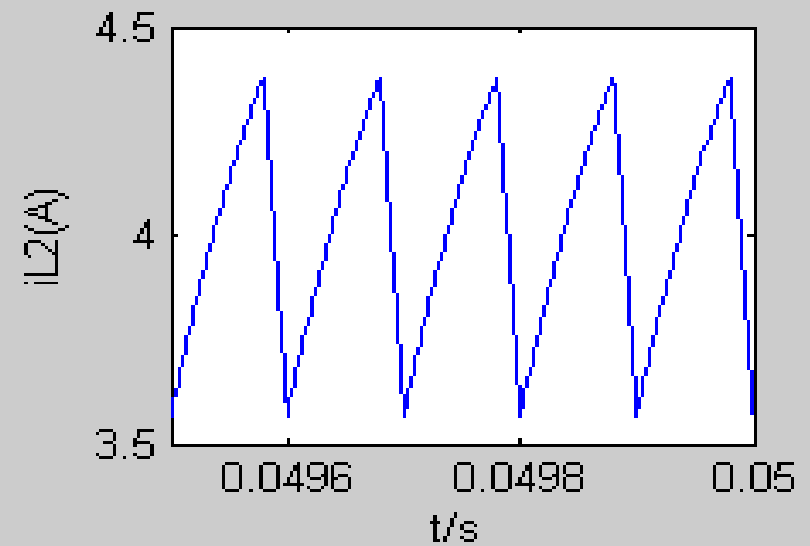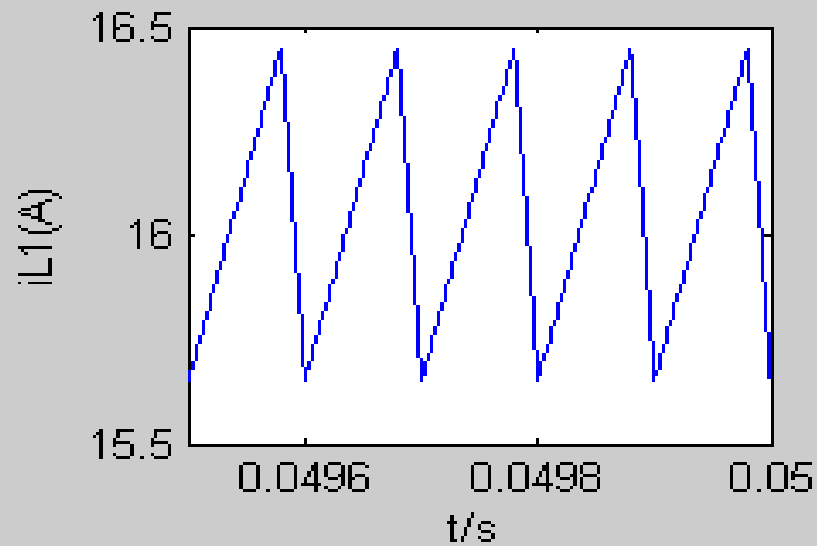

The End

