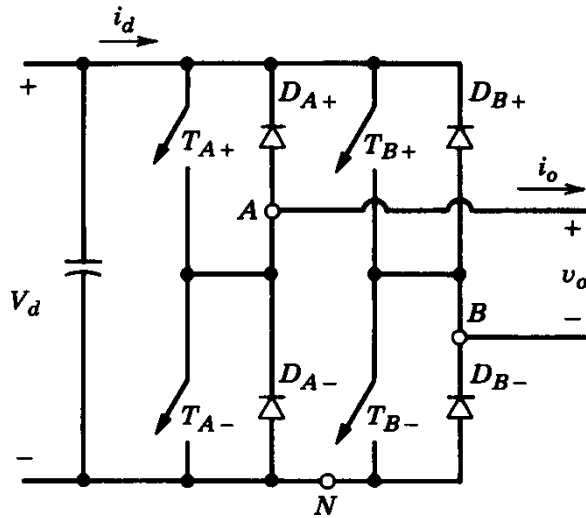


Chapter 6

DC-AC Inverters

6-1. Single-phase Bridge Inverters



a **blanking time** of a few μs after turn-off of **one switch** in a leg before **the other** in the same leg are turned on, otherwise a risk of re-conduction in the outgoing switch, giving a short-circuit.

Four combinations of switch states and the corresponding voltage levels:

1. T_{A+} , T_{B-} on: $v_{AN} = V_d$, $v_{BN} = 0$;
(T_{A-} , T_{B+} off) $v_o = V_d$
2. T_{A-} , T_{B+} on: $v_{AN} = 0$, $v_{BN} = V_d$;
(T_{A+} , T_{B-} off) $v_o = -V_d$
3. T_{A+} , T_{B+} on: $v_{AN} = V_d$, $v_{BN} = V_d$;
(T_{A-} , T_{B-} off) $v_o = 0$
4. T_{A-} , T_{B-} on: $v_{AN} = 0$, $v_{BN} = 0$;
(T_{A+} , T_{B+} off) $v_o = 0$

PWM with Bipolar Voltage Switching

DC-AC Inverters

Only one reference v_{control} is used for TA and TB signals (two switch states)

1. T_{A+}, T_{B-} on: $v_{AN} = V_d, v_{BN} = 0$;
 $(T_{A-}, T_{B+}$ off) $v_o = V_d$
2. T_{A-}, T_{B+} on: $v_{AN} = 0, v_{BN} = V_d$;
 $(T_{A+}, T_{B-}$ off) $v_o = -V_d$

amplitude modulation ratio:

$$m_a = V_{\text{control(peak)}} / V_{\text{tri(peak)}}$$

frequency modulation ratio:

$$m_f = f_s / f_1$$




a. synchronous PWM

— no subharmonics;



b. m_f an odd integer

— no even harmonics;

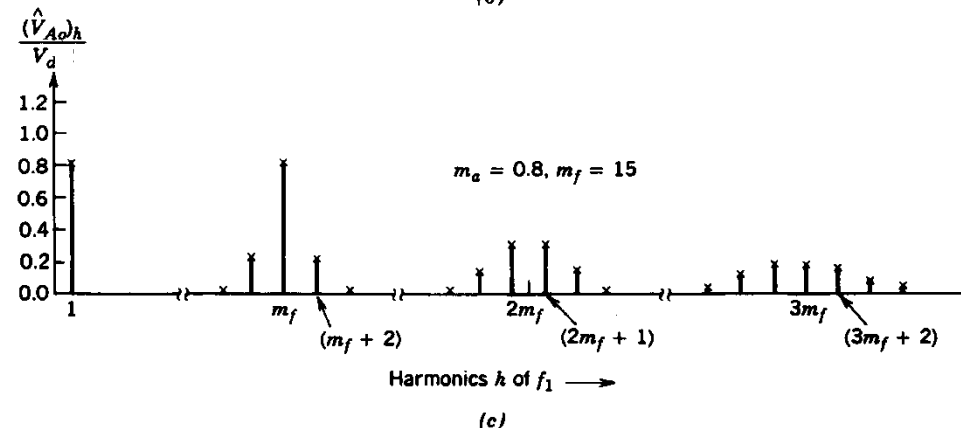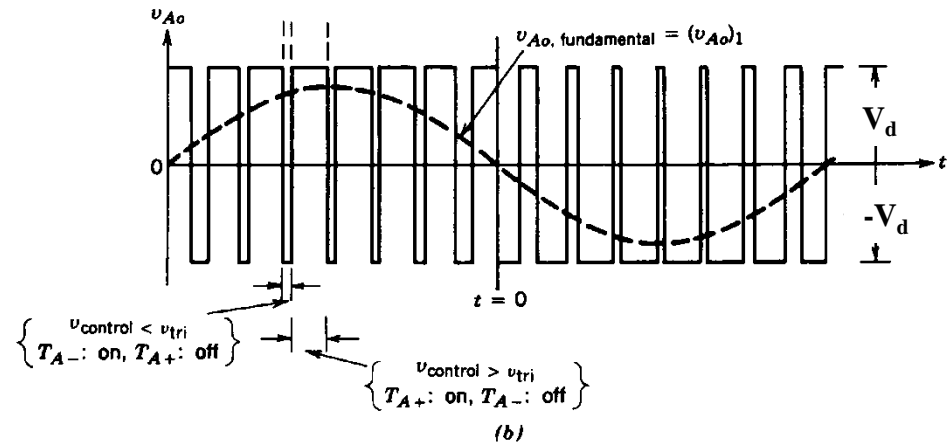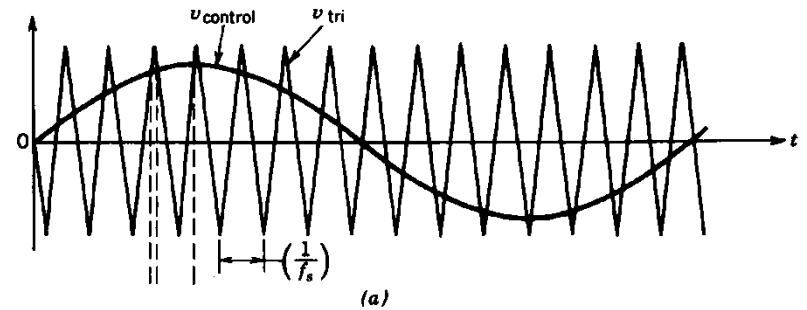
c. harmonics appearing as sidebands centered around m_f and its multiples.



PWM with Bipolar Voltage Switching

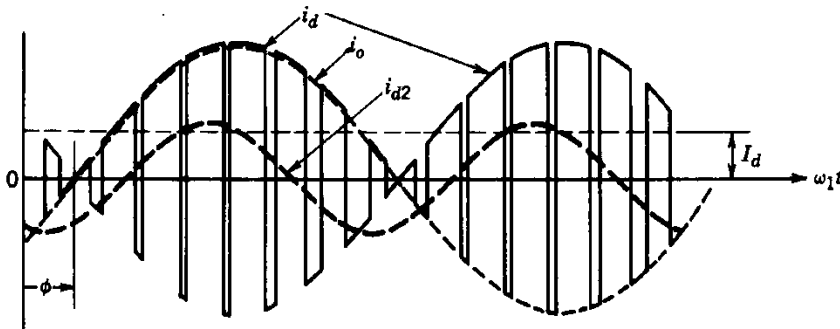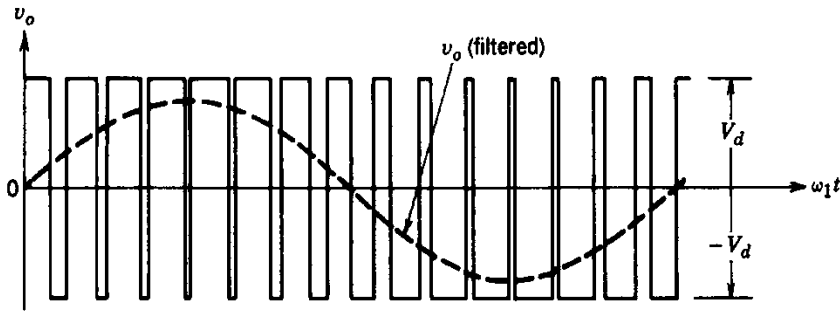

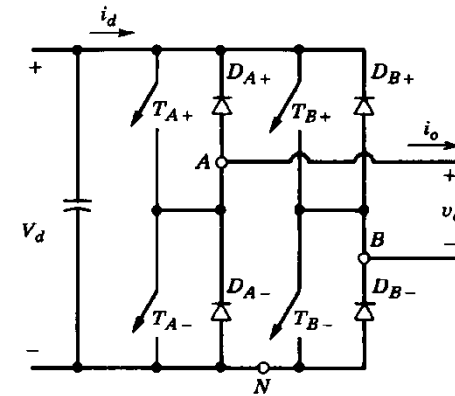i_d consists of I_d , i_{d2} and the high-frequency components due to inverter switchings.



1. T_{A+}, T_{B-} on: $v_{AN} = V_d, v_{BN} = 0$;
(T_{A-}, T_{B+} off) $v_o = V_d$

$$i_o > 0 \quad T_{A+}, T_{B-} \text{ conduct; } i_d = i_o$$

$$i_o < 0 \quad D_{A+}, D_{B-} \text{ conduct; } i_d = i_o$$

2. T_{A-}, T_{B+} on: $v_{AN} = 0, v_{BN} = V_d$;
(T_{A+}, T_{B-} off) $v_o = -V_d$

$$i_o < 0 \quad T_{A-}, T_{B+} \text{ conduct; } i_d = -i_o$$

$$i_o > 0 \quad D_{A-}, D_{B+} \text{ conduct; } i_d = -i_o$$

PWM with Bipolar Voltage Switching

Linear

$$V_{o1max} = m_a V_d$$

$$m_a \leq 1$$


Over-modulation

$$V_d < V_{o1max} < 4/\pi V_d$$

$$m_a > 1$$


Square-wave operation

$$V_{o1max} = 4/\pi V_d$$

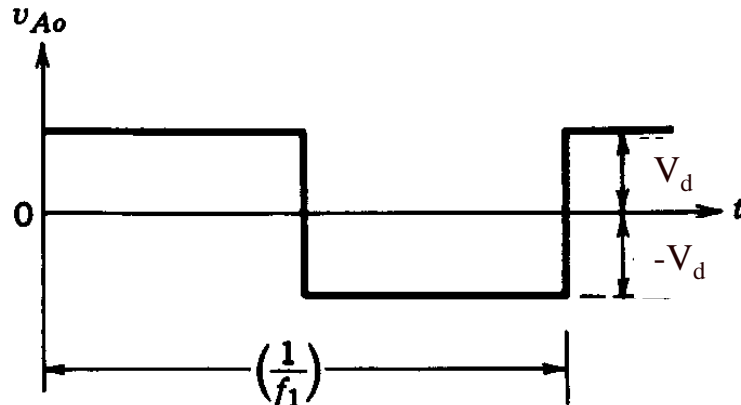



Square-Wave Mode of Operation

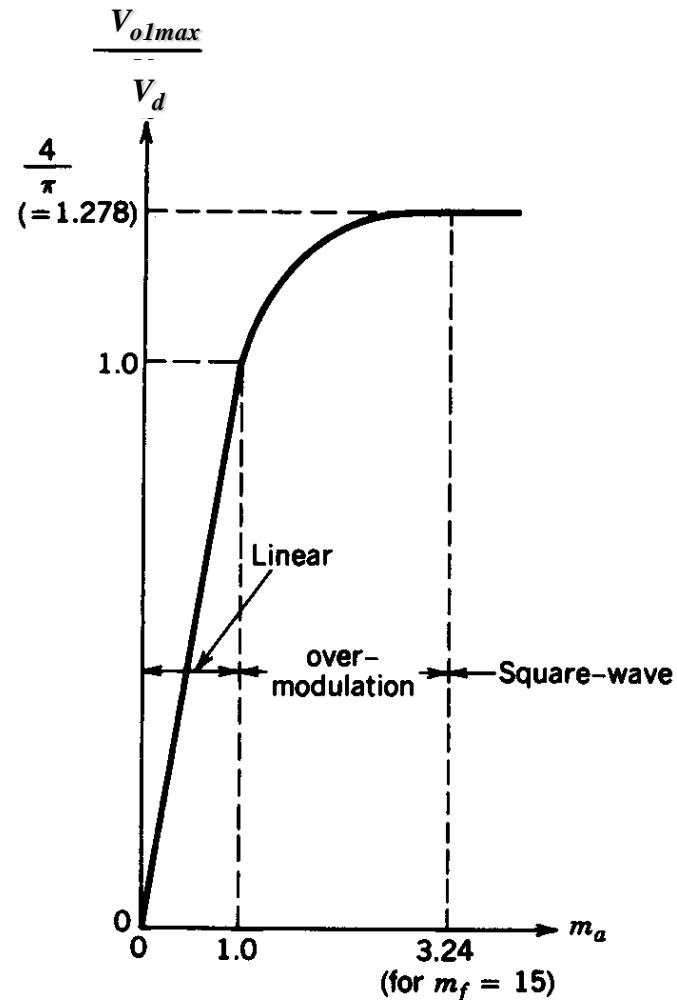Output voltage Fundamental
as a Function of m_a




PWM with Bipolar Voltage Switching


DC-AC Inverters

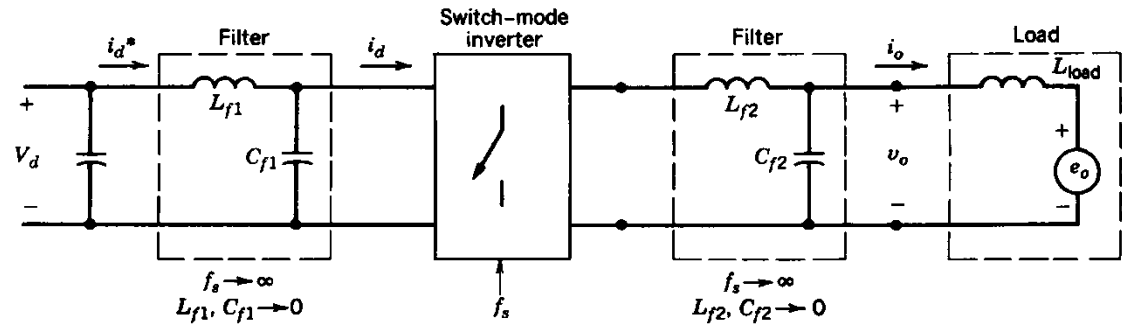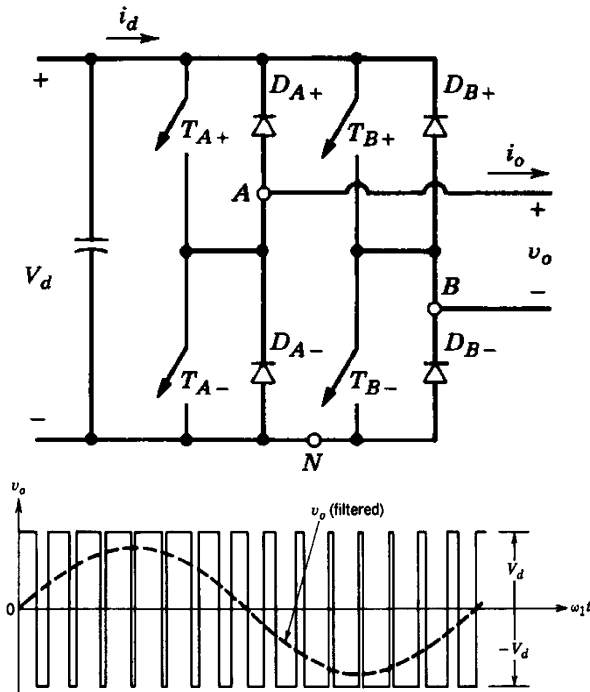

$$0 < \theta < 90$$

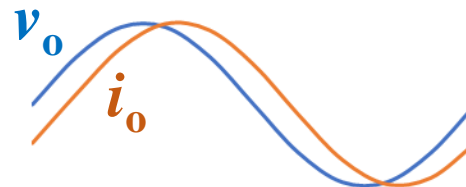



$$90 < \theta < 180$$

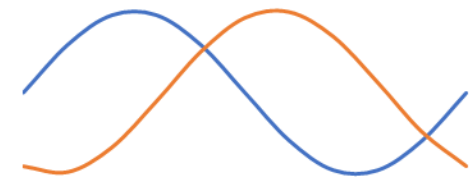

$$180 < \theta < 270$$



$$270 < \theta < 360$$

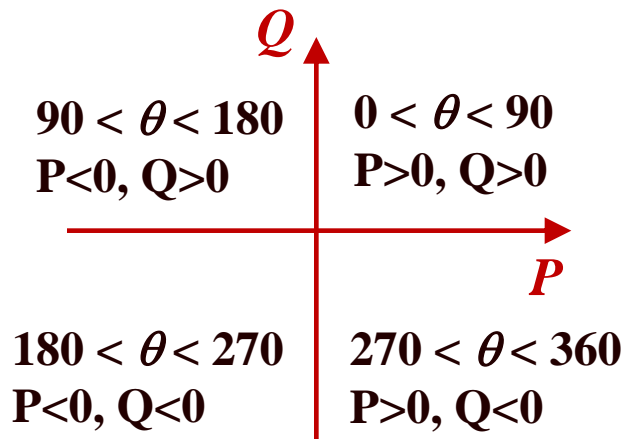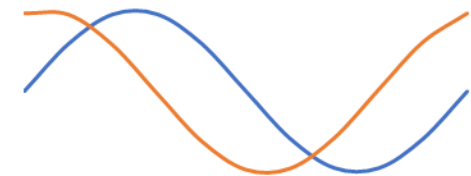

Four-quadrant operation

Single-Phase Inverter


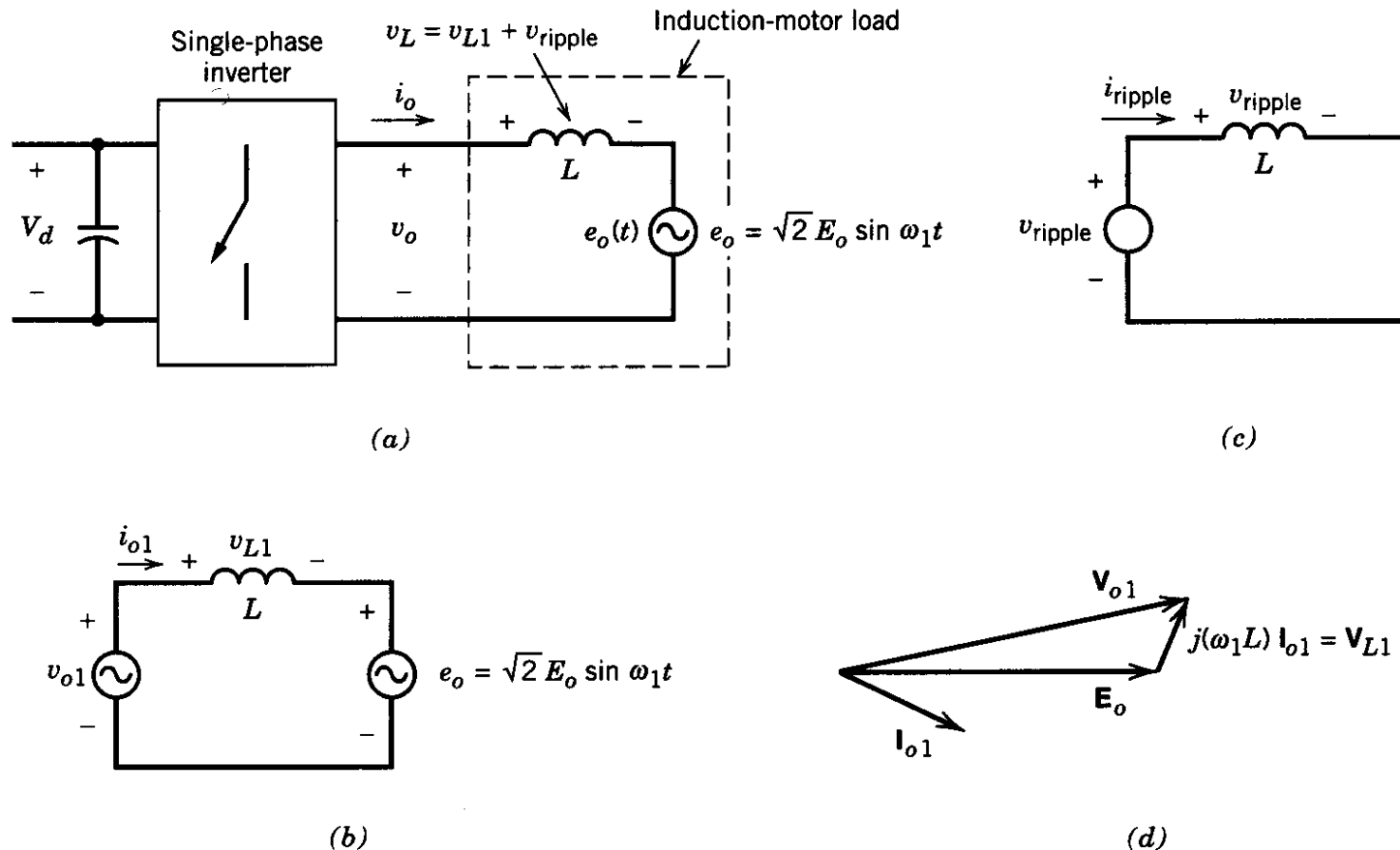


Figure 8-18 Single-phase inverter: (a) circuit; (b) fundamental-frequency components; (c) ripple frequency components; (d) fundamental-frequency phasor diagram.


DC power source – DC-AC Inverters – an AC load

DC Voltage converted to Sinusoidal AC Voltage

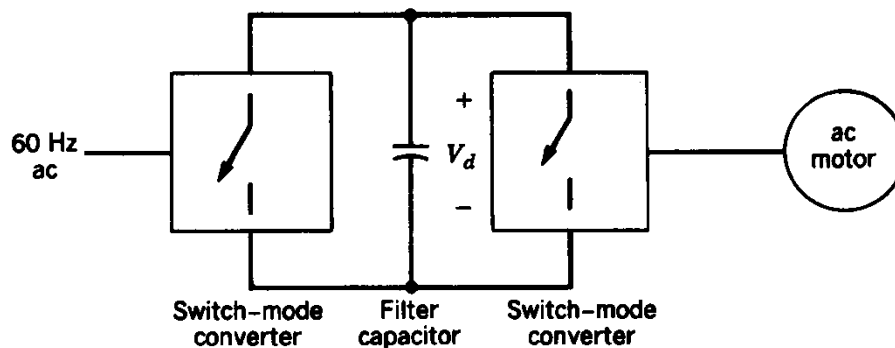- * Switch-mode using fast switching devices, anti diode (GTO, IGBT, power MOSFET, etc.)
- * Constant DC voltage source in DC side
- * both output amplitude and frequency variable
- * applications: AC motor drives and grid inverter



power flow bi-directional ac motor

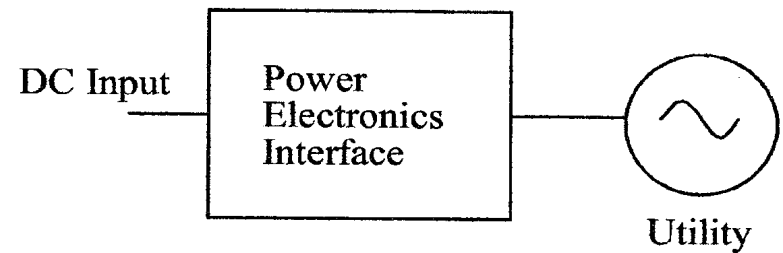

Photovoltaic Systems

PWM with Unipolar Voltage Switching

DC-AC Inverters

Leg A:

$$v_{control} > v_{tri} \quad T_{A+} \text{ on} \quad v_{AN} = V_d;$$

$$(T_{A-} \text{ off})$$

$$v_{control} < v_{tri} \quad T_{A-} \text{ on} \quad v_{AN} = 0;$$

$$(T_{A+} \text{ off})$$

Leg B:

$$-v_{control} > v_{tri} \quad T_{B+} \text{ on} \quad v_{BN} = V_d;$$

$$(T_{B-} \text{ off})$$






$$-v_{control} < v_{tri} \quad T_{B-} \text{ on} \quad v_{BN} = 0;$$

$$(T_{B+} \text{ off})$$


$$v_o = v_{AN} - v_{BN}$$

a. “effectively” doubling f_s

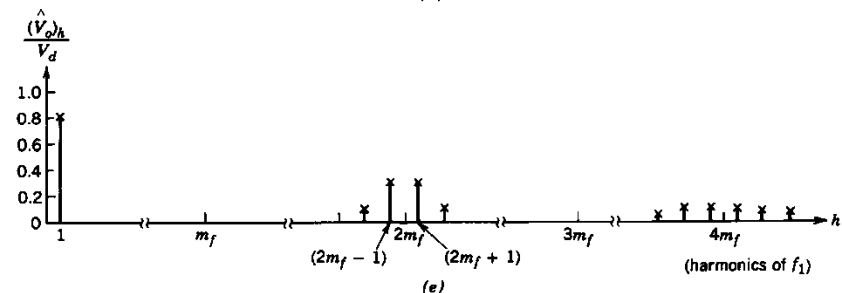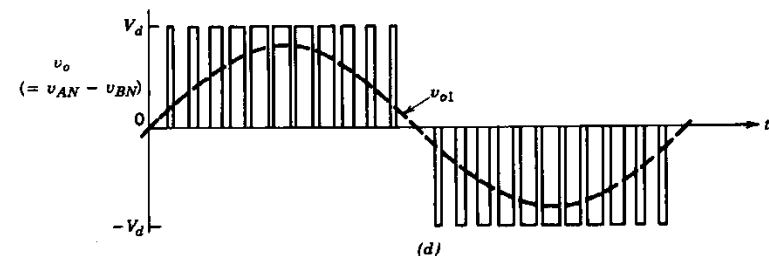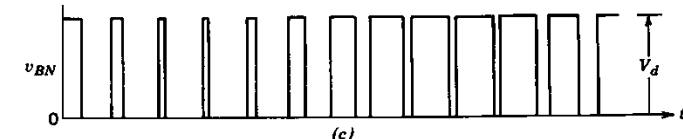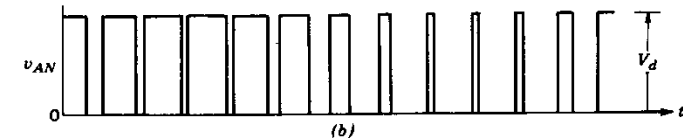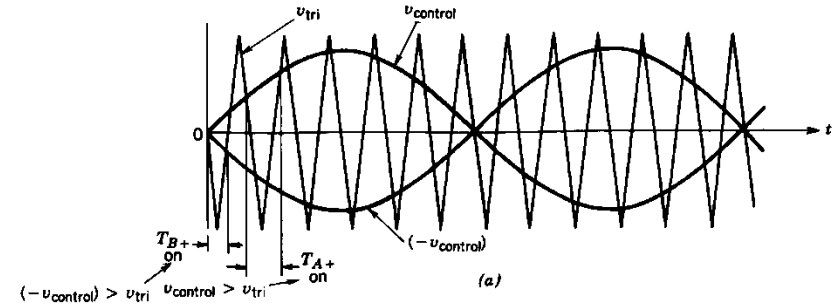b. harmonic components around f_s
are absent



PWM with Unipolar Voltage Switching

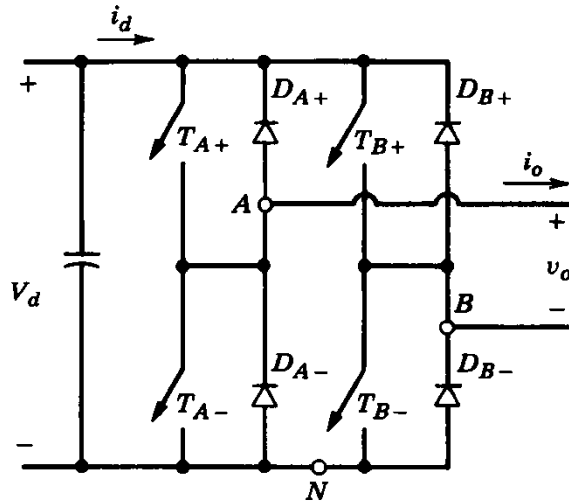


Leg A:

T_{A+} on $i_o > 0$ T_{A+} conducts; $i_{d1} = i_o$
 $i_o < 0$ D_{A+} conducts; $i_{d1} = i_o$
 T_{A-} on $i_o < 0$ T_{A-} conducts; $i_{d1} = 0$
 $i_o > 0$ D_{A-} conducts; $i_{d1} = 0$

Leg B:

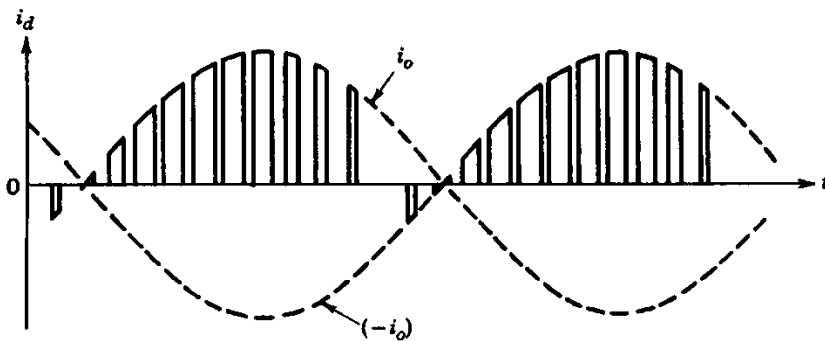T_{B+} on $i_o < 0$ T_{B+} conducts; $i_{d2} = -i_o$
 $i_o > 0$ D_{B+} conducts; $i_{d2} = -i_o$
 T_{B-} on $i_o > 0$ T_{B-} conducts; $i_{d2} = 0$
 $i_o < 0$ D_{B-} conducts; $i_{d2} = 0$



i_d consists of I_d , i_{d2} and the high-frequency components due to inverter switchings.

$$i_d = i_{d1} + i_{d2}$$

6-2. Three-phase Bridge Inverters

switch states

and the corresponding voltage levels

$[T_{A+}, T_{B+}, T_{C+}, T_{A-}, T_{B-}, T_{C-}]$

$= [0, 0, 0, 1, 1, 1]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [0, 0, 0]$

$= [1, 0, 0, 0, 1, 1]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [V_d, 0, -V_d]$

$= [0, 1, 0, 1, 0, 1]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [-V_d, V_d, 0]$


$= [1, 1, 0, 0, 0, 1]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [0, V_d, -V_d]$

$= [0, 0, 1, 1, 1, 0]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [0, -V_d, V_d]$

$= [1, 0, 1, 0, 1, 0]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [V_d, -V_d, 0]$

$= [0, 1, 1, 1, 0, 0]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [-V_d, 0, V_d]$

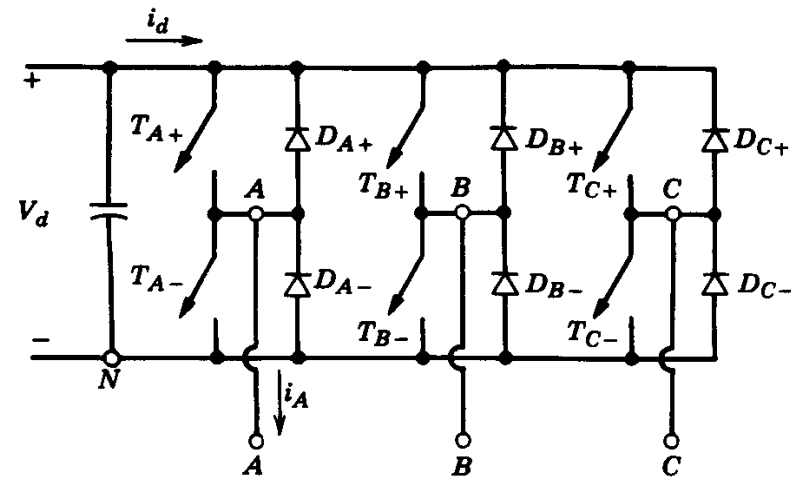$= [1, 1, 1, 0, 0, 0]$ for $V[v_{AB}, v_{BC}, v_{CA}] = [0, 0, 0]$



Three-Phase PWM Waveforms

Leg A:

$$\begin{aligned} v_{control, A} > v_{tri} & \quad T_{A+} \text{ on} \quad v_{AN} = V_d; \\ v_{control, A} < v_{tri} & \quad T_{A-} \text{ on} \quad v_{AN} = 0; \end{aligned}$$

Leg B:




$$\begin{aligned} v_{control, B} > v_{tri} & \quad T_{B+} \text{ on} \quad v_{BN} = V_d; \\ v_{control, B} < v_{tri} & \quad T_{B-} \text{ on} \quad v_{BN} = 0; \end{aligned}$$

Leg C:



$$\begin{aligned} v_{control, C} > v_{tri} & \quad T_{C+} \text{ on} \quad v_{CN} = V_d; \\ v_{control, C} < v_{tri} & \quad T_{C-} \text{ on} \quad v_{CN} = 0; \end{aligned}$$

$$v_{AB} = v_{AN} - v_{BN}$$

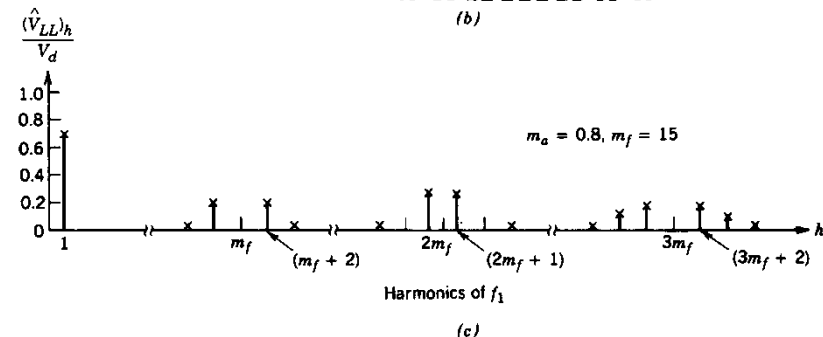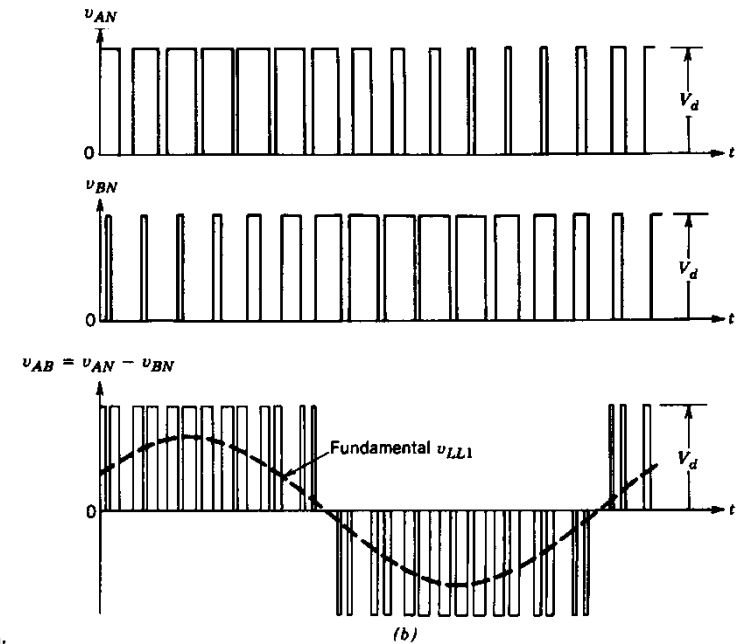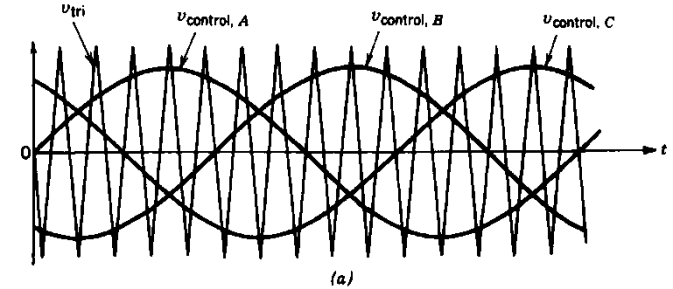m_f should be odd and a multiple of 3 to cancel out even harmonics and the harmonics at the odd multiples of m_f in the line-to-line voltage.



Three-Phase PWM Waveforms

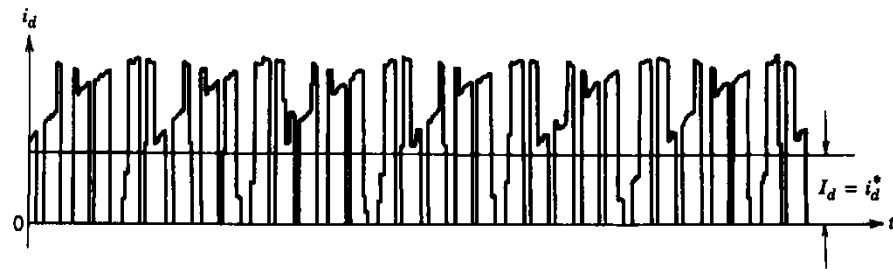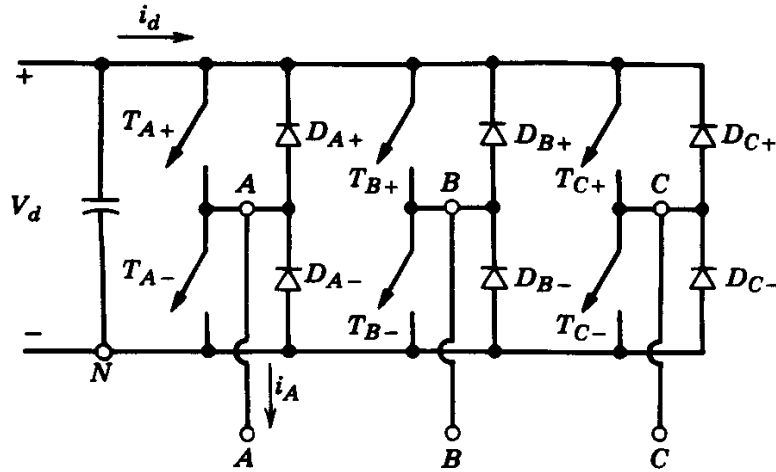

The current consists of a DC component and the switching-frequency related harmonics.

Leg A:

T_{A+} on $i_A > 0$ T_{A+} conducts; $i_{d1} = i_A$
 $i_A < 0$ D_{A+} conducts; $i_{d1} = i_A$
 T_{A-} on $i_A < 0$ T_{A-} conducts; $i_{d1} = 0$
 $i_A > 0$ D_{A-} conducts; $i_{d1} = 0$

Leg B:

T_{B+} on $i_B > 0$ T_{B+} conducts; $i_{d2} = i_B$
 $i_B < 0$ D_{B+} conducts; $i_{d2} = i_B$
 T_{B-} on $i_B < 0$ T_{B-} conducts; $i_{d2} = 0$
 $i_B > 0$ D_{B-} conducts; $i_{d2} = 0$

Leg C:

T_{C+} on $i_C > 0$ T_{C+} conducts; $i_{d3} = i_C$
 $i_C < 0$ D_{C+} conducts; $i_{d3} = i_C$
 T_{C-} on $i_C < 0$ T_{C-} conducts; $i_{d3} = 0$
 $i_C > 0$ D_{C-} conducts; $i_{d3} = 0$

$$i_d = i_{d1} + i_{d2} + i_{d3}$$

Three-Phase PWM Waveforms

Linear

$$V_{LL1rms} = 0.612 m_a V_d$$

$$m_a \leq 1$$



Over-modulation $0.612 V_d < V_{LL1rms} < 0.78 V_d$

$$m_a > 1$$



Square-wave operation

$$V_{LL1rms} = 0.78 V_d$$

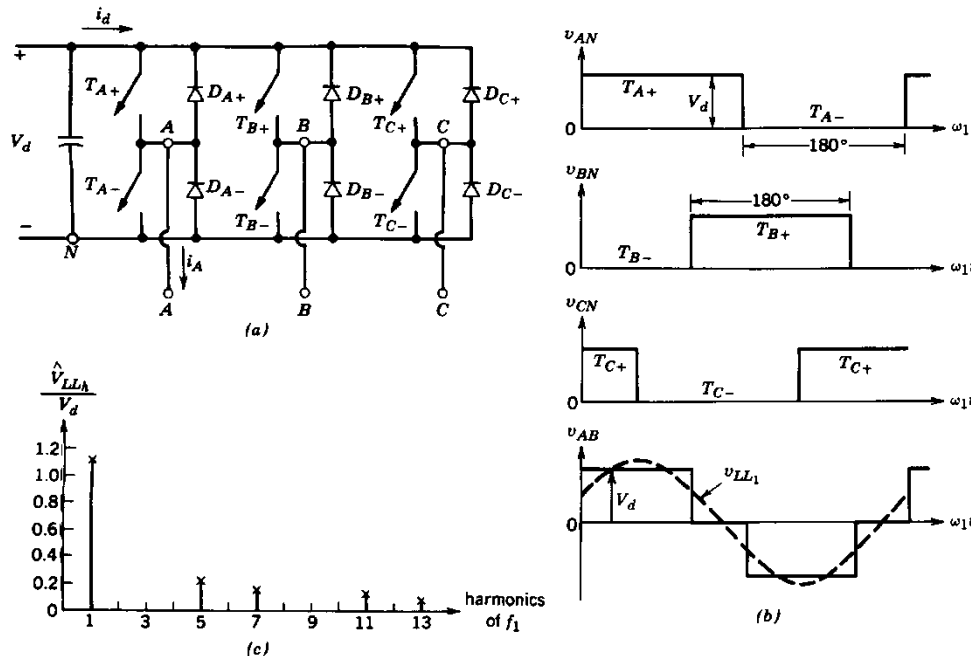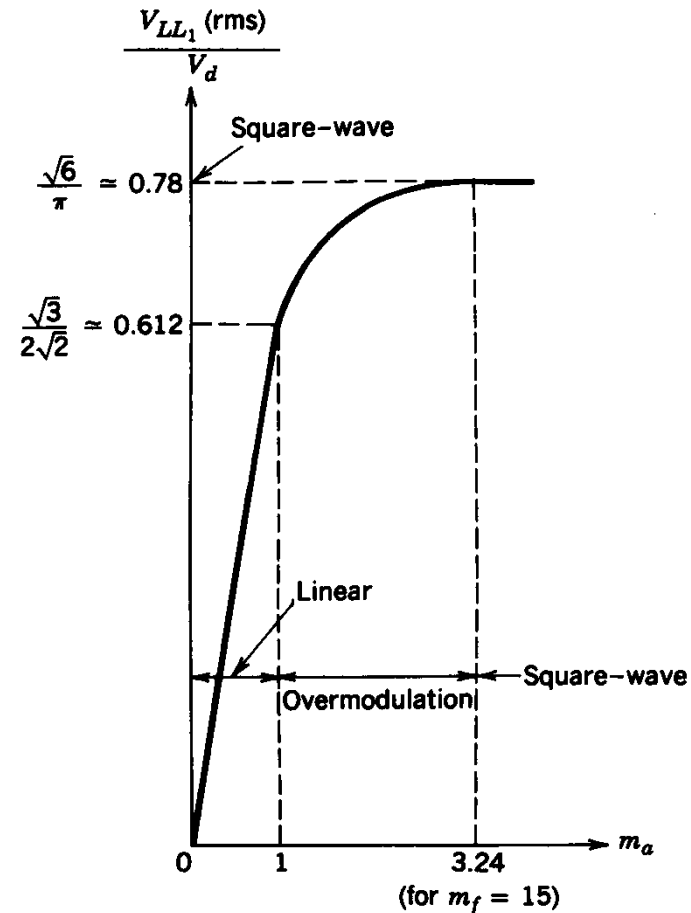Output voltage Fundamental
as a Function of m_a




Fundamental Frequency

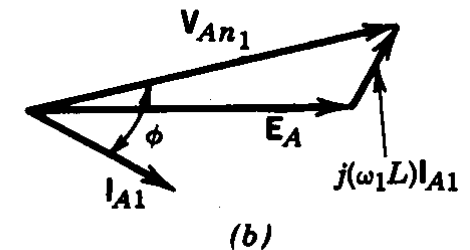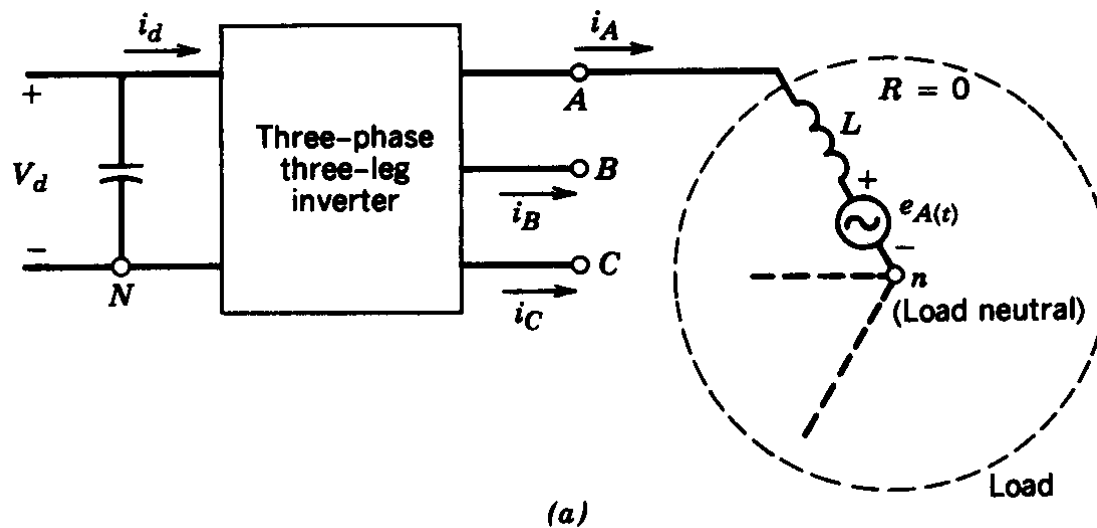


Analysis at the fundamental frequency can be done using phasors.


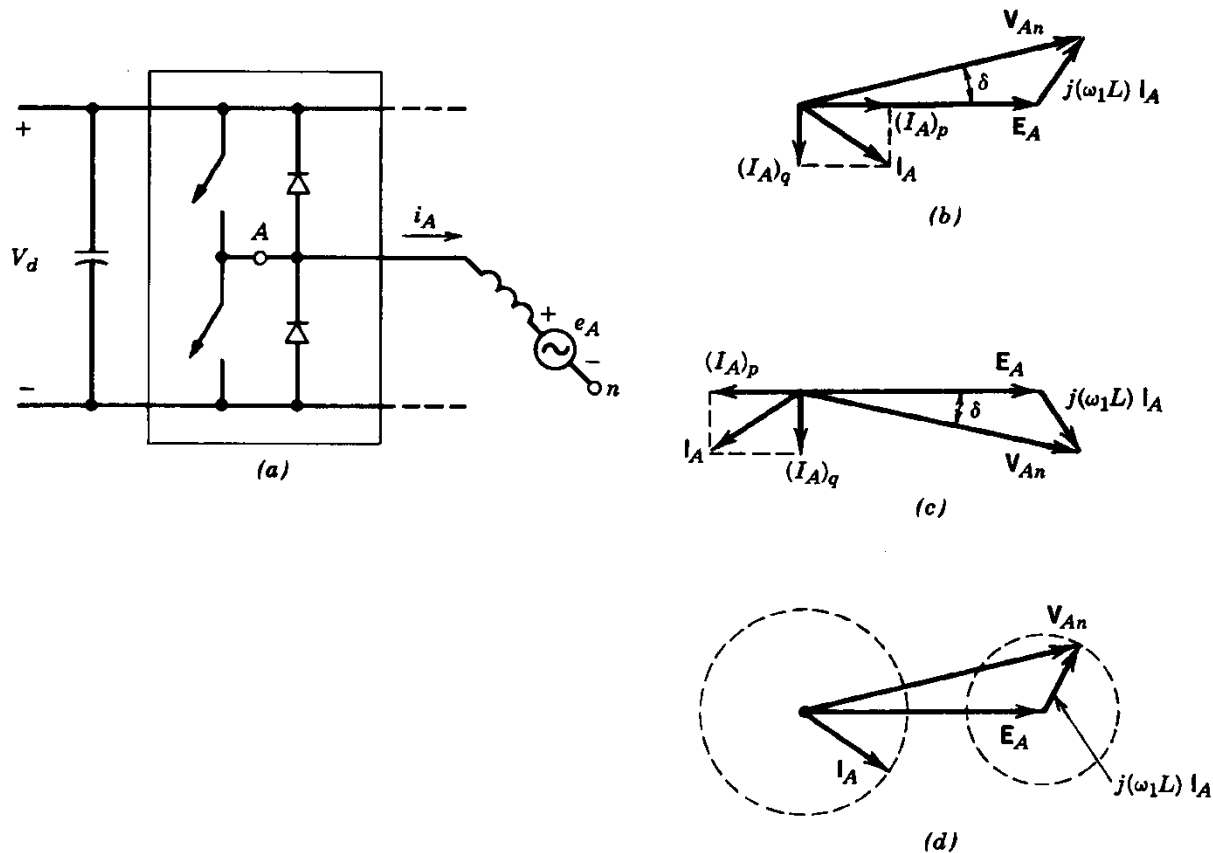
Transition from Inverter to Rectifier Mode





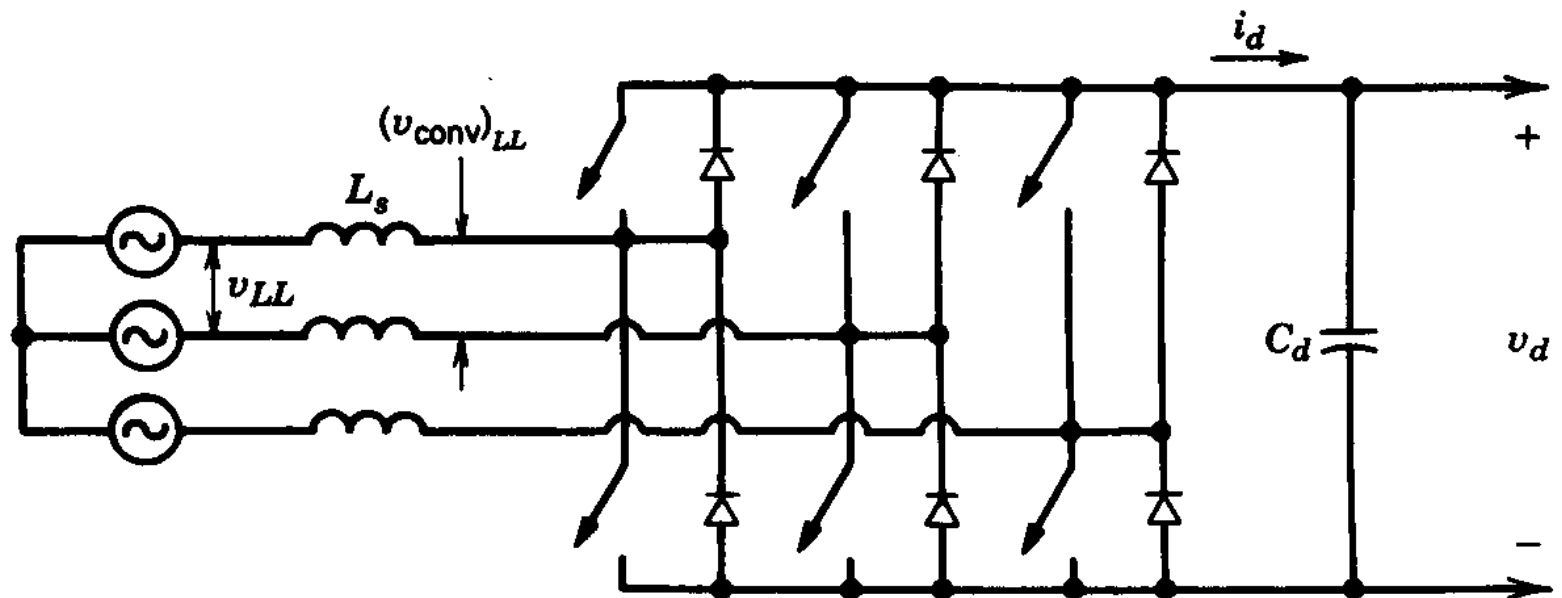
analysis based on the fundamental-frequency components



6-3. Effect of Blanking Time

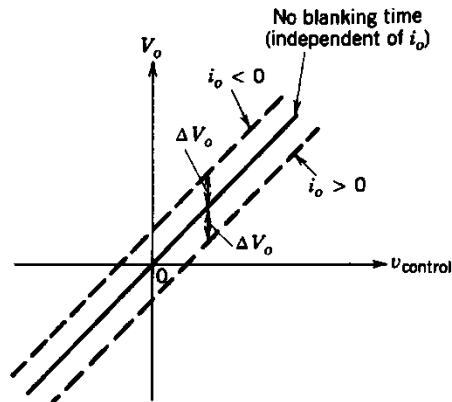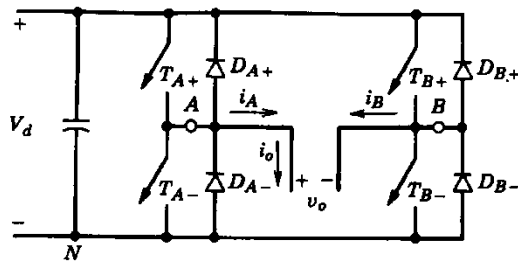

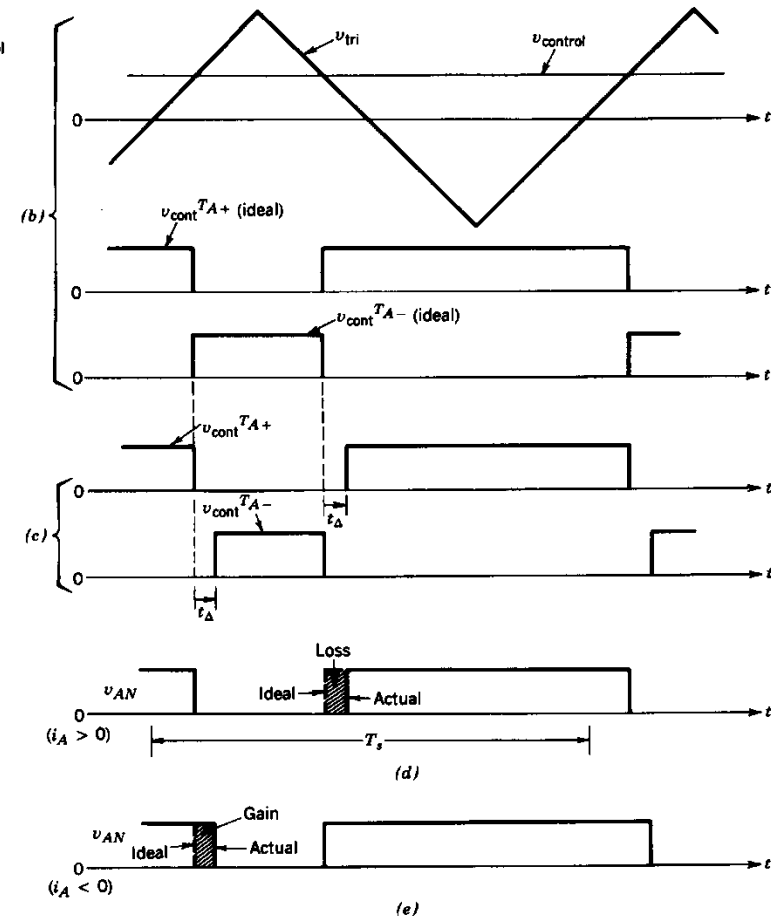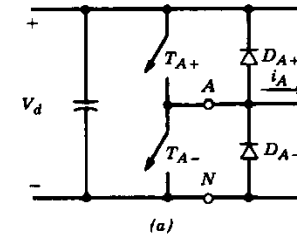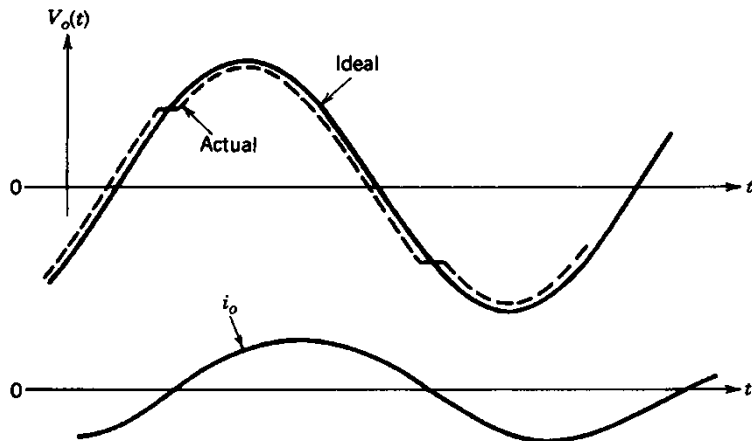Voltage jump when the current reverses direction



Summary:

- DC-AC inverter v.s. thyristor AC/DC inversion mode
- Switch states in DC/AC inverter (T, output voltage, current)
- Output voltage modulation method (waveforms)
- Output voltage and four-quadrant operation
- Frequency/amplitude modulation ratio: harmonics, over-modulation
- Required both for single-phase and three-phase DC-AC inverters

The End

