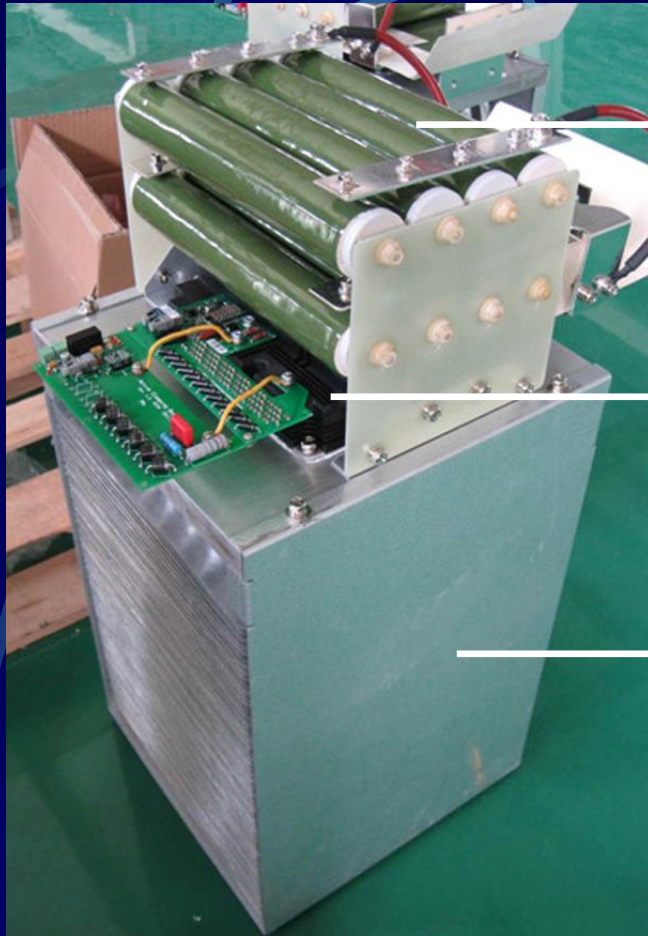


***Chapter 6***

# **Snubber Circuits**

# *Power Electronics*




**Snubber design during  
switching transients**

**IGBT**

**Heatsink**
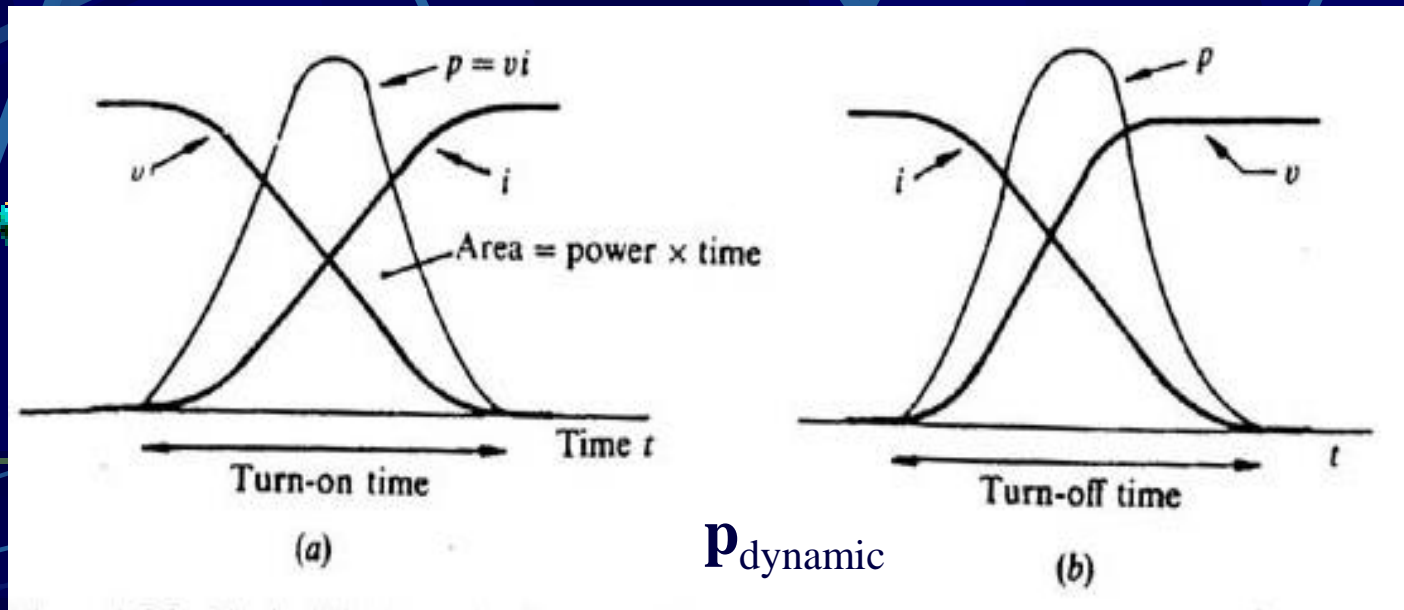
# Problem 1: Switching Power Losses of Power Devices





$$W_{\text{dynamic}} = \int_{\text{turn-on}} i(t) v(t) dt + \int_{\text{turn-off}} i(t) v(t) dt$$

$$P_{\text{dynamic}} = f W_{\text{dynamic}}$$

--- significant at high-frequency operation

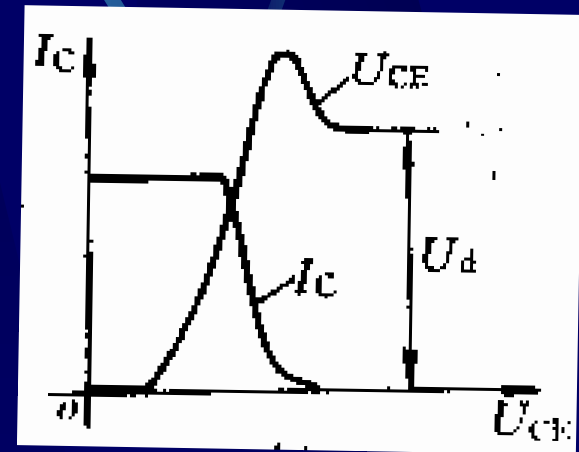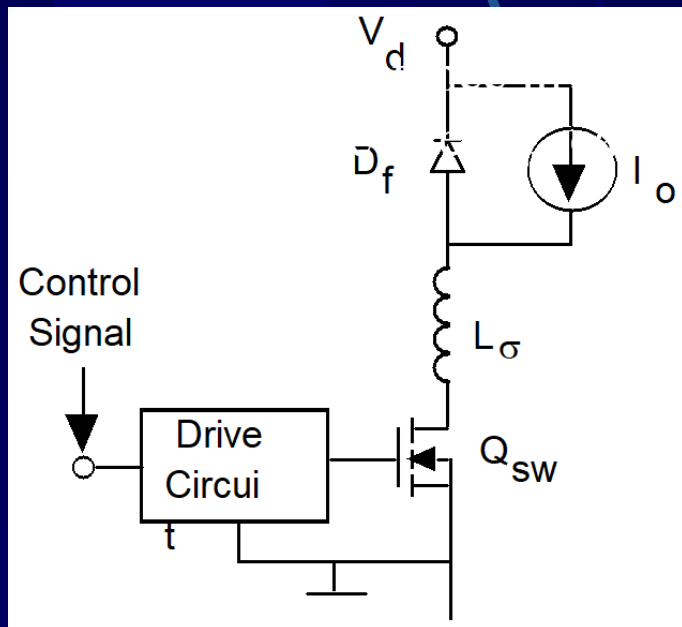
## Problem 2: Surge Voltage at Turn-off

Stray inductance in series with high-voltage side of power device  $Q_{sw}$  causes overvoltage at turn-off.







**$L_\sigma$  -- Stray inductance**

# Safe Operating Area

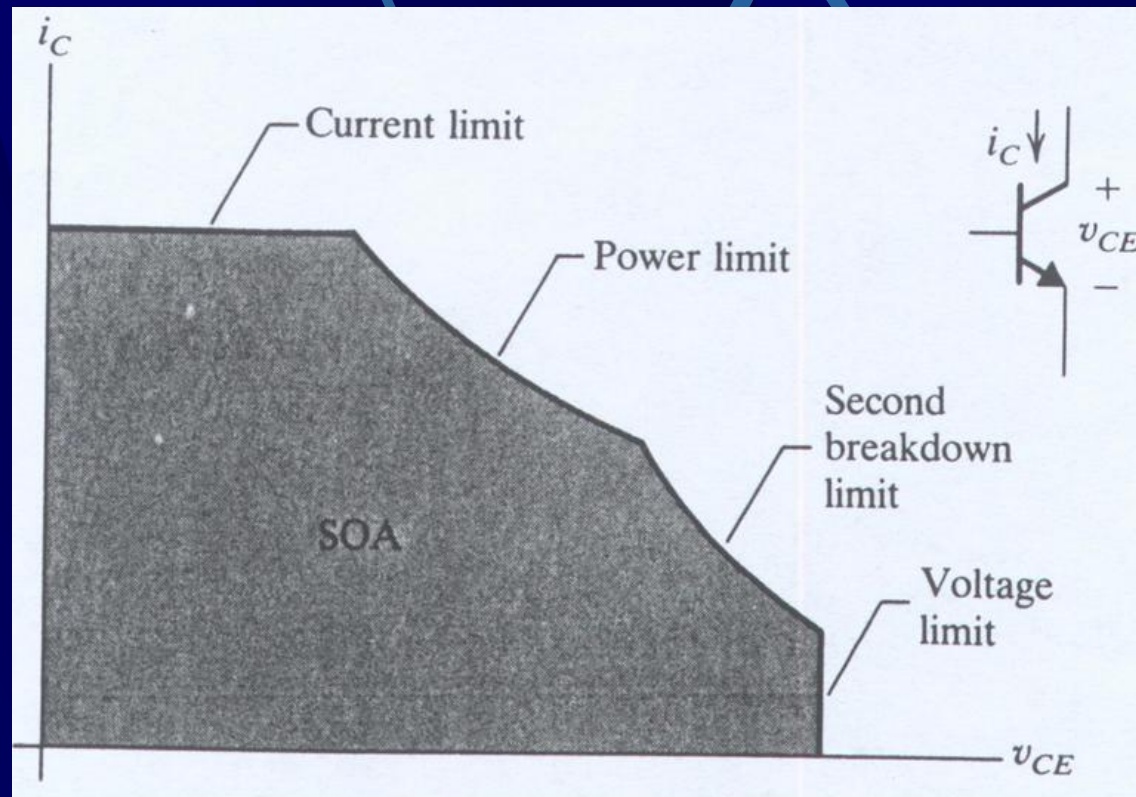
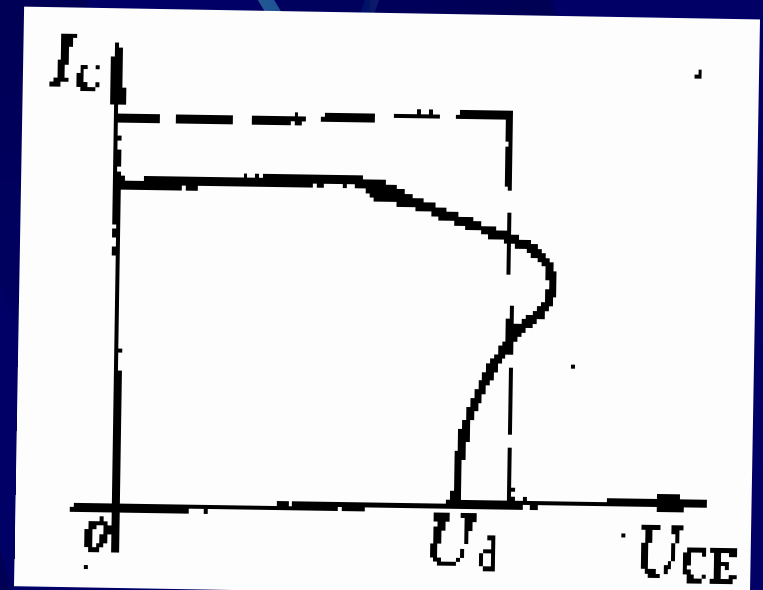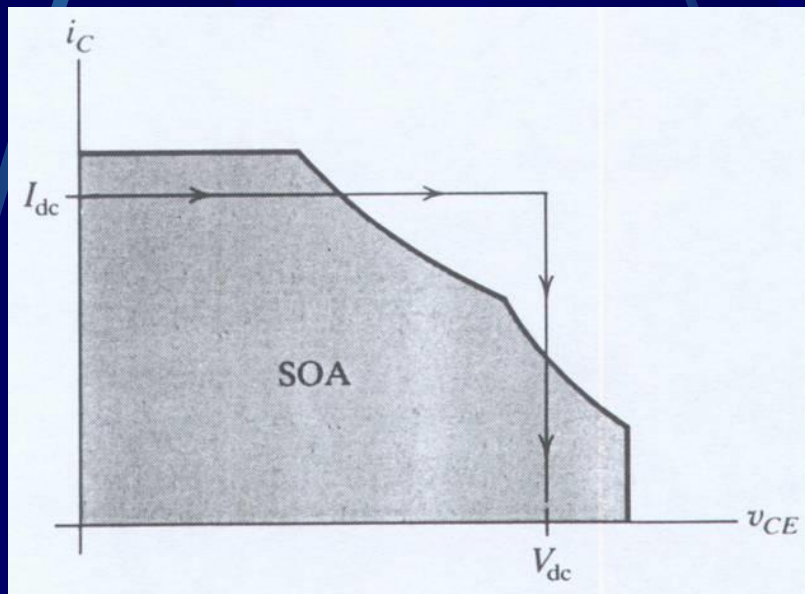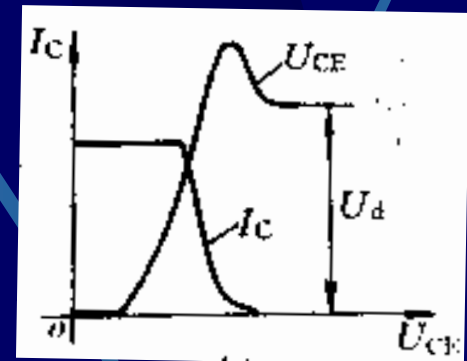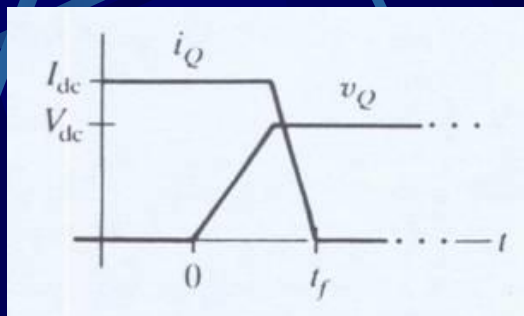
# Switching Locus of the Turn-off Transition





Without stray inductance

With stray inductance


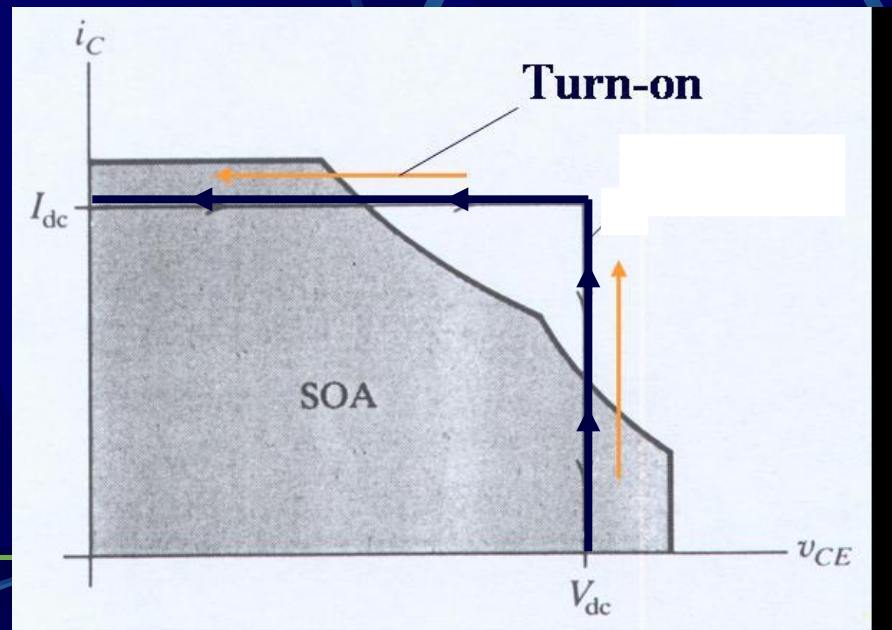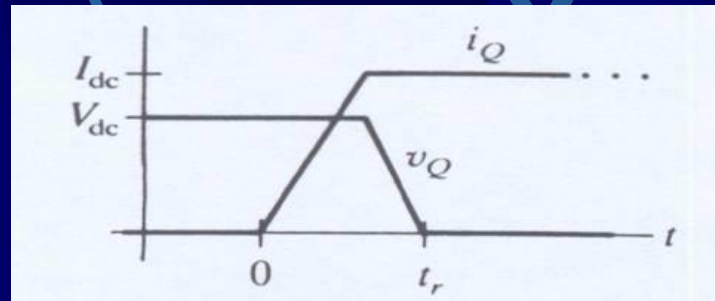
# Switching Locus of the Turn-on Transition



## Snubber Circuits

to control, or limit,  
the transient voltage and current of a power device  
**when it makes turn-off and turn-on commutations**

keeping the voltage and current  
within the **safe operating area**



## Two kinds of snubber circuits:

- **turn-off snubber**



to control the turn-off by small capacitors

- **turn-on snubber**

to control the turn-on by small inductors

# 6-1 The Turn-off Snubber

## Turn-off Dissipation

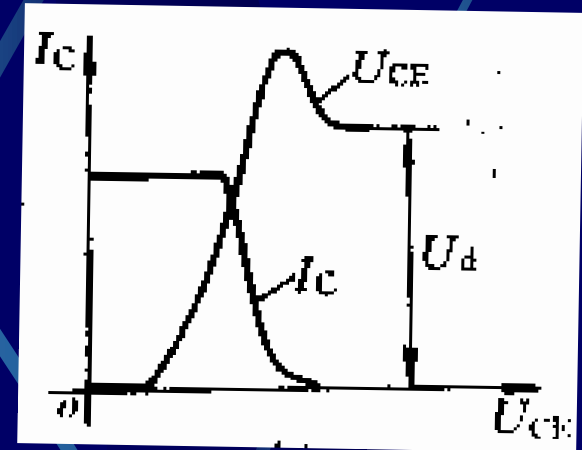
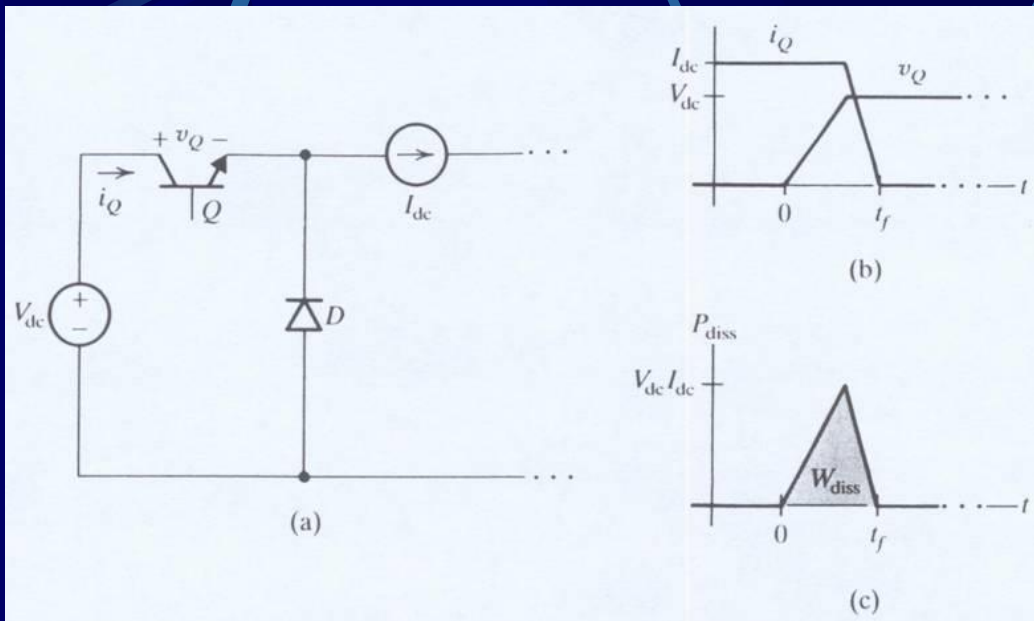


**With stray inductance**

$$W_{diss} = \int_0^{t_f} v_Q i_Q dt$$



If the switching frequency were  $f$  Hz,  $fW_{diss}$  would be dissipated in the transistor.

## A Basic Turn-off Snubber

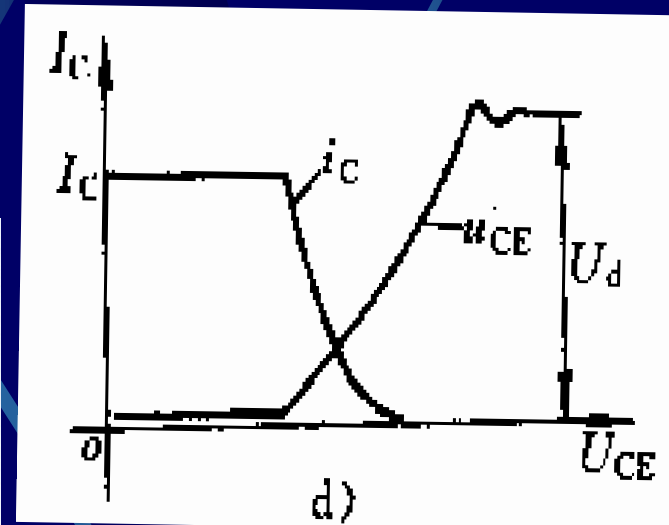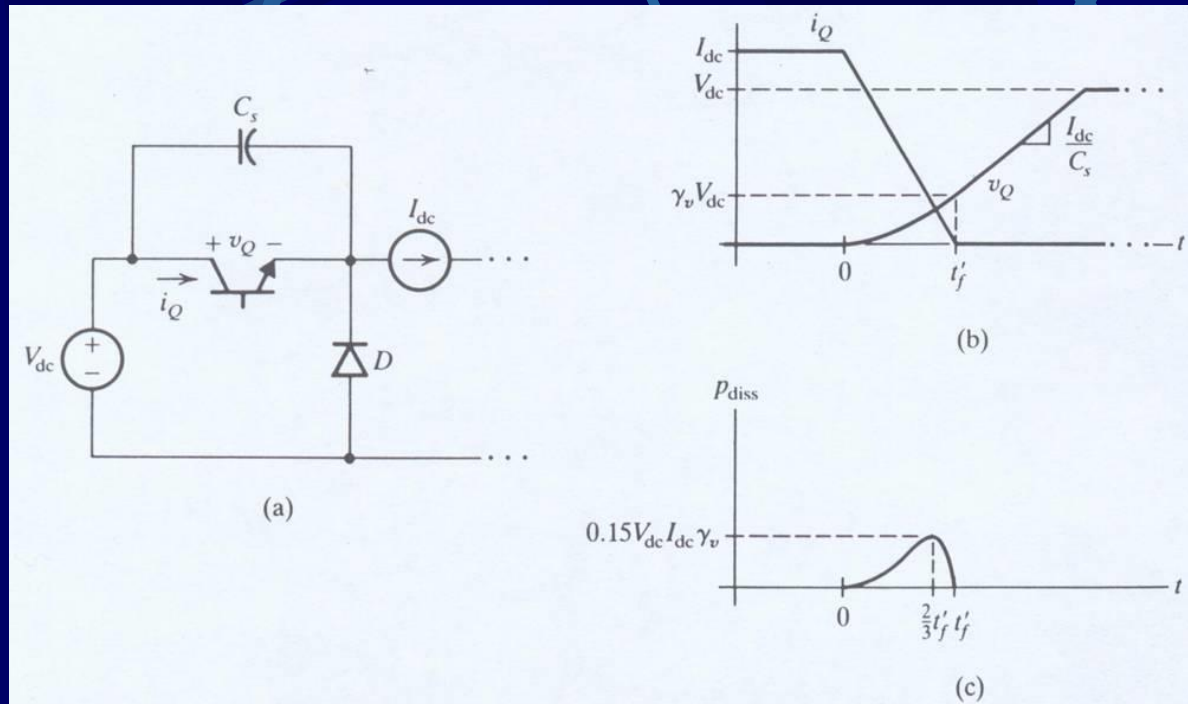

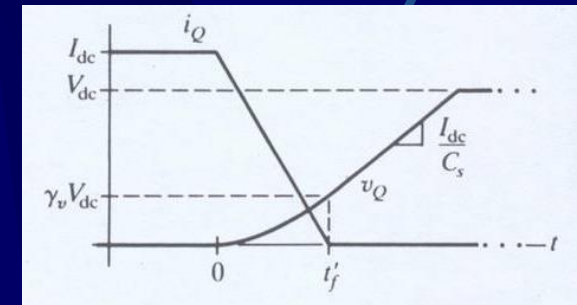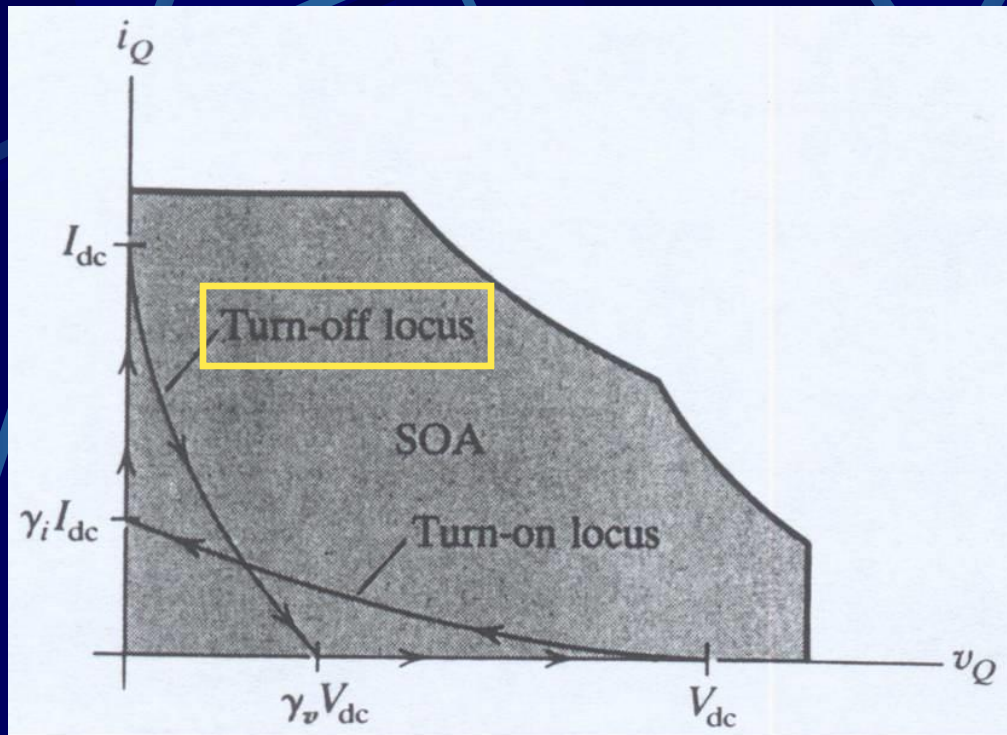
**With stray inductance**

**$C_s$**  -- to limit the rise rate of the voltage during the turn-off transition.



The turn-on and **turn-off** switching loci of the transistor when a basic snubber circuit added.

## A More Practical Snubber


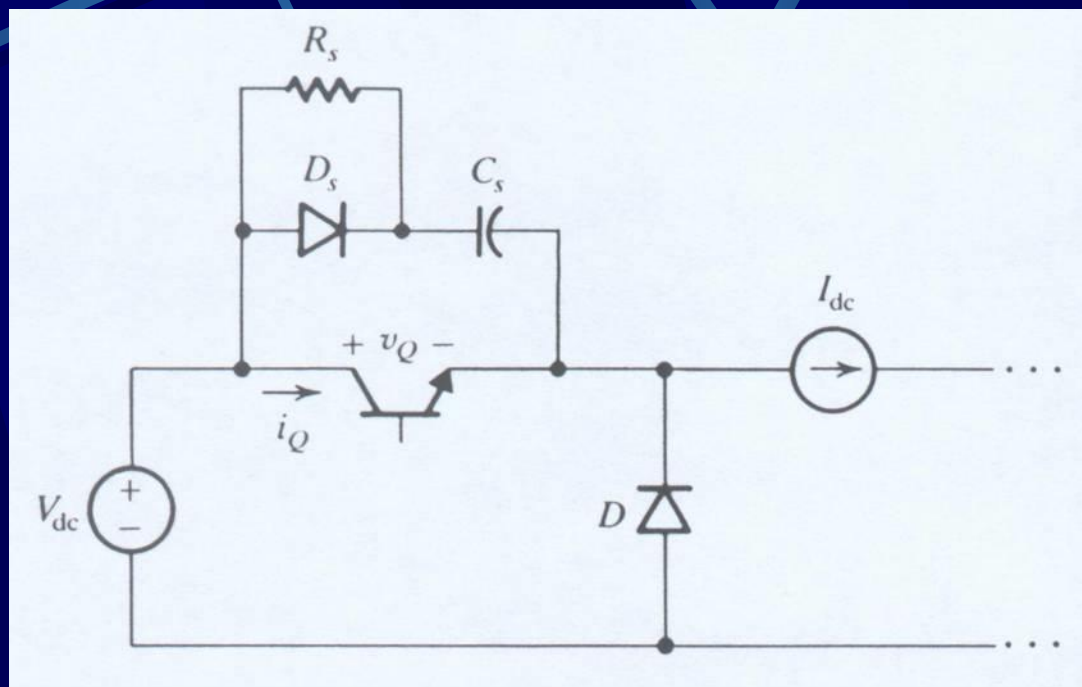


**$R_s$**  -- to limit the discharge current when the BJT is turned on.




**$D_s$**  -- to allow the charging current to bypass  **$R_s$**  during turn-off.

## 6-2 The Turn-on Snubber

### Turn-on Dissipation

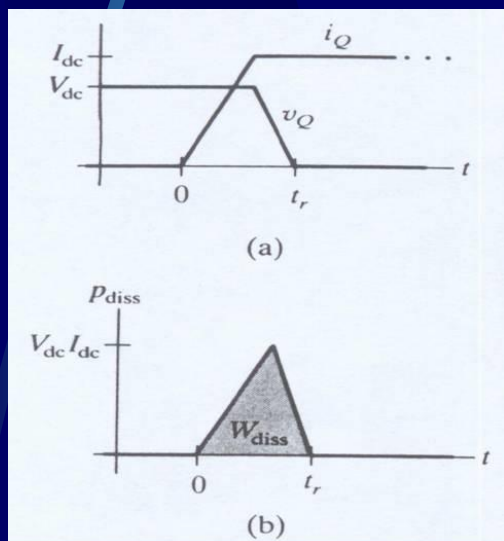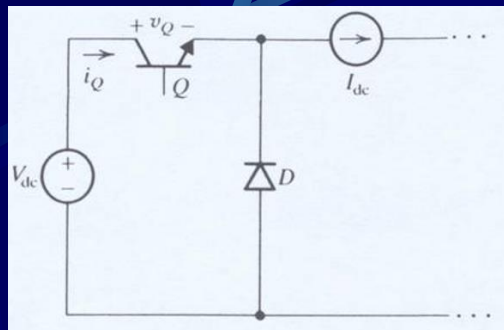



### A Basic Turn-on Snubber

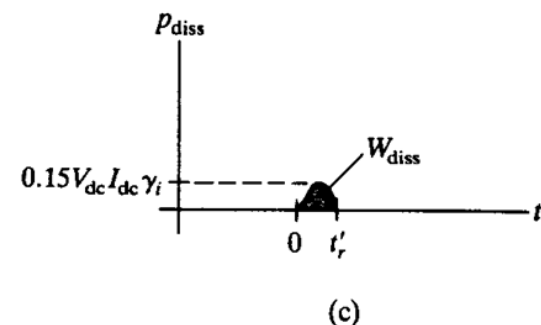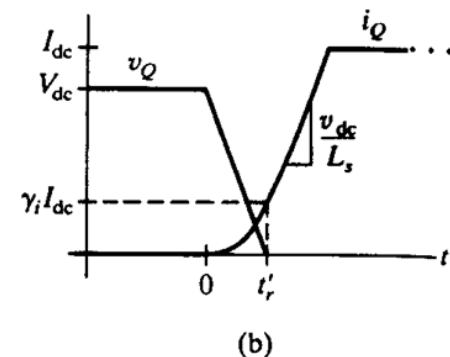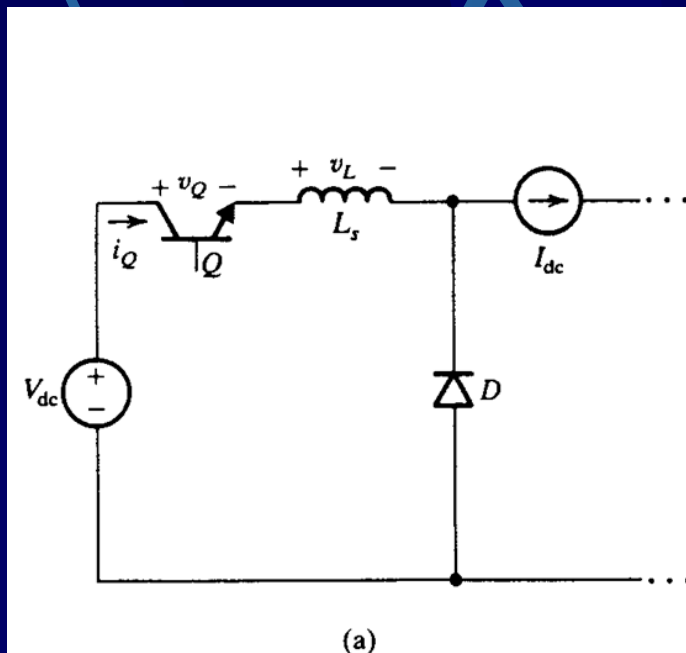

**Without snubber**

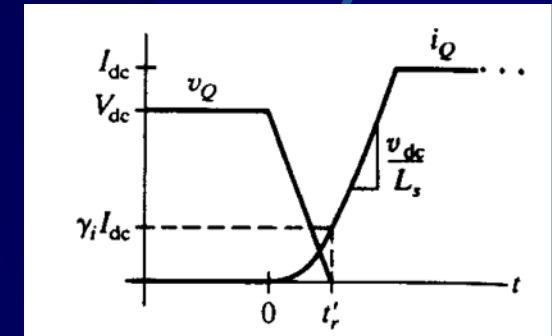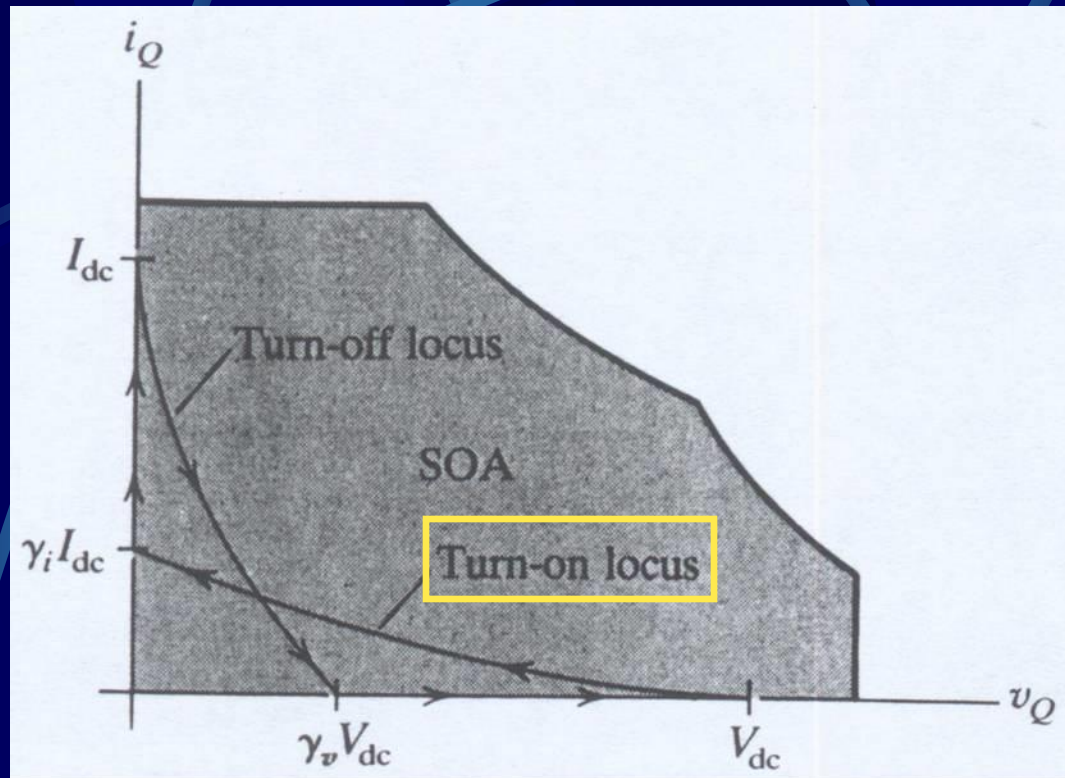**$L_s$  -- to limit the rise rate of the current during the turn-on transition.**






The **turn-on** and turn-off switching loci of the transistor when a basic snubber circuit added.




## A More Practical Snubber

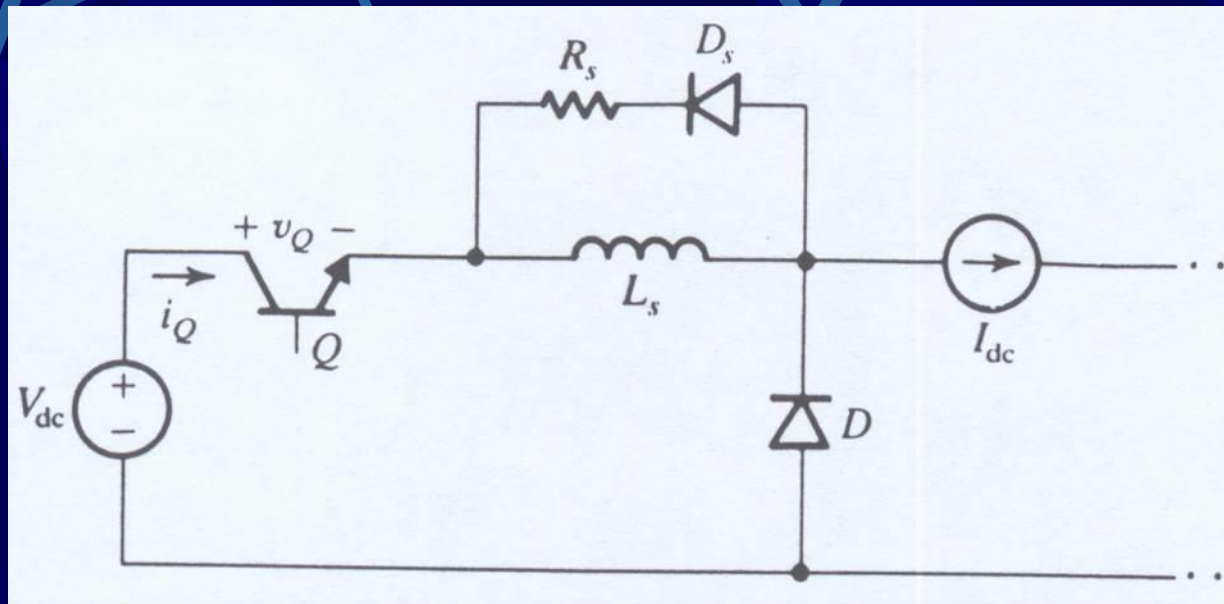


**$R_s$**  – to provide an alternative path for  **$L_s$**  current when turn-off.

**$D_s$**  -- to keep  **$R_s$**  from conducting during turn-on.

## 6-3 Energy Recovery Snubbers

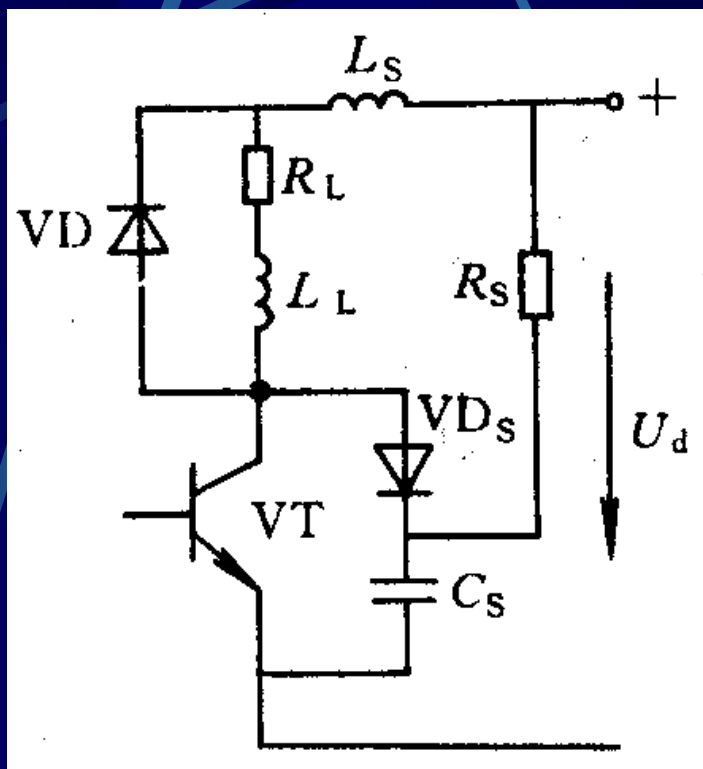


An clamp turn-off.

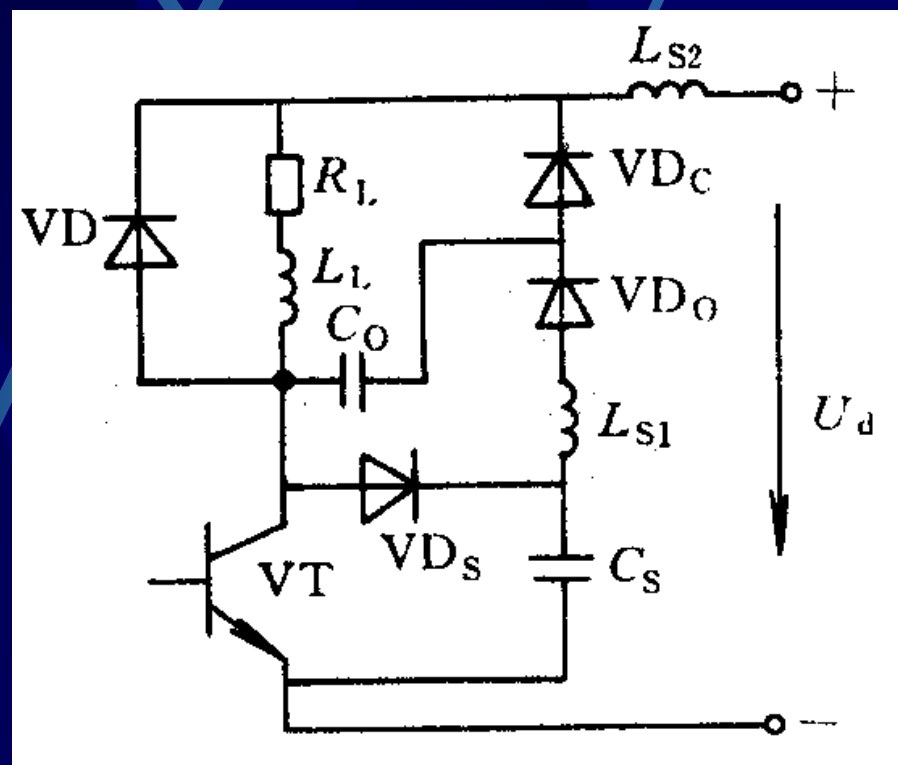

An energy recovery turn-off.

## 6-4 Snubbers in Bridge Inverters

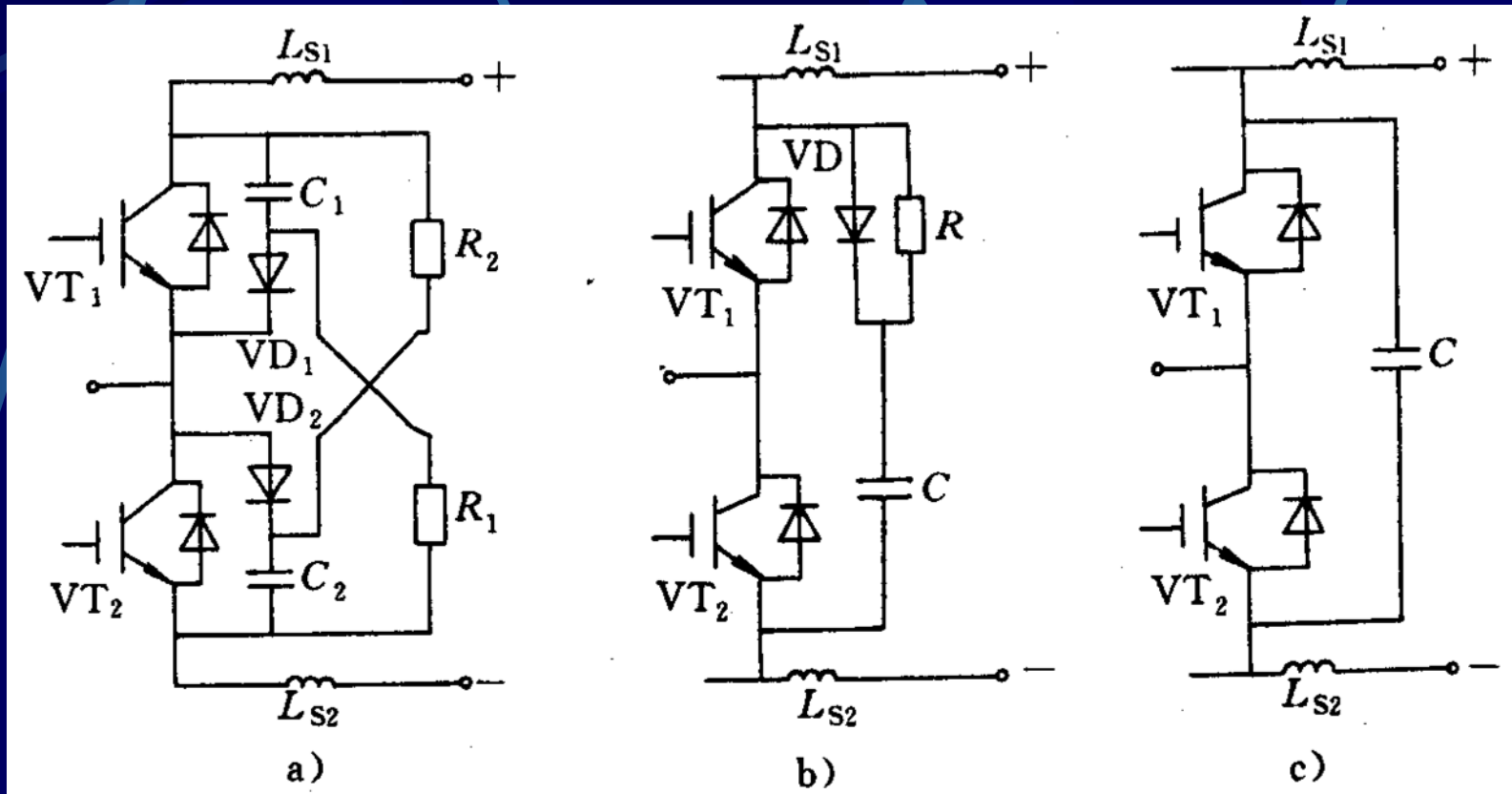

*The End*

