

Assignment

Simulate the single-phase and three-phase bridge DC-AC circuits using two sets of the circuit parameters below, analyze and compare the fundamental component and harmonics in the output line-to-line voltages and input current by the Fourier Analysis.

- 1) $V_d = 540 \text{ V}$, $R_{\text{load}} = 5 \Omega$, $L_{\text{load}} = 5 \text{ mH}$, $f_1 = 50 \text{ Hz}$, $m_a = 0.8$, $m_f = 39$;
- 2) $V_d = 540 \text{ V}$, $R_{\text{load}} = 5 \Omega$, $L_{\text{load}} = 5 \text{ mH}$, $f_1 = 50 \text{ Hz}$, $m_a = 1.2$, $m_f = 44$.

Simulate the frequency converter AC-DC-AC using the three phase bridge diode AC-DC with the input line voltage of 380 Vrms, design the capacitor of the DC link, calculate the power factor on the input AC side.