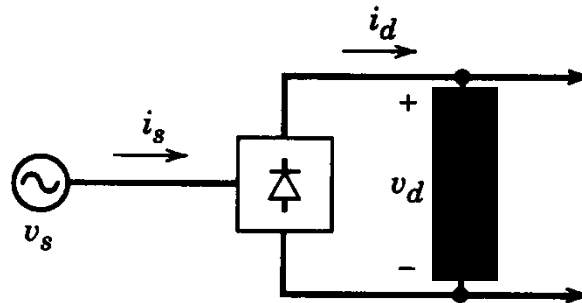


Chapter 2

Diode Rectifiers

a line-frequency diode rectifier:

a line-frequency AC voltage \rightarrow an uncontrolled DC voltage



Uncontrolled utility interface (AC to DC)

DC voltages: a mean (DC) level + *an alternating ripple*

AC currents: non-sinusoidal

$\gamma_f = \mathbf{f}_{R(rms)} / \mathbf{f}_{mean}$ — ripple factor (DC voltage)

$\xi_f = \mathbf{f}_{1(rms)} / \mathbf{f}_{rms}$ — distortion factor (AC current)



Study focus:

analyzing waveforms of various rectifiers

DC output: voltage, current waveforms


AC input: voltage, current waveforms

Devices: voltage, current waveforms

Assumption: 1) volt-drop negligible when conducting;
2) turn-on and turn-off times instantaneous.

a key point: commutation

Single-phase bridge

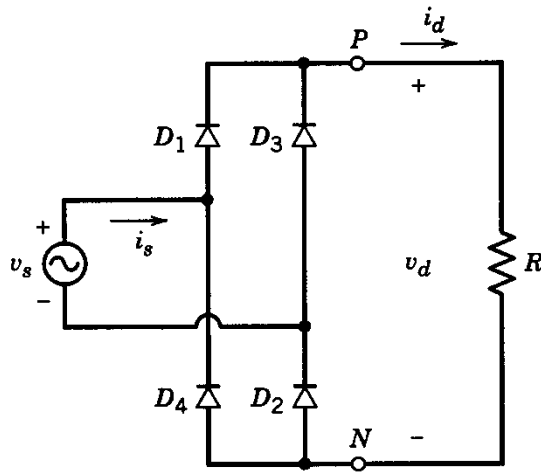

Load: pure resistance



DC output: v_d, i_d

AC input: v_s, i_s


Devices: $v_{\text{diode}}, i_{\text{diode}}$

Commutation
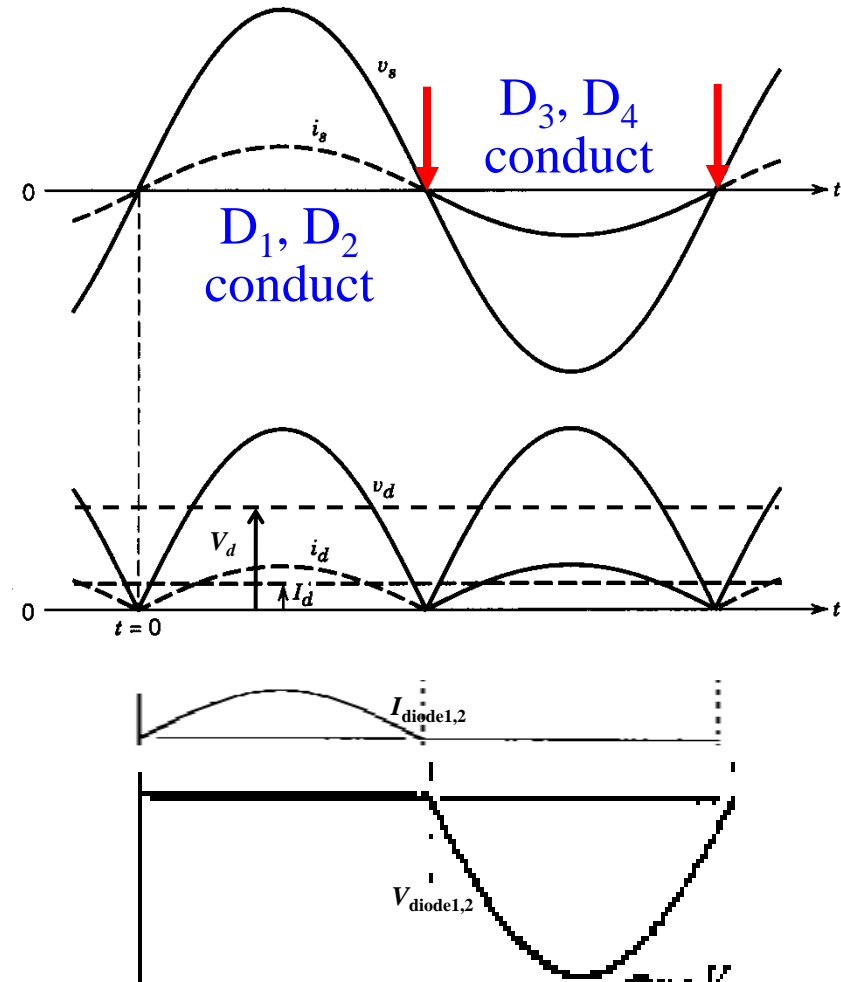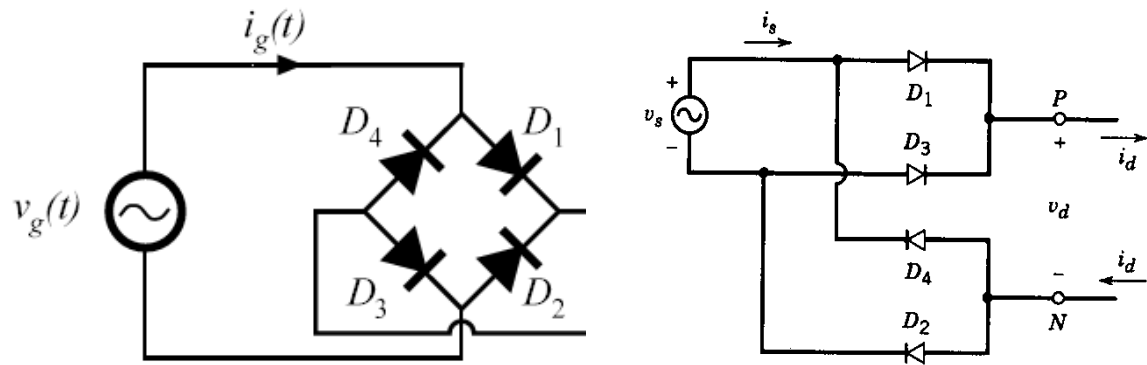
$$V_d = 2V_{\text{smax}}/\pi \quad I_d = V_d/R$$



Single-phase bridge

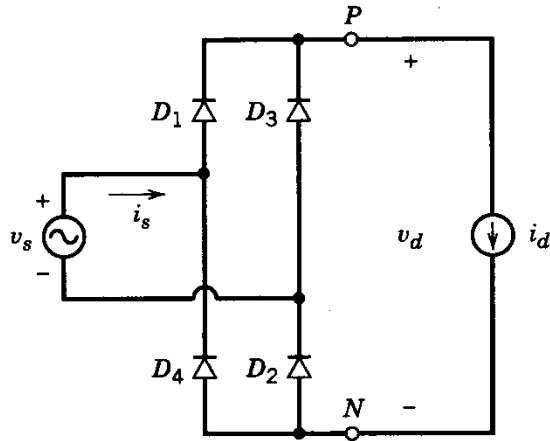



Inductive Load (R-L)

Load: idealized inductive

DC output: v_d, i_d

AC input: v_s, i_s

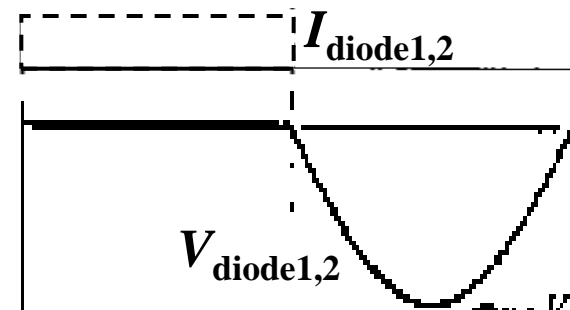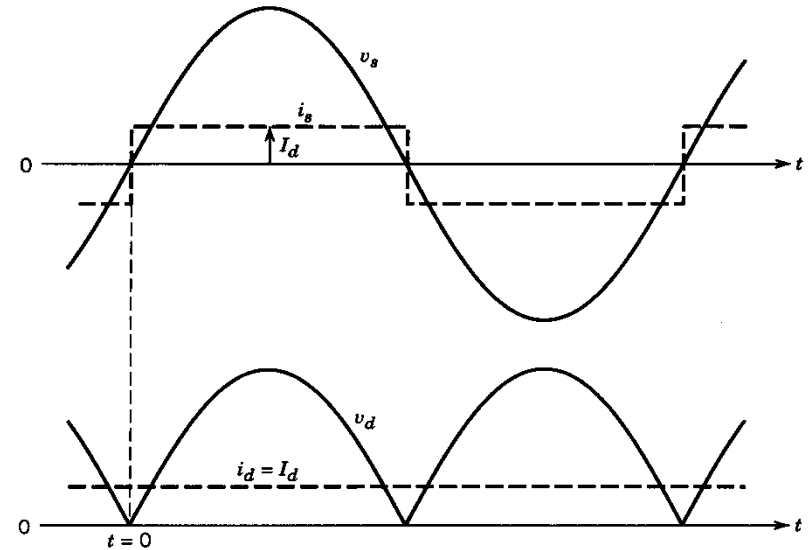
Devices: $v_{\text{diode}}, i_{\text{diode}}$



$$V_d = 2V_{\text{smax}}/\pi \quad I_d = V_d/R$$

Single-phase bridge

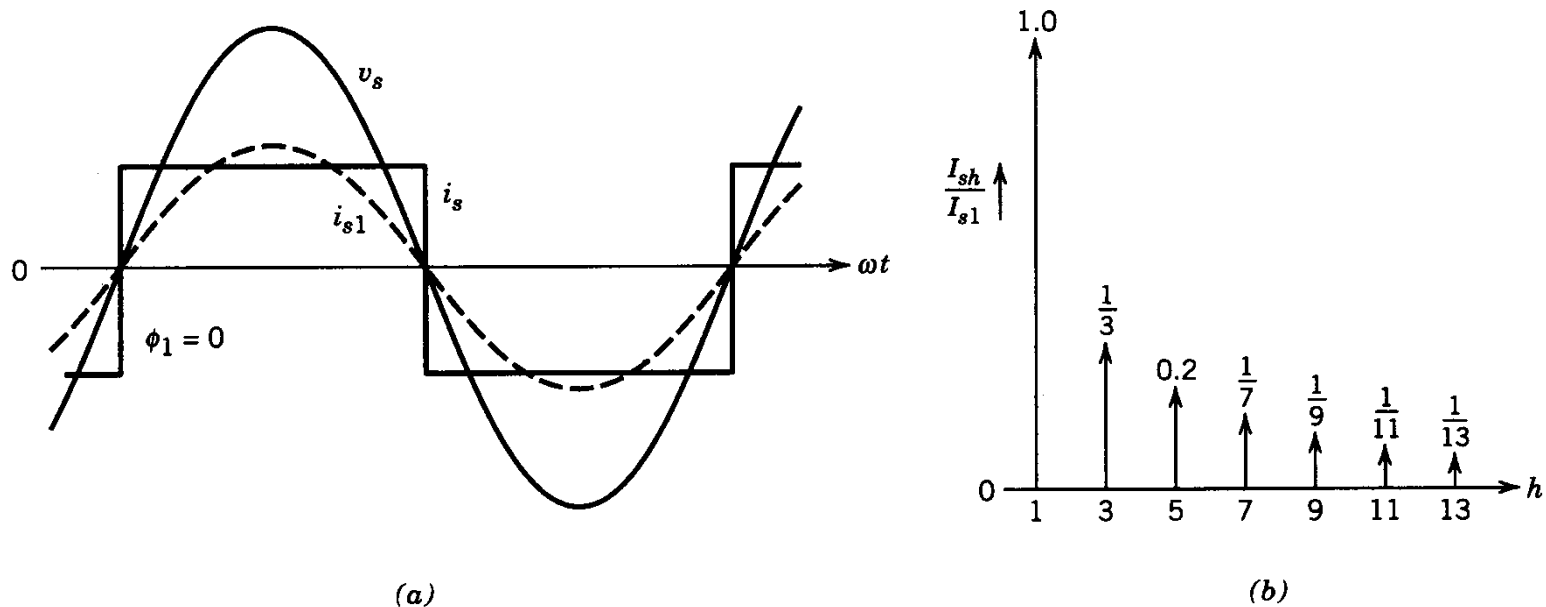Input current and its harmonic components



$$I_{s1} = 0.9I_d$$

$$\xi \text{ (distortion factor)} = I_{s1}/I_s = 0.9$$


$$\text{PF (power factor)} = \xi \cos\phi_1 = 0.9$$



Single-phase bridge

Circuit analysis with ac-side inductance

Understanding current commutation

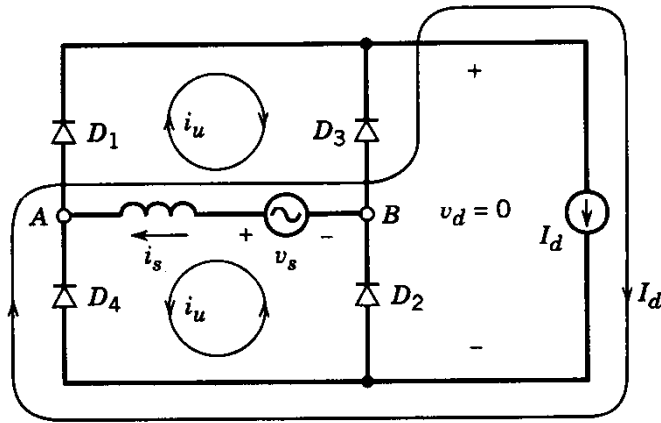

$$v_s = V_{smax} \sin \omega t = L_s di_s / dt$$



$$[t = 0, \quad i_s = -I_d] \quad i_s = V_{smax} / (\omega L_s) \bullet (1 - \cos \omega t) - I_d$$

$$\omega t = u \text{ (overlap angle), } i_s = I_d$$

$$I_d = V_{smax} / (\omega L_s) \bullet (1 - \cos u) - I_d$$



$$\cos u = 1 - 2 \omega L_s I_d / V_{smax}$$

$$V_d = V_{smax} / \pi (1 + \cos u)$$

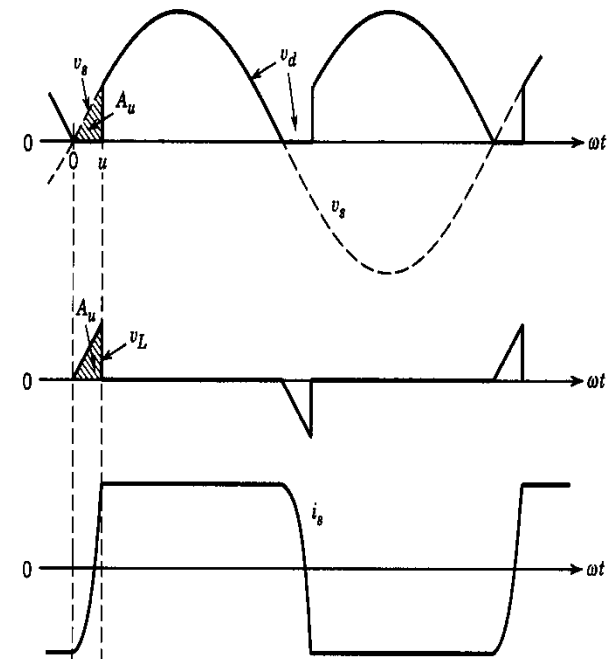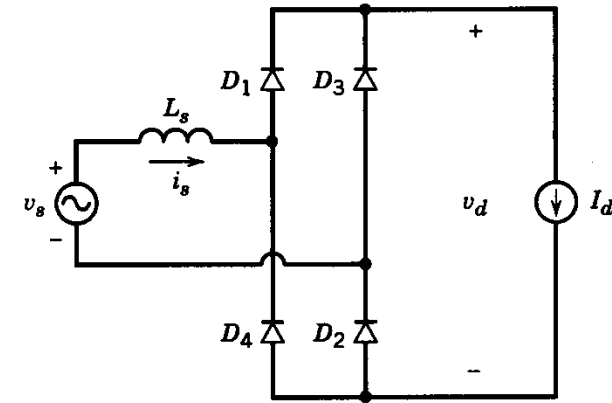


Single-phase bridge

Diode Rectifiers

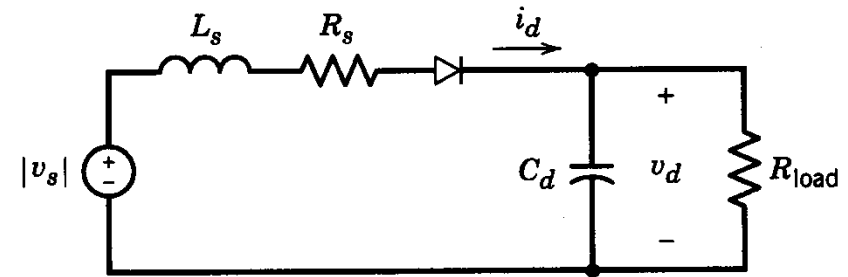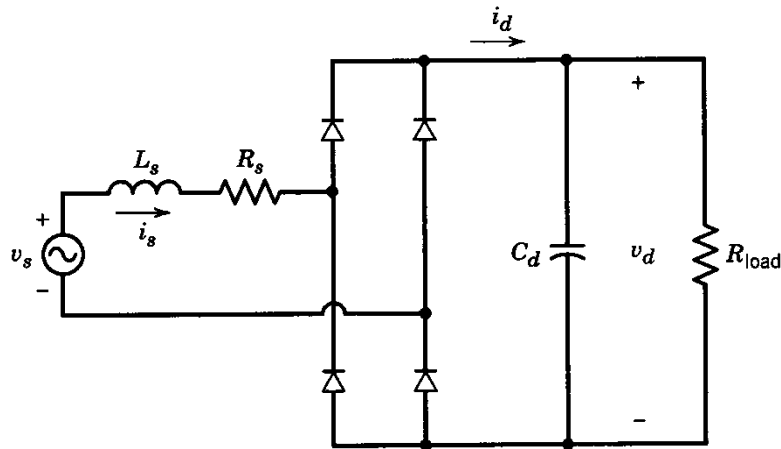


Equivalent circuit on one-half cycle basis

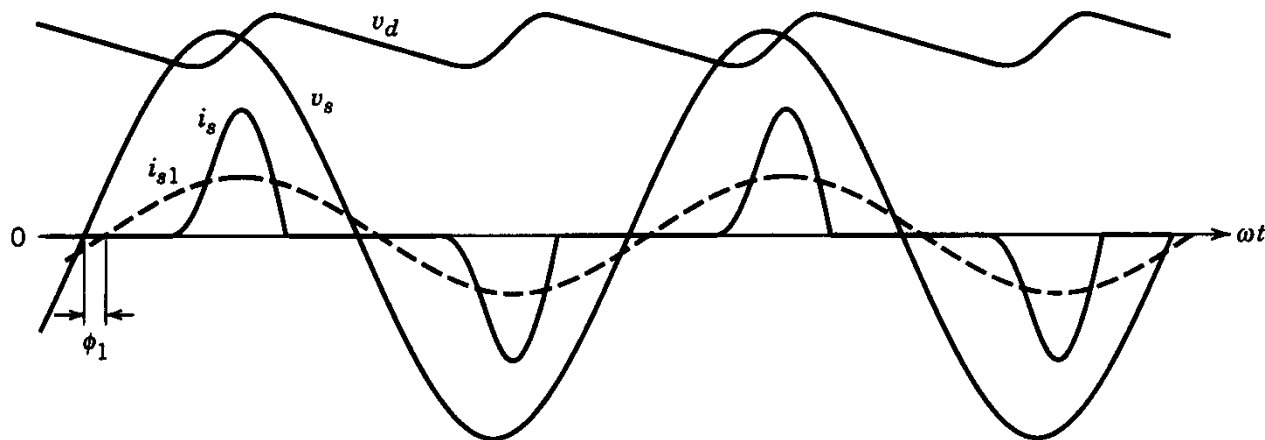**Practical diode-bridge rectifier
with a filter capacitor.**




$$V_s = 120\text{V at } 60\text{Hz}, L_s = 1\text{mH}, R_s = 1\text{m}\Omega, C_d = 100\mu\text{F}, R_{load} = 20\Omega.$$



Single-phase bridge

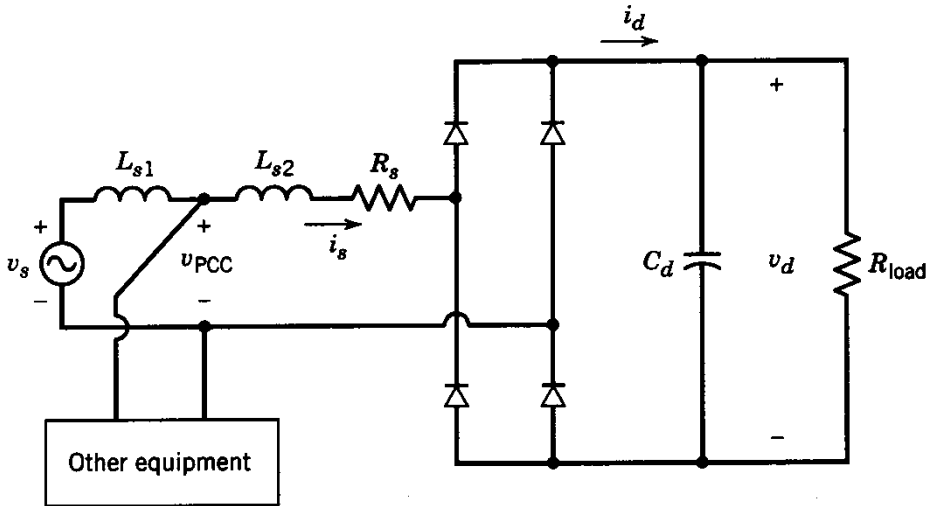


Line-Voltage Distortion

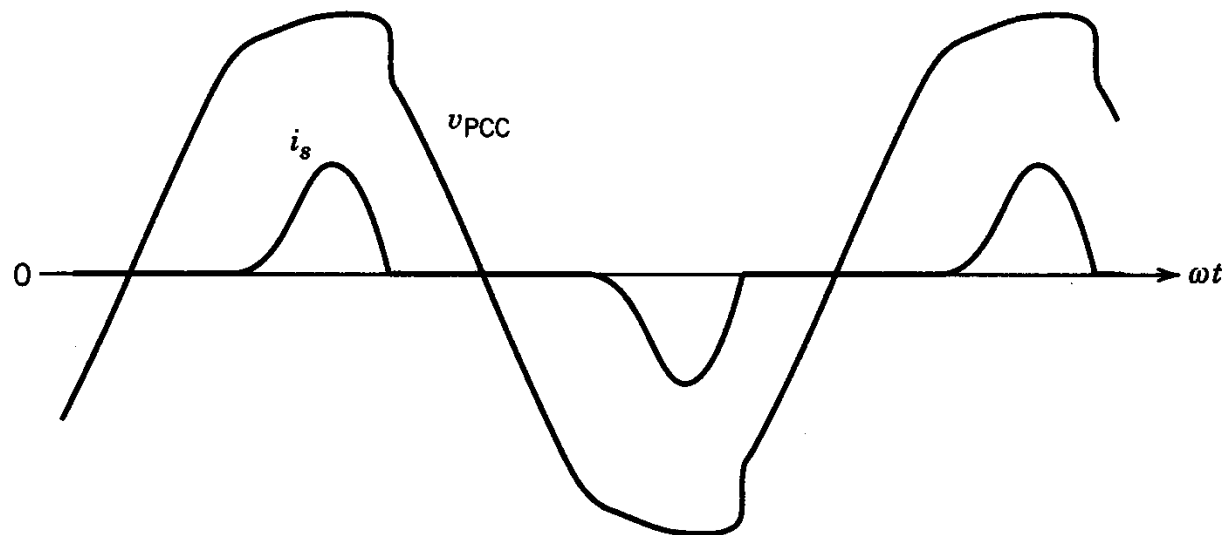

Three-phase bridge

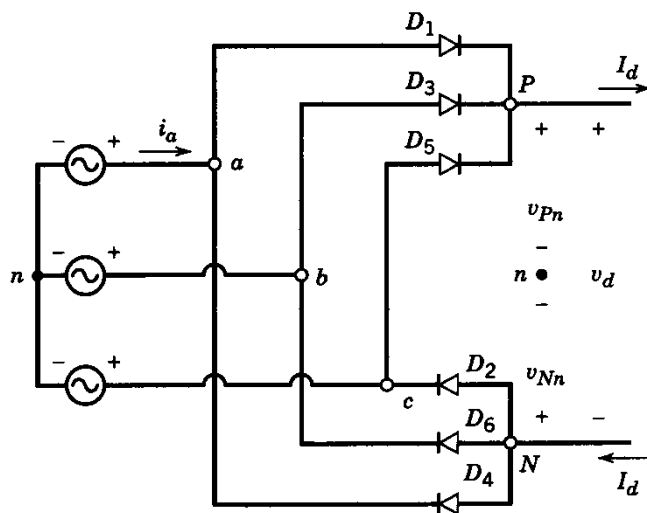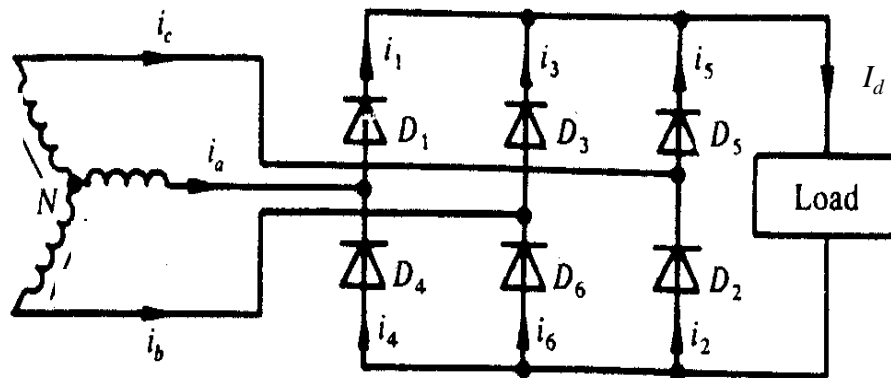

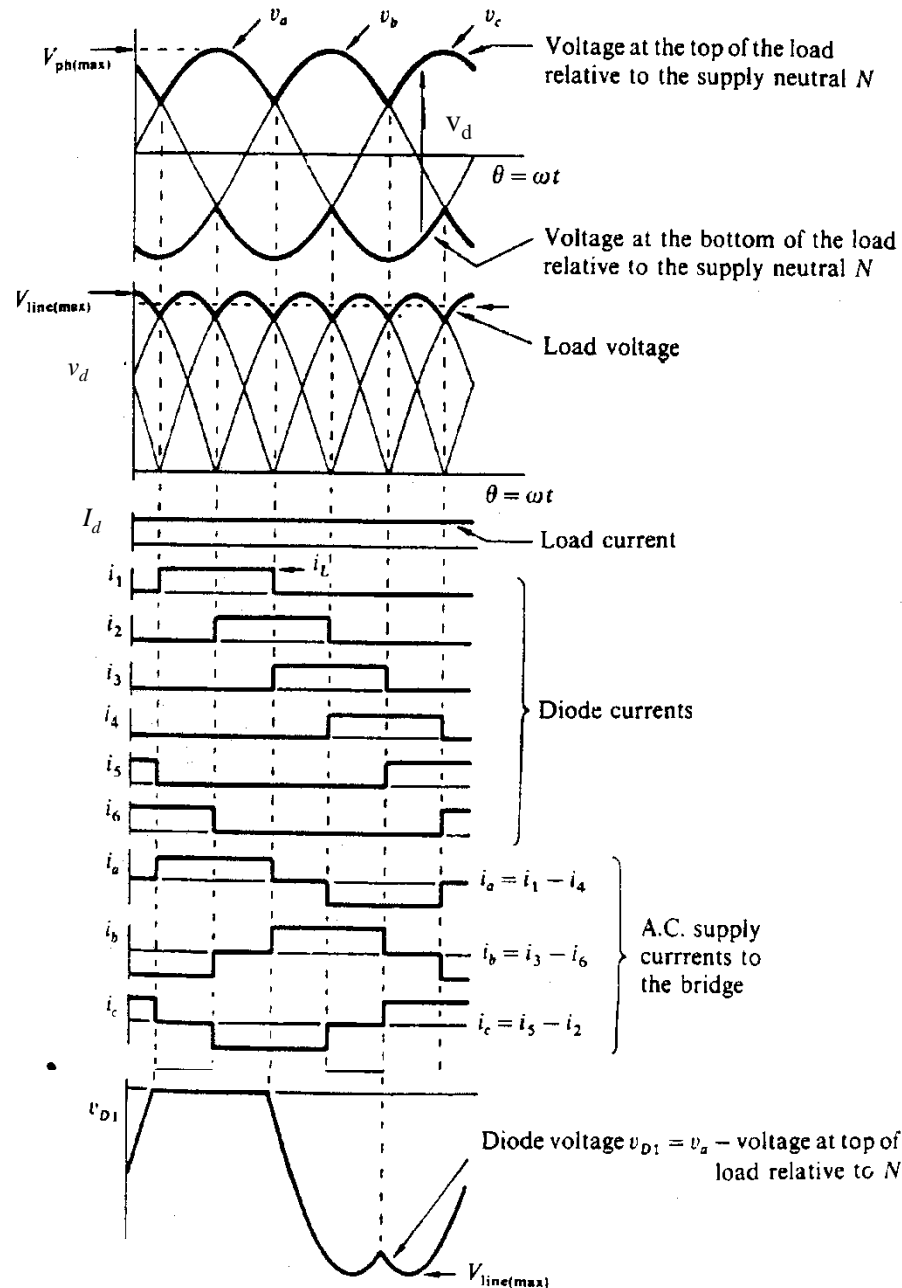
$$V_d = 2 \times 3 \sqrt{3} / 2\pi V_{ph(max)} \\ = 3/\pi V_{line(max)}$$



Three-phase bridge

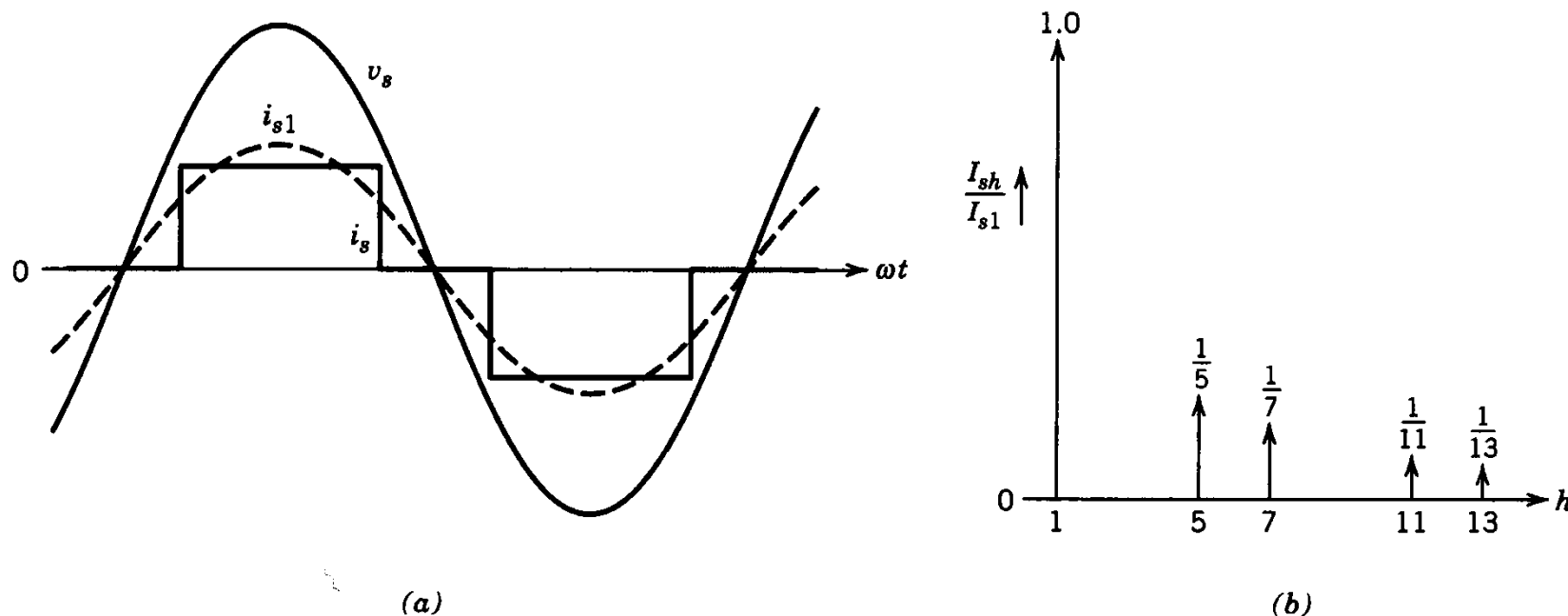Input current and its harmonic components



$$I_{s1} = 0.78I_d$$


$$\xi \text{ (distortion factor)} = I_{s1} / I_s = 0.955$$

$$\text{PF (power factor)} = \xi \cos\phi_1 = 0.955$$

Three-phase bridge

Circuit analysis with ac-side inductance

Understanding current commutation

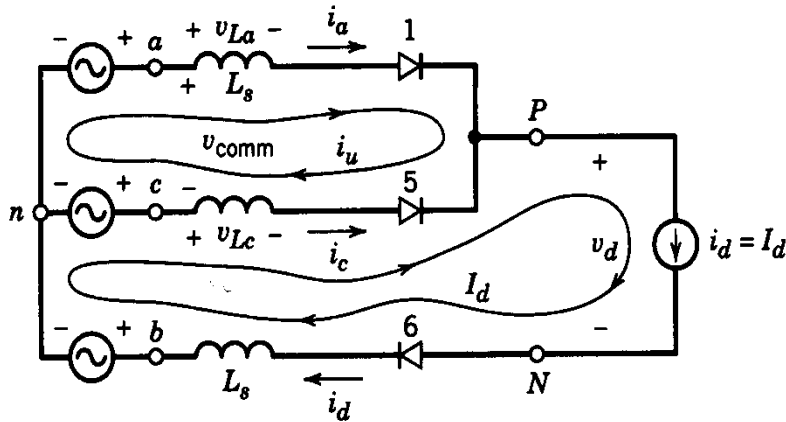

$$v_a - v_c = \sqrt{3}V_{\text{line(max)}} \sin \omega t = 2L_s di_u/dt$$

$$i_a = i_u, \quad i_c = I_d - i_u$$




$$t = 0, \quad i_u = 0$$

$$i_a = i_u = V_{\text{line(max)}} / (2\omega L_s) \bullet (1 - \cos \omega t)$$

$$\omega t = u, \quad i_a = I_d \quad (\omega L_s = X)$$

$$\cos u = 1 - 2XI_d / V_{\text{line(max)}}$$
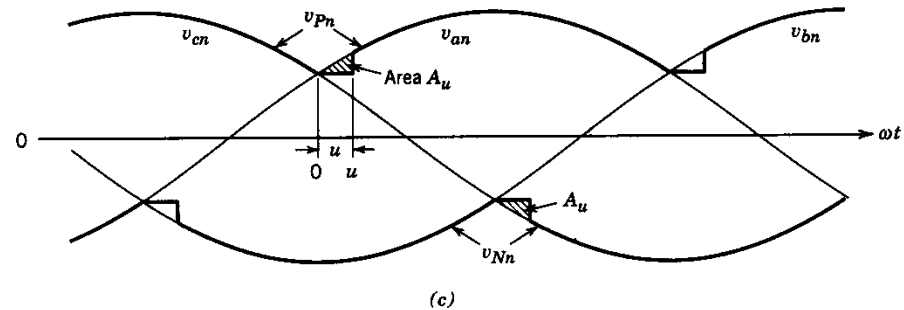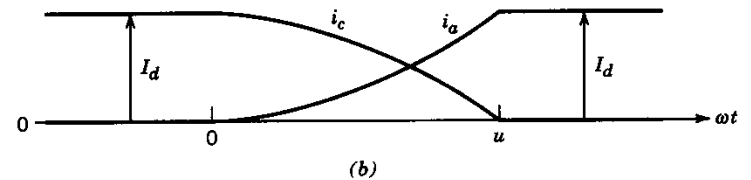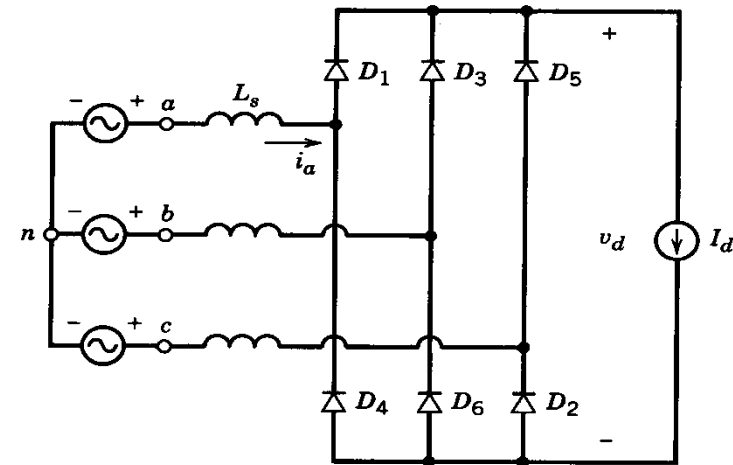
$$V_d = 3V_{\text{line(max)}} / 2\pi (1 + \cos u)$$



Diode Rectifiers


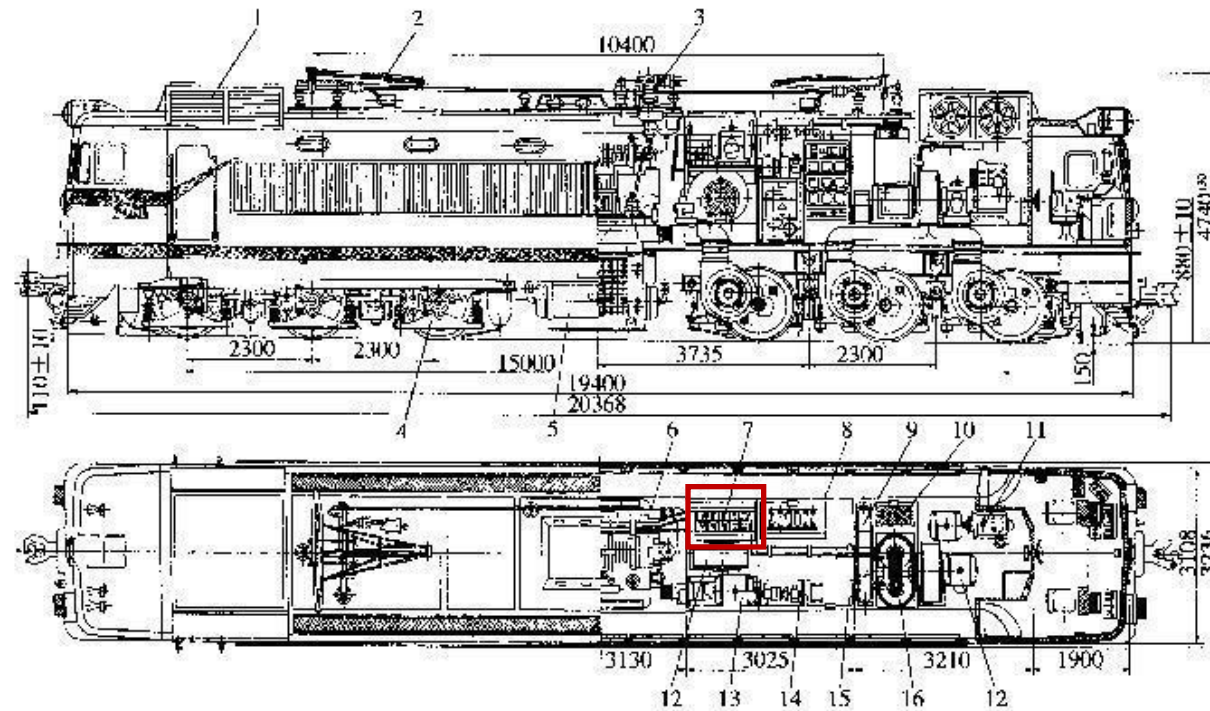


图 3·2·1-1 SS₁ 型电力机车总体布置

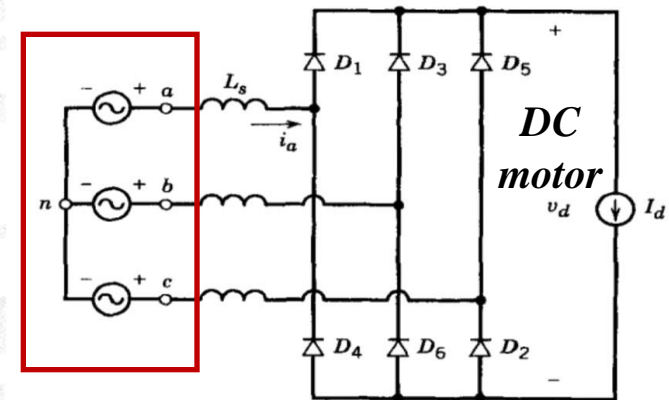
1—车体；2—受电弓；3—主断路器；4—转向架；5—主风缸；6—主变压器；7—整流柜；8—高压柜；9—蓄电池箱；10—电源柜（I）/励磁柜（II）；11—压缩机；12—牵引通风机；13—劈相机；14—控制柜（I）/升弓压缩机（II）；15—低压柜；16—平波电抗器。



SS1, 1968




AC source w/
tapped transformer

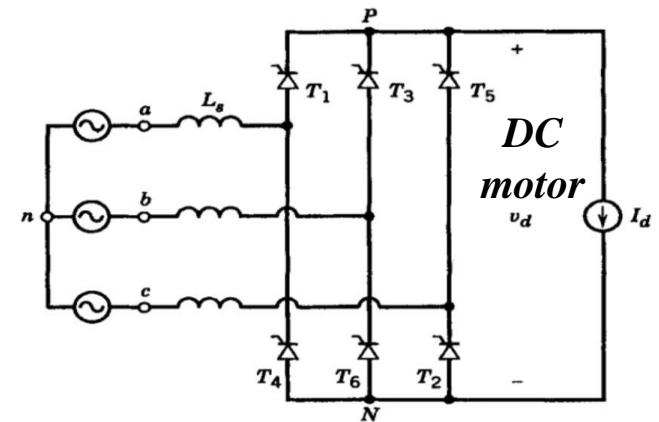

Thyristor-based AC/DC

Summary:

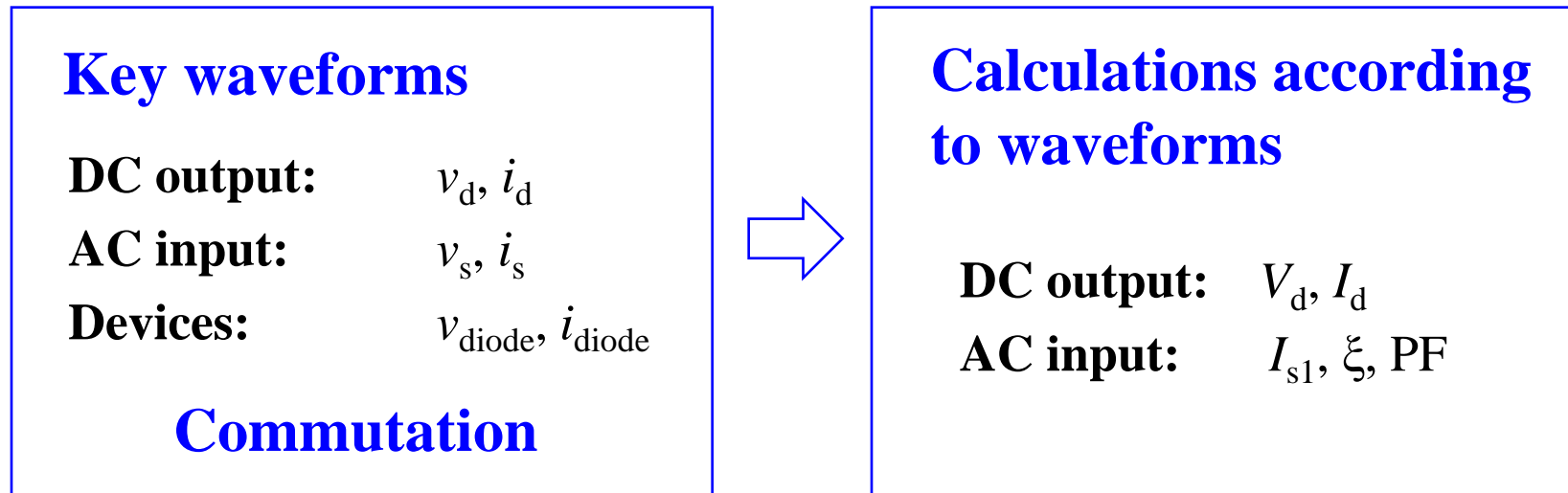
- Diode rectifier: uncontrolled AC-DC
- Function analysis according to key waveforms



Considering impact of load and ac-side inductance

Required both for single-phase and three-phase diode rectifiers

The End

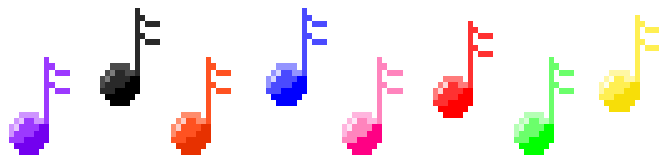

Supplement 2-1 Harmonics and Power Factor

Harmonic analysis

Any periodic waveform can be expressed mathematically as a Fourier series.

$$f = f_{\text{mean}} + \sum a_n \sin n\omega t + \sum b_n \cos n\omega t$$

$$f_{\text{mean}} = (1/2\pi) \int_0^{2\pi} f d(\omega t)$$

$$a_n = (1/\pi) \int_0^{2\pi} f \sin n\omega t d(\omega t), \quad b_n = (1/\pi) \int_0^{2\pi} f \cos n\omega t d(\omega t)$$

$$f_{n(\text{rms})} = 1/1.414 \cdot (a_n^2 + b_n^2)^{1/2}$$

$$f_{\text{rms}} = (f_{\text{mean}}^2 + \sum f_{n(\text{rms})}^2)^{1/2}$$

$$f_{R(\text{rms})} = (\sum f_{n(\text{rms})}^2)^{1/2}$$

$$\gamma_f = f_{R(\text{rms})} / f_{\text{mean}} \text{ — ripple factor (DC voltage)}$$

$$\xi_f = f_{1(\text{rms})} / f_{\text{rms}} \text{ — distortion factor (AC current)}$$



Power factor

$$\lambda = P/S$$

P – active mean power: $P = U_0 I_0 + \Sigma U_{n(rms)} I_{n(rms)} \cos \phi_n$

S – apparent power: $S = U_{rms} I_{rms}$

supply phase voltage — sinusoidal

$$P = U_{1(rms)} I_{1(rms)} \cos \phi_1, \quad S = U_{1(rms)} I_{rms}$$

$$\lambda = \xi_i \cos \phi_1$$

ξ_i — input current distortion factor

$\cos \phi_1$ — input displacement factor

